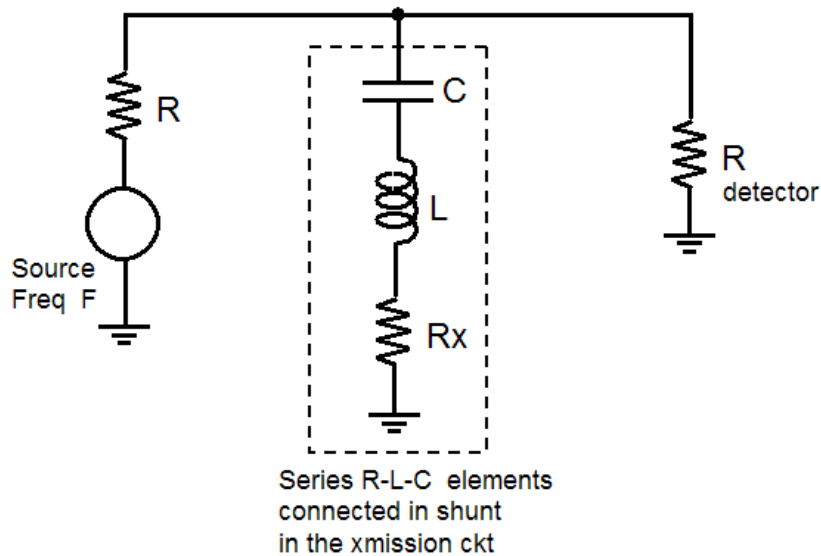


**CALCULATIONS OF L, C in a SERIES CIRCUIT using Leq and Ceq where Leq and Ceq are the apparent values as seen above and below the resonant frequency.**

**See: EXAMPLE OF COMPLETE Rx - L - C CALCULATIONS pages 4 - 6 below as implemented in my Excel file**

Jacques Audet



Note that the real part of Rx-L-C impedance is always Rx.  
It will not influence the calculations of the Leq and Ceq values.

Z<sub>LC\_SERIE</sub> with Rx

$$Z = j \cdot 2 \cdot \pi \cdot F \cdot L + \frac{1}{j \cdot 2 \cdot \pi \cdot F \cdot C} + R_x \quad \text{general expression}$$

$$Z = R_x + \frac{4 \cdot \pi^2 \cdot C \cdot F^2 \cdot L - 1}{2 \cdot \pi \cdot C \cdot F} \cdot j$$

**If Z is inductive**

$$L_{eq} = \frac{\left(4 \cdot \pi^2 \cdot F^2 \cdot L \cdot C - 1\right)}{2 \cdot \pi \cdot F \cdot C}$$

$$L_{eq} = \frac{4 \cdot \pi^2 \cdot F^2 \cdot L \cdot C - 1}{4 \cdot \pi^2 \cdot F^2 \cdot C} \quad \text{eq A}$$

**If Z is capacitive**  $X_c = \frac{4 \cdot \pi^2 \cdot C \cdot F^2 \cdot L - 1}{2 \cdot \pi \cdot C \cdot F} = \frac{1}{2 \cdot \pi \cdot F \cdot C_{eq}} \quad \frac{4 \cdot \pi^2 \cdot C \cdot F^2 \cdot L - 1}{2 \cdot \pi \cdot C \cdot F} = \frac{-1}{2 \cdot \pi \cdot F \cdot C_{eq}}$

Solving for Ceq:

$$C_{eq} = \frac{C}{1 - 4 \cdot \pi^2 \cdot C \cdot F^2 \cdot L} \quad \text{eq B}$$

### Example

$$F1 := 146 \cdot 10^6 \quad L := 100 \cdot 10^{-9} \quad C := 20 \cdot 10^{-12} \quad R_x := 0.1$$

Resonant frequency :  $F_r := \frac{1}{2 \cdot \pi \cdot \sqrt{L \cdot C}} \quad F_r = 1.125 \times 10^8$

Since  $F1 > F_r$  then Z is inductive

$$Z := j \cdot 2 \cdot \pi \cdot F1 \cdot L + \frac{1}{j \cdot 2 \cdot \pi \cdot F1 \cdot C} + R_x \quad Z = 0.1 + 37.229i$$

$$L_{eq} := \frac{4 \cdot \pi^2 \cdot F1^2 \cdot L \cdot C - 1}{4 \cdot \pi^2 \cdot F1^2 \cdot C} \quad L_{eq} = 4.058 \times 10^{-8}$$

Since  $F2 < F_r$  then Z is capacitive

$$F2 := 100 \cdot 10^6$$

$$Z := j \cdot 2 \cdot \pi \cdot F2 \cdot L + \frac{1}{j \cdot 2 \cdot \pi \cdot F2 \cdot C} + R_x \quad Z = 0.1 - 16.746i$$

$$C_{eq} := \frac{C}{1 - 4 \cdot \pi^2 \cdot C \cdot F2^2 \cdot L} \quad C_{eq} = 9.504 \times 10^{-11}$$

$$L_{eq} = \frac{4 \cdot \pi^2 \cdot F1^2 \cdot L \cdot C - 1}{4 \cdot \pi^2 \cdot F1^2 \cdot C} \quad \text{eq A with F replaced by F1}$$

$$C_{eq} = \frac{C}{1 - 4 \cdot \pi^2 \cdot C \cdot F2^2 \cdot L} \quad \text{eq B with F replaced by F2}$$

Solve for C in eq. B:

$$C = \frac{C_{eq}}{4 \cdot \pi^2 \cdot C_{eq} \cdot L \cdot F_2^2 + 1} \quad \text{eq C}$$

eq. C into eq. A:

$$L_{eq} = \frac{4 \cdot \pi^2 \cdot F_1^2 \cdot L \cdot C - 1}{4 \cdot \pi^2 \cdot F_1^2 \cdot C} \quad \text{eq A}$$

$$L_{eq} = -\frac{4 \cdot \pi^2 \cdot C_{eq} \cdot L \cdot F_2^2 - 4 \cdot \pi^2 \cdot C_{eq} \cdot L \cdot F_1^2 + 1}{4 \cdot \pi^2 \cdot C_{eq} \cdot F_1^2} \quad \text{eq D}$$

solve for L=

$$L = \frac{4 \cdot \pi^2 \cdot C_{eq} \cdot L_{eq} \cdot F_1^2 + 1}{4 \cdot \pi^2 \cdot C_{eq} \cdot F_1^2 - 4 \cdot \pi^2 \cdot C_{eq} \cdot F_2^2} \quad \text{eq E}$$

$$L = \frac{4 \cdot \pi^2 \cdot C_{eq} \cdot L_{eq} \cdot F_1^2 + 1}{4 \cdot \pi^2 \cdot C_{eq} \cdot (F_1^2 - F_2^2)} \quad \text{eq E rearranged}$$

Check :

$$L := \frac{4 \cdot \pi^2 \cdot C_{eq} \cdot L_{eq} \cdot F_1^2 + 1}{4 \cdot \pi^2 \cdot C_{eq} \cdot (F_1^2 - F_2^2)} \quad L = 1 \times 10^{-7} \quad \text{We get the initial value of L}$$

Sub eq E into eq C:

$$C = \frac{C_{eq}}{4 \cdot \pi^2 \cdot C_{eq} \cdot L \cdot F_2^2 + 1} \quad \text{eq C}$$

$$C = \frac{C_{eq} \cdot F_1^2 - C_{eq} \cdot F_2^2}{4 \cdot \pi^2 \cdot C_{eq} \cdot L_{eq} \cdot F_1^2 \cdot F_2^2 + F_1^2} \quad \text{eq F}$$

$$C = \frac{C_{eq} \cdot (F_1^2 - F_2^2)}{F_1^2 \cdot (4 \cdot \pi^2 \cdot C_{eq} \cdot L_{eq} \cdot F_2^2 + 1)} \quad \text{eq F rearranged}$$

Check :

$$C := \frac{C_{eq} \cdot (F_1^2 - F_2^2)}{F_1^2 \cdot (4 \cdot \pi^2 \cdot C_{eq} \cdot L_{eq} \cdot F_2^2 + 1)} \quad C = 2 \times 10^{-11} \quad \text{We get the initial value of C}$$

Calculating the L-C series elements from Leq and Ceq  
in a (R) ohm system after measuring attenuation  
below and above the resonant frequency

F1 is the highest frequency with a corresponding attenuation: dB1

F2 is the lowest frequency with a corresponding attenuation: dB2

As shown above:

$$L = \frac{4 \cdot \pi^2 \cdot C_{eq} \cdot L_{eq} \cdot F1^2 + 1}{4 \cdot \pi^2 \cdot C_{eq} \cdot (F1^2 - F2^2)} \quad \text{eq E}$$

$$C = \frac{C_{eq} \cdot (F1^2 - F2^2)}{F1^2 \cdot (4 \cdot \pi^2 \cdot C_{eq} \cdot L_{eq} \cdot F2^2 + 1)} \quad \text{eq F}$$

## EXAMPLE OF COMPLETE Rx - L - C CALCULATIONS

CALCULATE Rx from the (negative) attenuation measured in dB at the frequency of minimum transmission:  
FR

R is the load and source resistance.

**Calculation of Rx** (The reactances of L and C cancel at resonance)

$$\text{MHz} := 10^6 \quad R := 50 \quad \text{dB} := -40.5926 \quad FR := 150 \cdot \text{MHz}$$

On mesure Rx à cette freq

Calculating the shunt resistance Rx:

See: [Calcul\\_RparV11a.mcd](#) or [Calcul\\_RparV11a.pdf](#)

$$R_x(\text{dB}) := \frac{1}{2} \cdot \frac{R \cdot 10^{\frac{\text{dB}}{20}}}{\left(1 - 10^{\frac{\text{dB}}{20}}\right)} \quad R_x(\text{dB}) = 0.23571$$

$$R_x := R_x(\text{dB})$$

F1 is the highest freq. corresponding to dB1 (dB)

$$F1 := 160 \cdot \text{MHz}$$

$$F2 := 149 \cdot \text{MHz}$$

$$\text{dB1} := -7.24306$$

$$\text{dB2} := -25.8895$$

### Calculation of Leq et Ceq

$$\text{att1(dB)} := 10^{\frac{\text{dB1}}{20}}$$

$$\text{att2(dB)} := 10^{\frac{\text{dB2}}{20}}$$

Attenuations in dB are converted to linear attenuation: att1 and att2

The equivalent Inductance Leq may be calculated:

See: [Calcul\\_Lpar-avecRX-V11a.mcd](#) or [Calcul\\_Lpar-avecRX-V11a.pdf](#)

$$\text{Leq(dB1)} := \frac{\sqrt{4 \cdot \text{att1(dB1)}^2 \cdot R_x^2 + 4 \cdot R \cdot R_x \cdot \text{att1(dB1)}^2 + R^2 \cdot \text{att1(dB1)}^2 - 4 \cdot R_x^2}}{4 \cdot \pi \cdot F1 \cdot \sqrt{1 - \text{att1(dB1)}^2}}$$

The equivalent Capacitance Ceq may be calculated:

See: [Calcul\\_Cpar-avecRX-V11a.mcd](#) or [Calcul\\_Cpar-avecRX-V11a.pdf](#)

$$\text{Ceq(dB2)} := \frac{\sqrt{1 - \text{att2(dB2)}^2}}{\pi \cdot F2 \cdot \sqrt{4 \cdot \text{att2(dB2)}^2 \cdot R_x^2 + 4 \cdot R \cdot R_x \cdot \text{att2(dB2)}^2 + R^2 \cdot \text{att2(dB2)}^2 - 4 \cdot R_x^2}}$$

$$\text{Leq(dB1)} = 1.21 \times 10^{-8}$$

$$\text{Ceq(dB2)} = 8.473 \times 10^{-10}$$

### Calculating the L-C series elements from Leq and Ceq:

$$L(\text{dB1}) := \frac{4 \cdot \text{Leq(dB1)} \cdot \pi^2 \cdot F1^2 \cdot \text{Ceq(dB1)} + 1}{4 \cdot \pi^2 \cdot \text{Ceq(dB1)} \cdot (F1^2 - F2^2)}$$

eq E

$$L(\text{dB1}) = 9.9945 \times 10^{-8}$$

$$C(\text{dB2}) := \frac{\text{Ceq(dB2)} \cdot (F1^2 - F2^2)}{4 \cdot F2^2 \cdot \text{Leq(dB2)} \cdot \pi^2 \cdot F1^2 \cdot \text{Ceq(dB2)} + F1^2}$$

eq F

$$C(\text{dB2}) = 1.12641 \times 10^{-11}$$

$$\text{Fres} := \frac{1}{2 \cdot \pi \cdot \sqrt{L(\text{dB1}) \cdot C(\text{dB2})}}$$

$$\frac{\text{Fres}}{\text{MHz}} = 150$$

$$\% \text{Error: } \frac{100 \cdot (\text{Fres} - \text{FR})}{\text{Fres}} = 3.004 \times 10^{-4}$$

### Calculating the quality factor: Q

$$Q := \frac{2 \cdot \pi \cdot \text{Fres} \cdot L(\text{dB1})}{R_x}$$

$$Q = 399.619$$

# SIMULATION WITH SUPERSTAR

