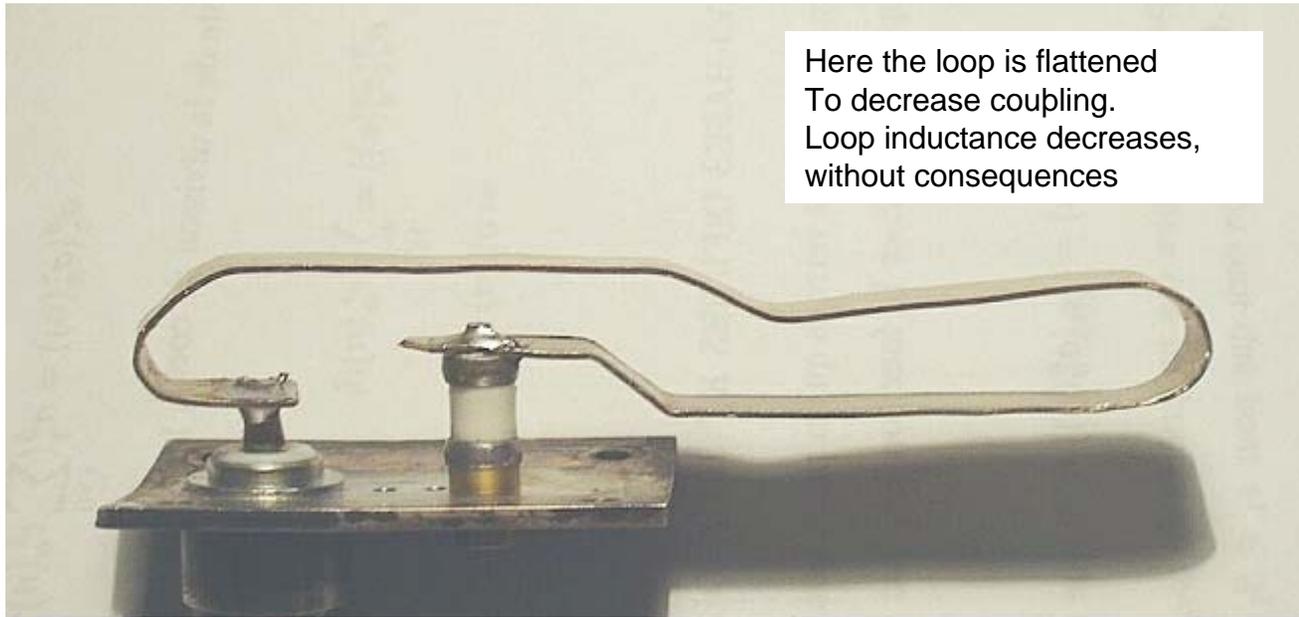


## *Tests on Various Duplexer Coupling Loops*

J. Audet  
VE2AZX

- 146 MHz Notch-Bandpass Cavities with 600 KHz TX-RX Separation.
- Loops uses a Series Capacitor
- Loop Shape must be modified to get the desired insertion loss at the bandpass frequency, when the loop cannot be rotated to change the coupling
- Loops Shapes were Tested for Insertion Loss at the Bandpass Frequency and Q factor
- Q Factor Measured Using the Excel file: Calc\_Series\_RLC.xls and by Using a Tee at the Connector and with the Cavity Cylinder Removed.

## RX CAVITY



Here the loop is flattened  
To decrease coupling.  
Loop inductance decreases,  
without consequences


$L = 59.5 \text{ nH}$   
 $C = 19.5 \text{ pF}$   
 $Q = 396$

This coupling loop gives  $\sim 0.5 \text{ dB}$  at the passband  
and  $-36 \text{ à } -37 \text{ dB}$  at the notch notch

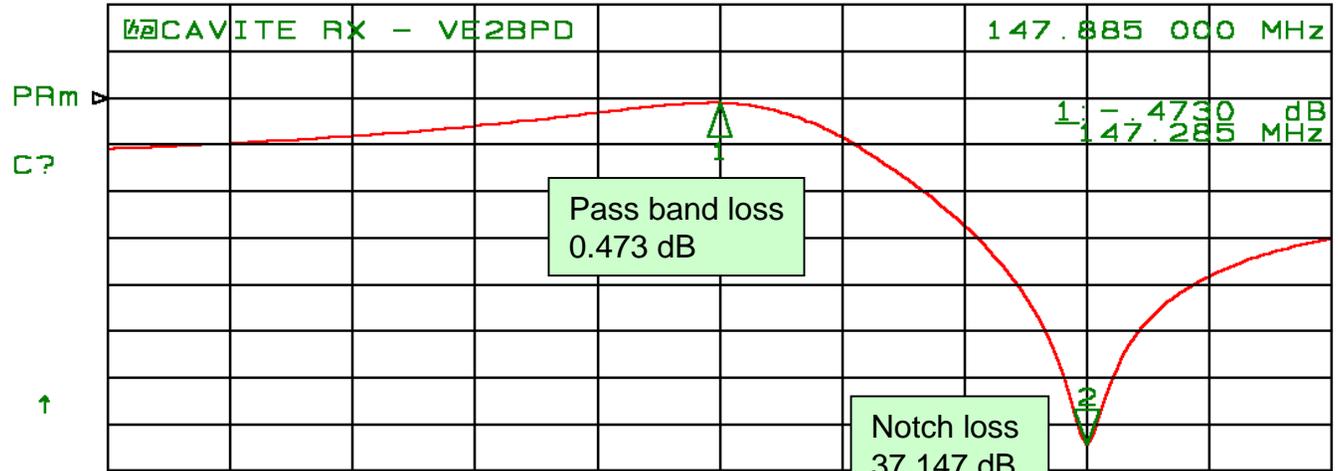
# RX CAVITY

19 May 2003 19:32:00



CH1 S<sub>21</sub> log MAG 5 dB/ REF 0 dB 2: -37.147 dB



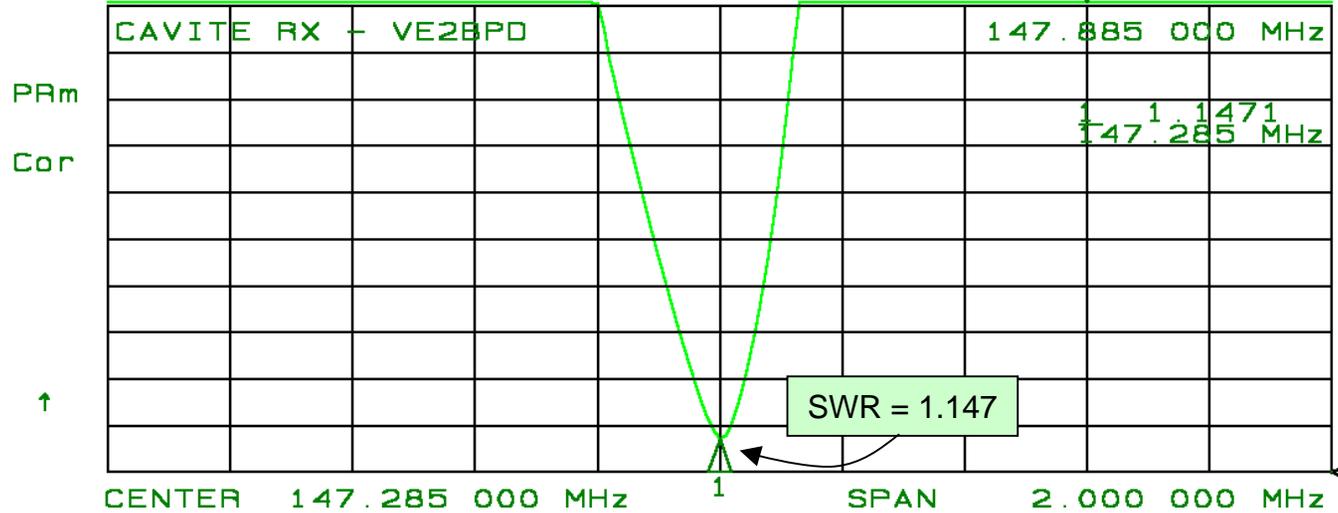CH2 S<sub>11</sub> SWR 200 m / REF 1 2: 46.273



## TX CAVITY - loop 1

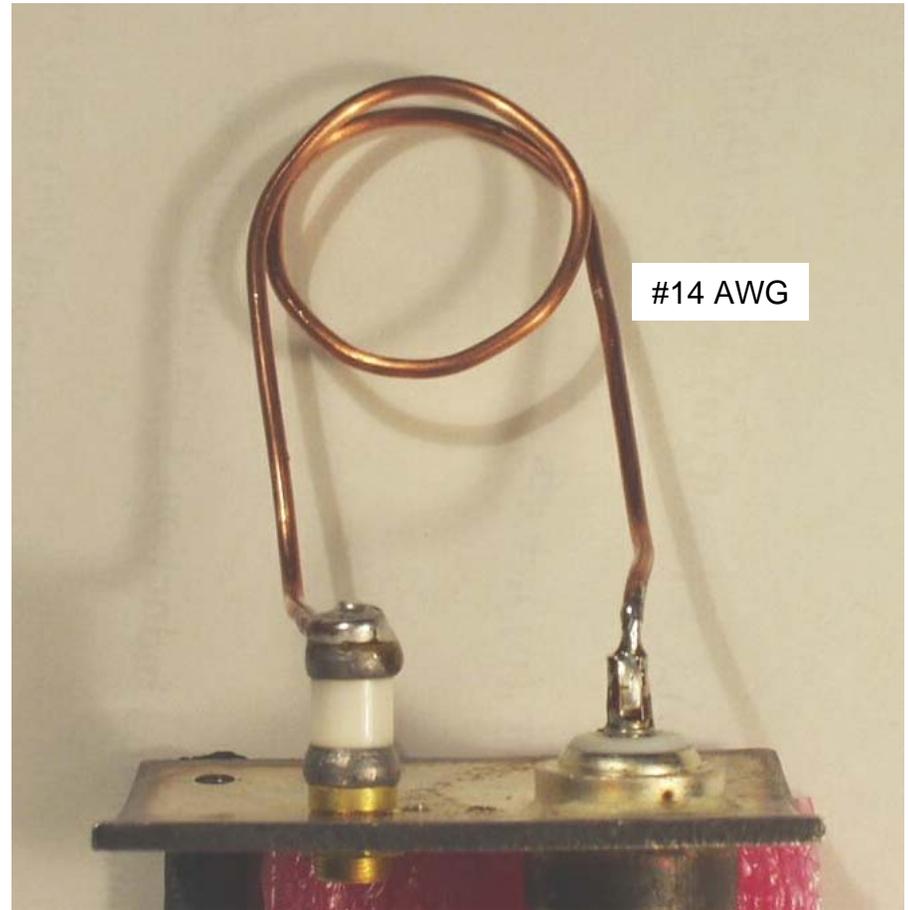
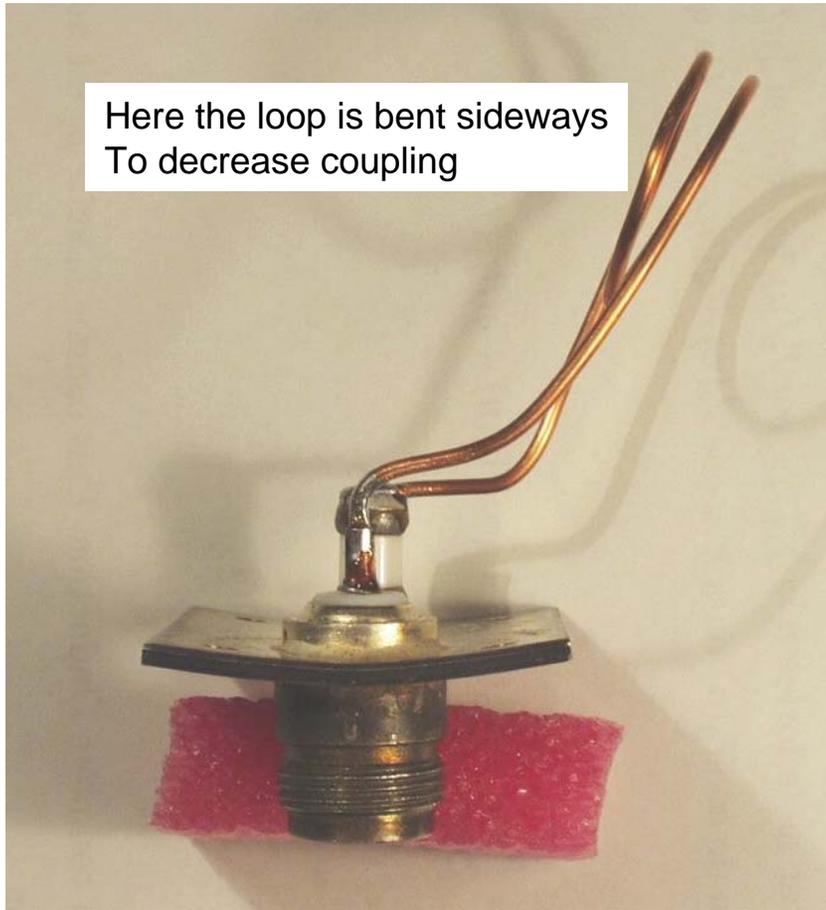


$L = 160.1 \text{ nH}$   
 $C = 7.28 \text{ pF}$   
 $Q = 707$   
 $\text{ESR} = 0.21 \text{ ohms}$


Note the high Q here.

# TX CAVITY - loop 1

19 May 2003 19:37:46

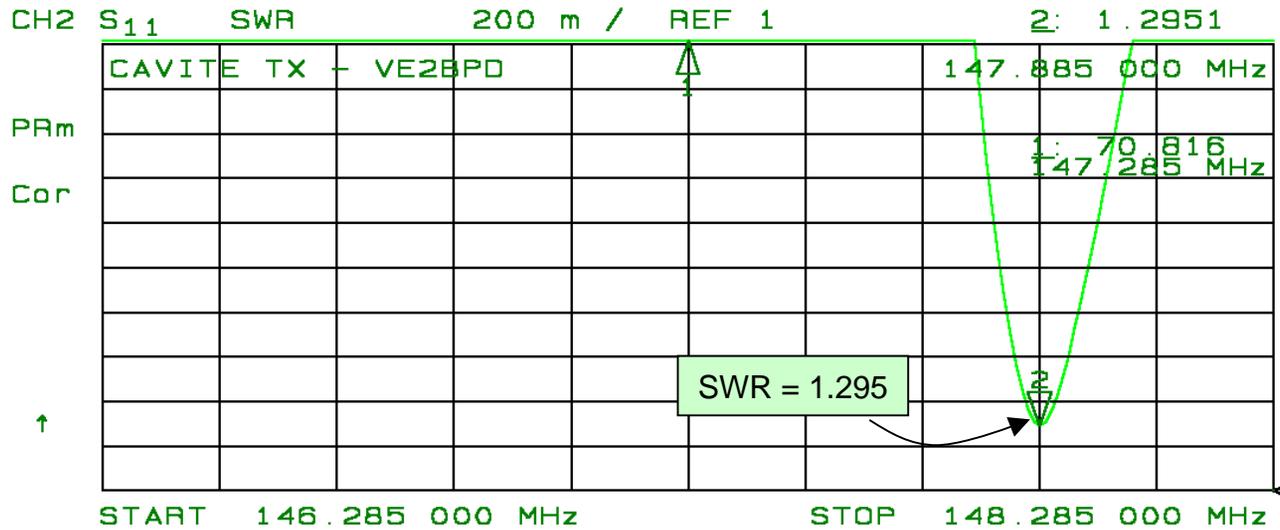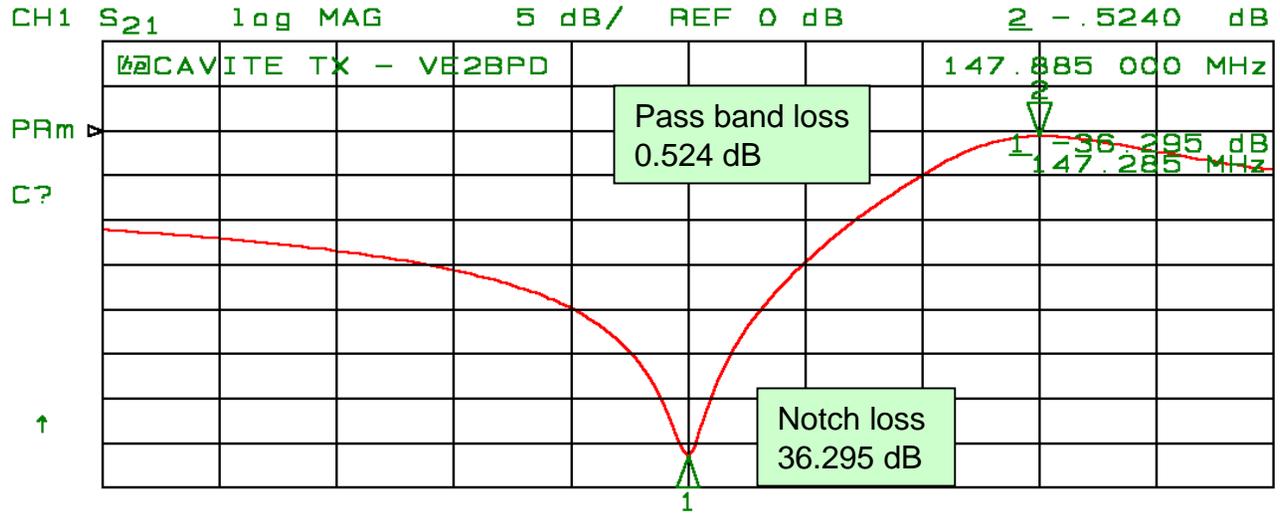


## TX CAVITY - loop 2

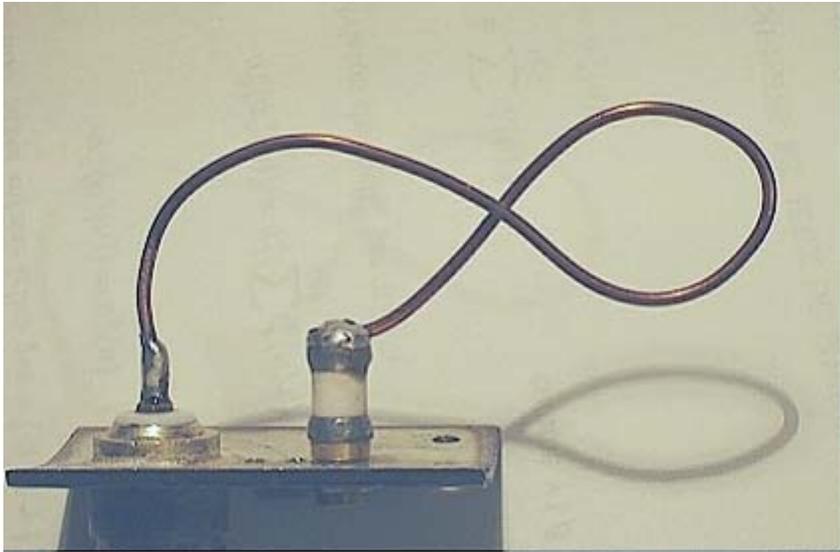

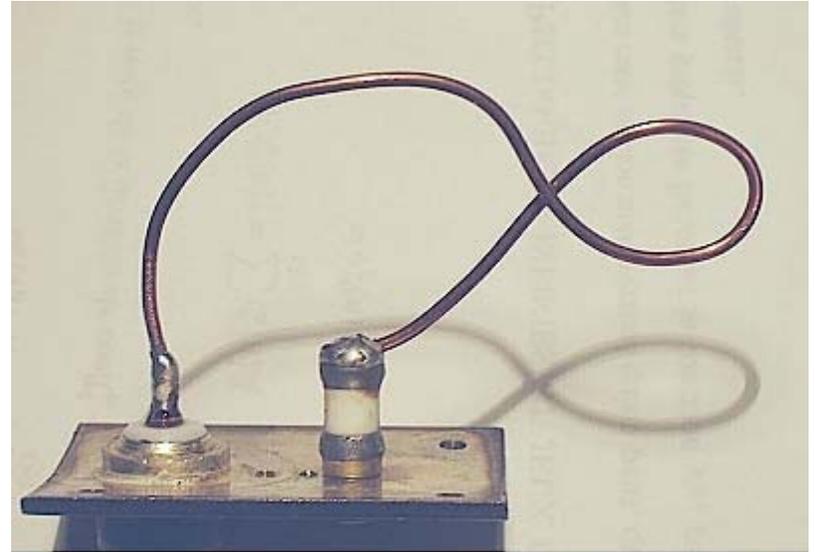5.2 dB passband loss  
The coupling is weak since both loops have about the same area.

NOTE: This loop with an 8 shape allows control of the coupling by changing the area of each loop. The magnetic field in each loop has opposite directions and partly cancel each other, reducing the inductance and coupling




0.5 dB passband loss  
This is the loop that was used.

$L = 103.2 \text{ nH}$   
 $C = 11.3 \text{ pF}$   
 $Q = 565$   
 $\text{ESR} = 0.169 \text{ ohms}$

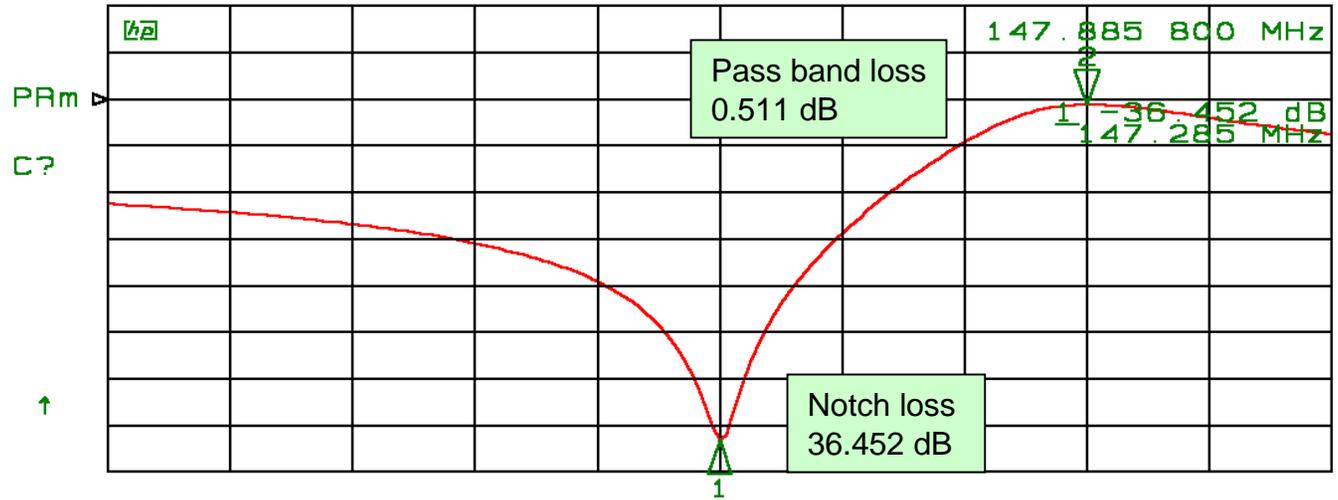
# TX CAVITY - loop 2

21 May 2003 19:42:24


CH1 S<sub>21</sub> log MAG 5 dB/ REF 0 dB 2 -0.5111 dB



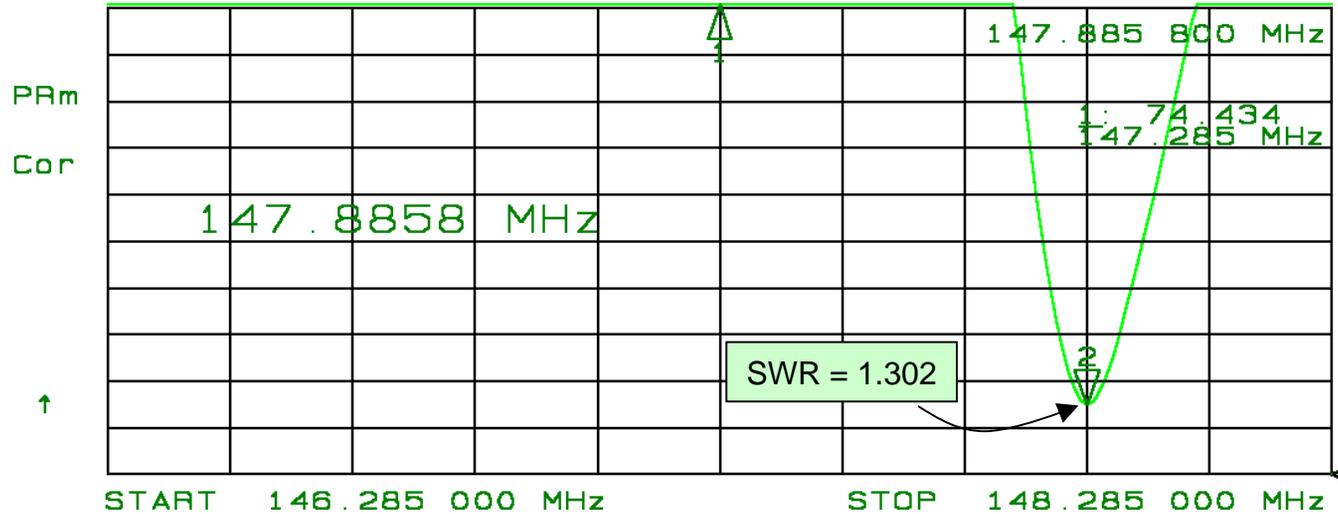CH2 S<sub>11</sub> SWR 200 m / REF 1 2: 1.3023


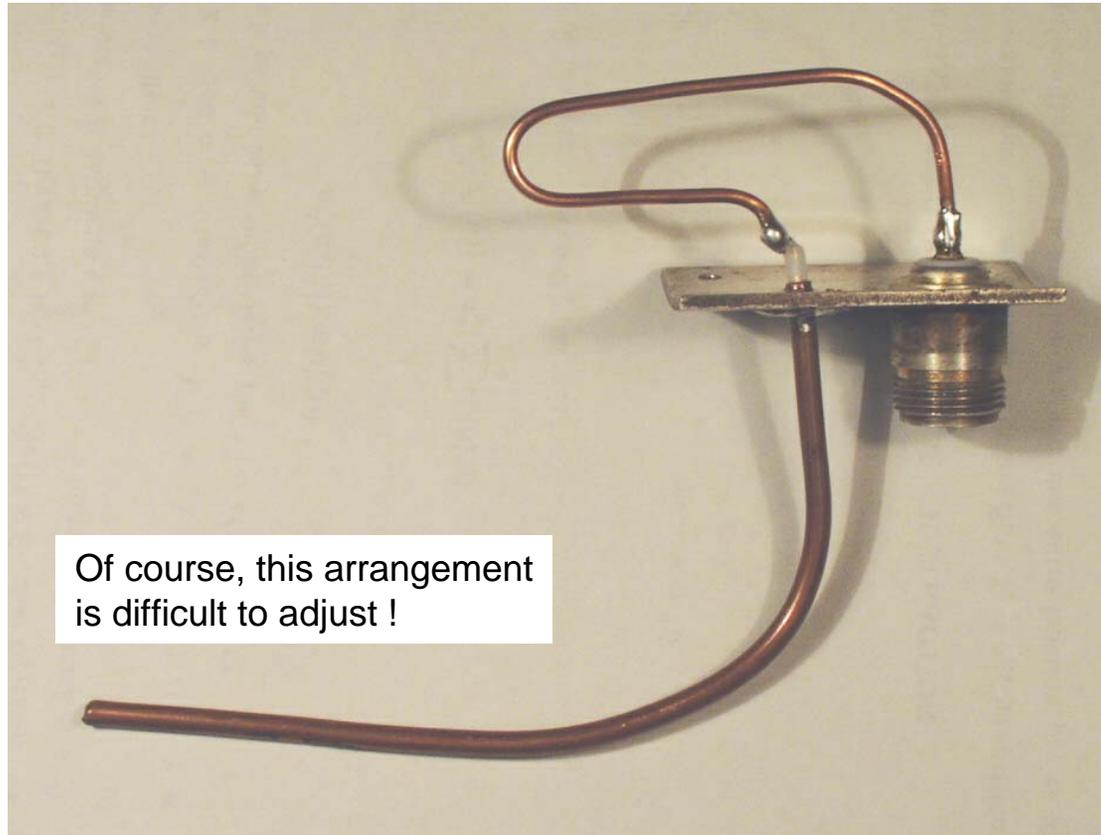
## RX CAVITY with semi-rigid coax for the capacitor





Note the lower Q here, but still OK.

$L = 85 \text{ nH}$   
 $C = 16 \text{ pF}$   
 $Q = 381$   
 $\text{ESR} = 0.191 \text{ ohms}$

# RX CAVITY with semi-rigid coax for the capacitor

21 May 2003 20:33:20

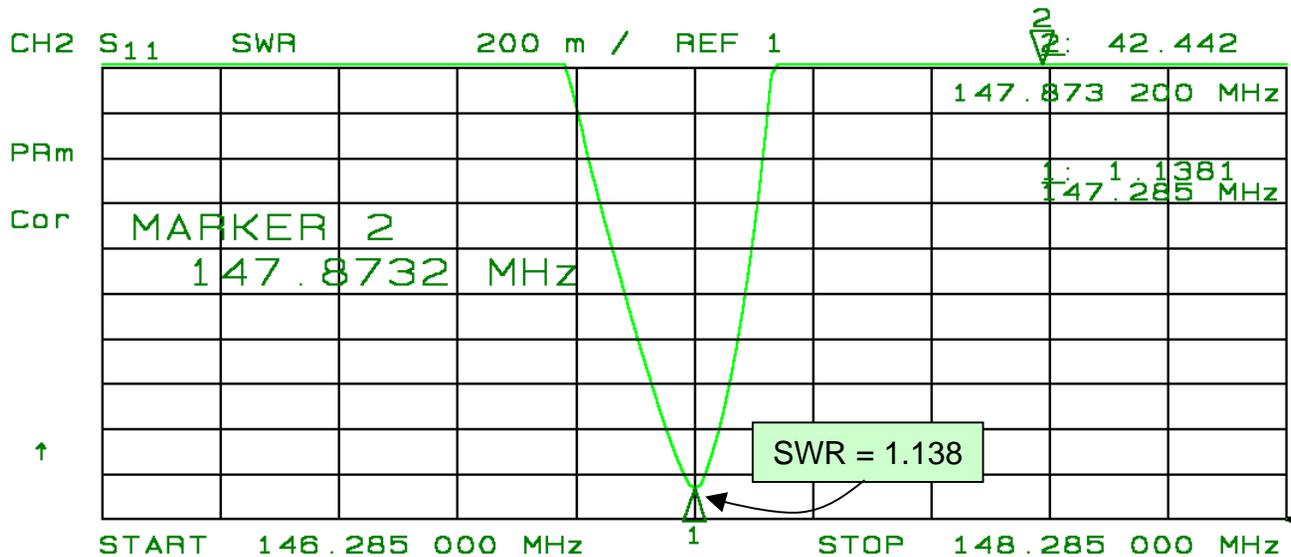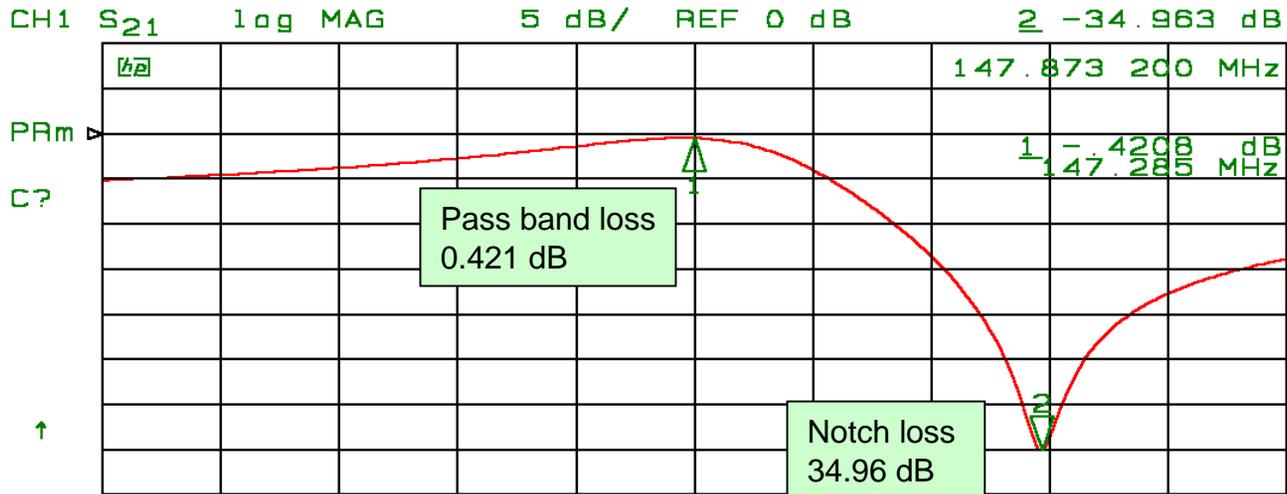

## Remember:

The size of the coupling loop is not that important.

You can make a bigger coupling loop and place it further away from the center resonator.

If the coupling is the same then big or small it makes little difference.

The size is not important, but the coupling is.

The only impedance associated with the loop itself, is its self inductance, which is not critical.

There are no 50 ohm loops as such.

Consider the bandpass cavity with an input and an output loop.

At the resonant frequency the impedance seen at the input will be close to 50 ohms IF the output is also terminated into 50 ohms.

Basically there is a one to one impedance transformation at the resonant frequency, assuming that the loops have the same number of turns and the bandpass filter is adjusted (read: coupling) for reasonable values of insertion loss.

So with the output loop terminated into 75 ohms, the input impedance will also be around 75 ohms.

What causes the input impedance to deviate from the output ?

It's the insertion loss. The higher the insertion loss, the more the input impedance will deviate from the output.

The losses associated with the cavity resonator are the main contributor to insertion losses.

Keep in mind that insertion loss is closely related to the input/output impedances.

In general, the lower the insertion losses, the lower the SWR will be at the input.