

IMPROVED MATCHING OF A SEVEN BAND ZS6BKW TYPE ANTENNA

Jacques Audet
VE2AZX
Dec. 2023

SUMMARY

The ZS6BKW antenna is an improved multi band version of the G5RV. It is a shortened dipole on 80m.

The ZS6BKW antenna needs two feeder lengths to cover 80, 40, 20, 17, 15, 12, 10m bands.

The shorter feeder is required on 80m and 15m, while the longer feeder is required to cover the other bands.

This means switching in an additional feeder length to cover the 40, 20, 17, 12, 10m bands.

Here I designed an inverted Vee version of the ZS6BKW that implements the additional feeder length using a Tee circuit: It uses two series inductors and a shunt capacitor connected in the middle.

The Tee circuit is optimized to limit the SWR to less than 2:1 on 40, 20, 17, 12m bands.

On 10m the SWR is less than 3:1 over the full band of 28 MHz to 29.7 MHz.

The Tee matching circuit is connected between the ladder line and the 50 ohm coax balun.

It is switched in/out using two DPDT relays which are operated via DC voltage on the coax feeder.

SWR losses are minimized since the matching circuit is connected at the end of the ladder line.

The 80m band does not use any matching and was set to provide the minimum VSWR at 3750 KHz.

This SWR minimum is around 3.5:1, when measured at the end of a 50 foot length of RG-8.

Simulations show that it is possible to add the 80m band to the 40, 20, 17, 12, 10m bands by adding a series capacitor, as shown on pages 22 and 23.

The 15m band uses an optional correction circuit that shifts the resonance slightly at midband.

The L – C – L circuit must be bypassed for this band.

This is a well balanced antenna that minimize the RX noise and the TX shield currents.

SIMULATIONS using Eznec+ V6.0

Wires


Ref: G5RV-Inverted Vee NO TRL 2x 39.5pi.ez

Wire Create Edit Other


☐ Coord Entry Mode ☐ Preserve Connections ☒ Show Wire Insulation

Wires													
	No.	End 1				End 2				Diameter	Segs	Insulation	
		X (ft)	Y (ft)	Z (ft)	Conn	X (ft)	Y (ft)	Z (ft)	Conn			Diel C	Thk (in)
	1	0	-1	47	W3E1	0	-39.5	20		#12	31	1	0
▶	2	0	1	47	W3E2	0	39.5	20		#12	31	1	0
	3	0	-1	47	W1E1	0	1	47	W2E1	#12	1	1	0
*													

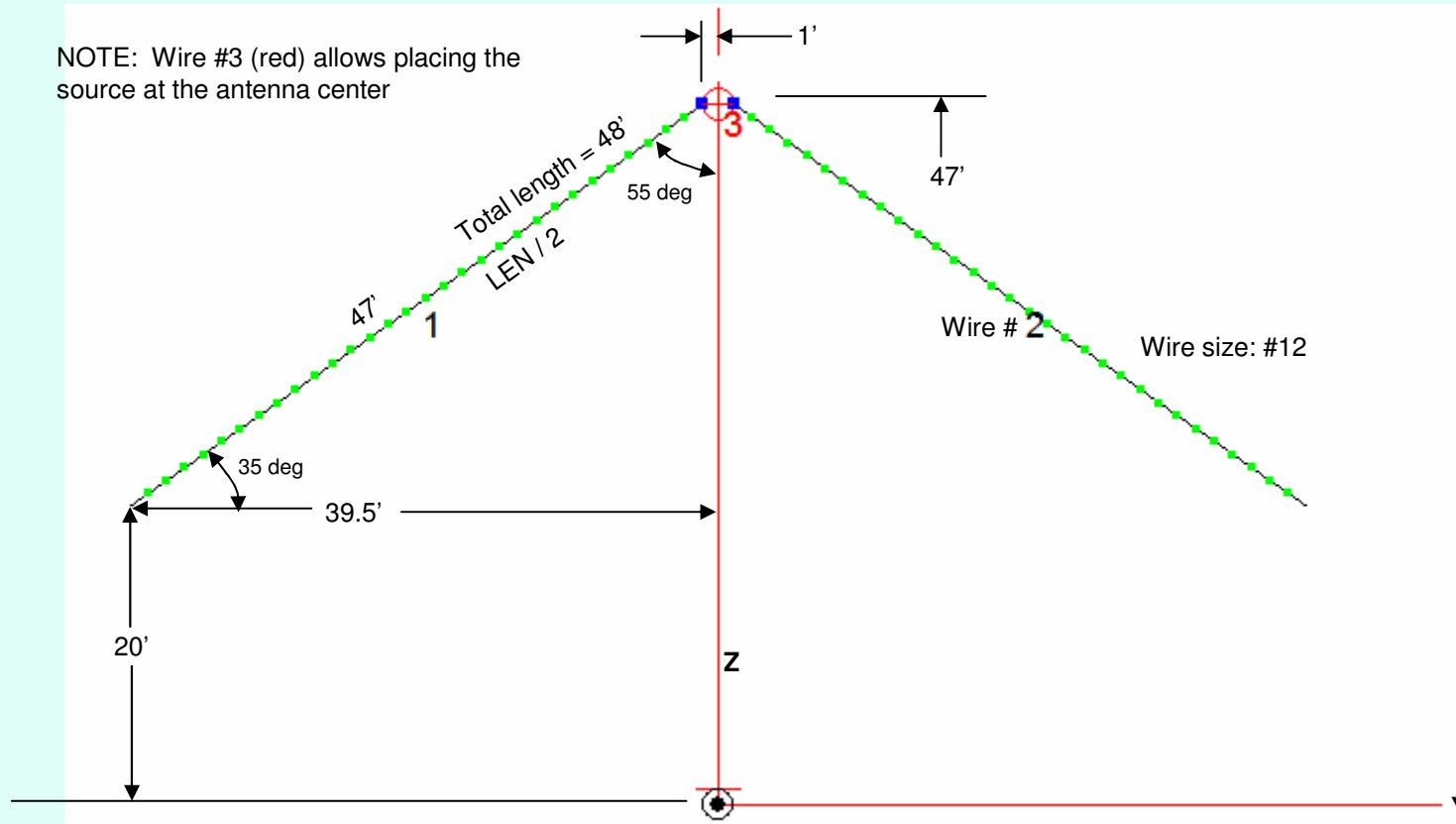NOTE: Wire #3 (red) allows placing the source at the antenna center




INVERTED VEE as BUILT

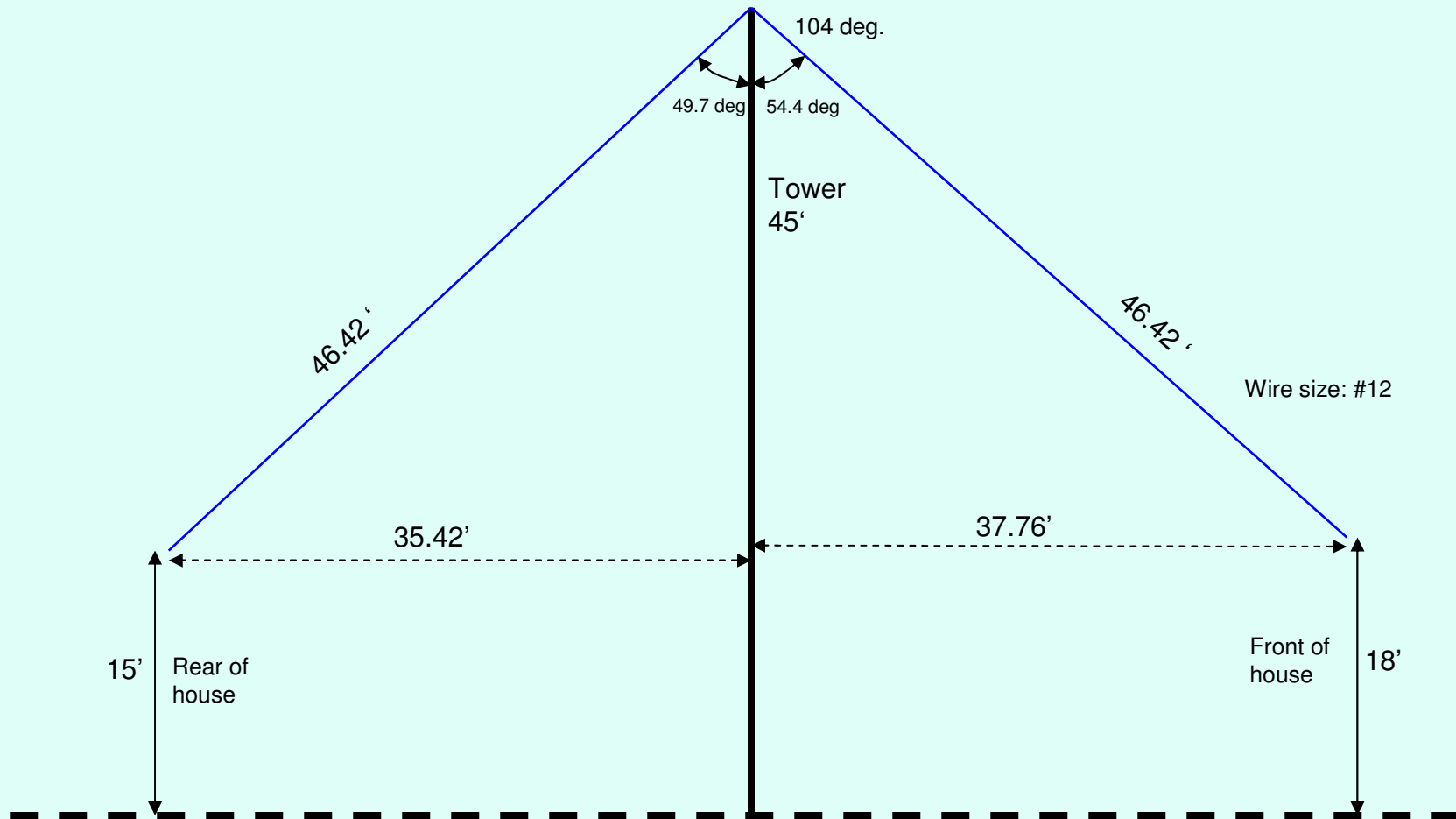

Delhi Tower: $48' - (6 \text{ sections} * 6'') = 45'$

Antenna wire length = $50' - 43'' = 46.42'$ after adjustment with short feeder to give SWR minimum at 3.75 MHz.

SIMULATIONS RESULTS

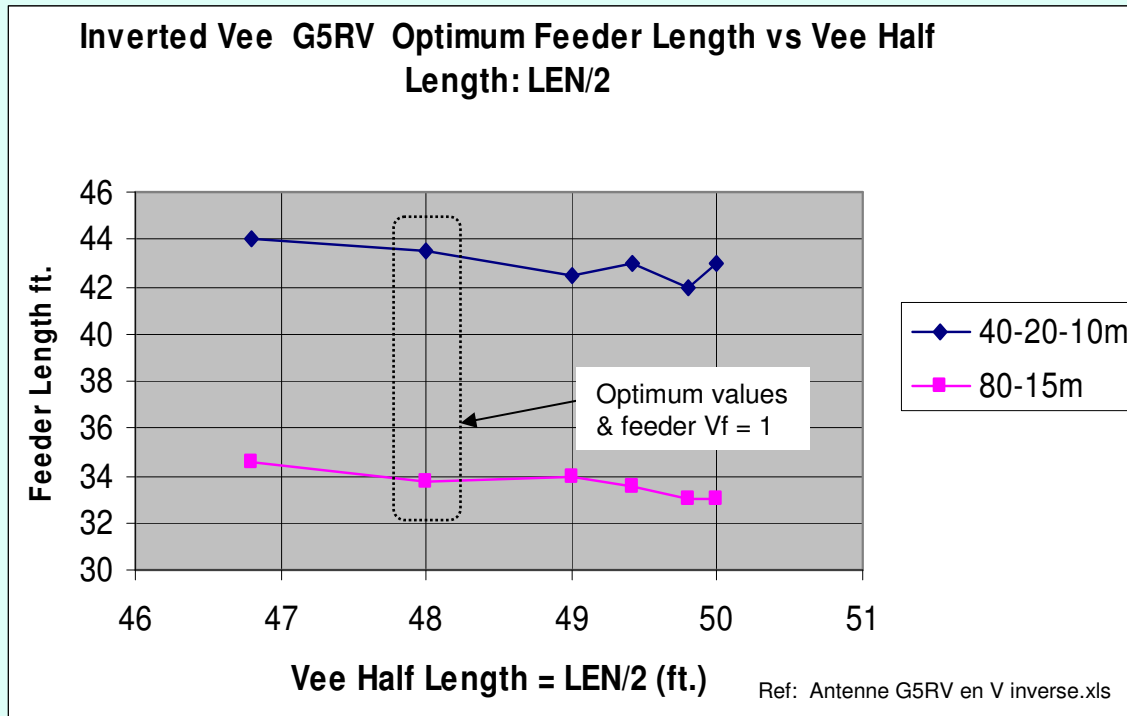

- The optimum combination of Vee half length and feeder length is found first at 80 and 15m.
- Then the feeder length is increased to optimize VSWR on 10, 12, 17, 20, 40m.
- The feeder impedance used in the simulations was 400 Ω .

Optimum Values found from simulations, Giving best VSWR from 10, 12, 15, 17, 20, 40, 80m

Vee Half Length = LEN/2 = 48 ft.

Feeder = 33.7 ft @ 15m and 80m ($V_f=1$)

Feeder = 43.5 ft @ 10, 12, 17, 20, 40m ($V_f=1$)

Note that the dipole first resonance (F_o) occurs at 4.875 MHz
The second resonance ($3.F_o$) occurs at 14.625 MHz
The third resonance ($5.F_o$) occurs at 24.375 MHz

The 33.7 ft feeder quarter wave resonance occurs at 7.3 MHz, 21.9 MHz
The 33.7 ft feeder half wave resonance occurs at 14.6 MHz.

The 43.5 ft feeder quarter wave resonance occurs at 5.6 MHz, 17 MHz
The 43.5 ft feeder half wave resonance occurs at 11.3 MHz.

Velocity Factor Measurement on my '400' ohms Transmission Line

$Z = \text{SQRT}(L/C)$ Where L measured with line shorted, C is measured with line opened.

$L = 10.457 \mu\text{H}$ $C = 62.025 \text{ pF}$ measured @ 100 KHz with my UT612 LCR Meter.

$Z = 410.6 \Omega$ This value will be used in the simulations.

c = speed of light λ =wavelength f in Hz V_f = velocity factor len = length of TRL in feet

$$c = 3 \cdot 10^8 \frac{\text{m}}{\text{sec}} \quad c = 9.84 \cdot 10^8 \frac{\text{feet}}{\text{sec}} \quad c := 9.84 \cdot 10^8$$

$$\lambda \cdot f = c \cdot V_f$$

$$V_f = \frac{\lambda \cdot \text{len} \cdot f}{c}$$

$\lambda = 2$ for 180 deg resonance, Test in series transmission mode
 $\lambda = 4$ for 90 deg resonance Test in shunt transmission mode

$$\text{len} := 22.167 \quad \lambda := 2 \quad f := 19.89 \text{ MHz}$$

$$V_f := \frac{\lambda \cdot \text{len} \cdot f \cdot 10^6}{c} \quad V_f = 0.896$$

$$\text{len} := 22.167 \quad \lambda := 4 \quad f := 9.9 \text{ MHz}$$

$$V_f := \frac{\lambda \cdot \text{len} \cdot f \cdot 10^6}{c} \quad V_f = 0.892$$

Averaged V_f used = 0.894

TRL = $33.7 \cdot 0.894 = 30.13 \text{ ft} = 30 \text{ ft} + 1.5 \text{ in.}$

NOTE: 33.7 ft is the value used for antenna simulations with $V_f = 1$
 Initial feeder length = 30 ft + 1.5 in.

The revised feeder length is 29 ft + 9.6 in. after subtracting 4 in. (from the matching circuit)

REPLACING THE 9.8 FT FEEDER BY L – C CIRCUITS

Feeder = 33.7 ft @ 15m and 80m (@ $V_f=1$)

Adding 9.8 ft is required to obtain the 43.5 ft below to cover the five additional bands.

Feeder = 43.5 ft @ 10, 12, 17, 20, 40m (@ $V_f=1$)

The additional 9.8 ft may be realized using a double PI circuit using 3 shunt caps and 2 series inductors.

The VSWR will remain unchanged when the 9.8 ft line or the double PI is switched in.

It was found that a double PI which behaves like a 550 ohms line will further improve the VSWR.

Is this an optimal solution ?

NO !

The double PI components values may be optimized to improve VSWR on 10, 12, 17, 20, 40m bands.

The result is a circuit having a Tee configuration, where we have:

L series ... Cshunt ... Lseries


Three components instead of five are now required to optimize matching.

And the VSWR is below 2:1 and centered on the 12, 17, 20, 40m bands and below 3:1 on 10m !

For the 10, 12, 17, 20, 40m bands, the new matching circuit is switched in with two DPDT relays using DC voltage sent on the coax feed line.


For the 80m and 15m bands the matching circuit is bypassed.

OPTIMIZED MATCHING CIRCUIT

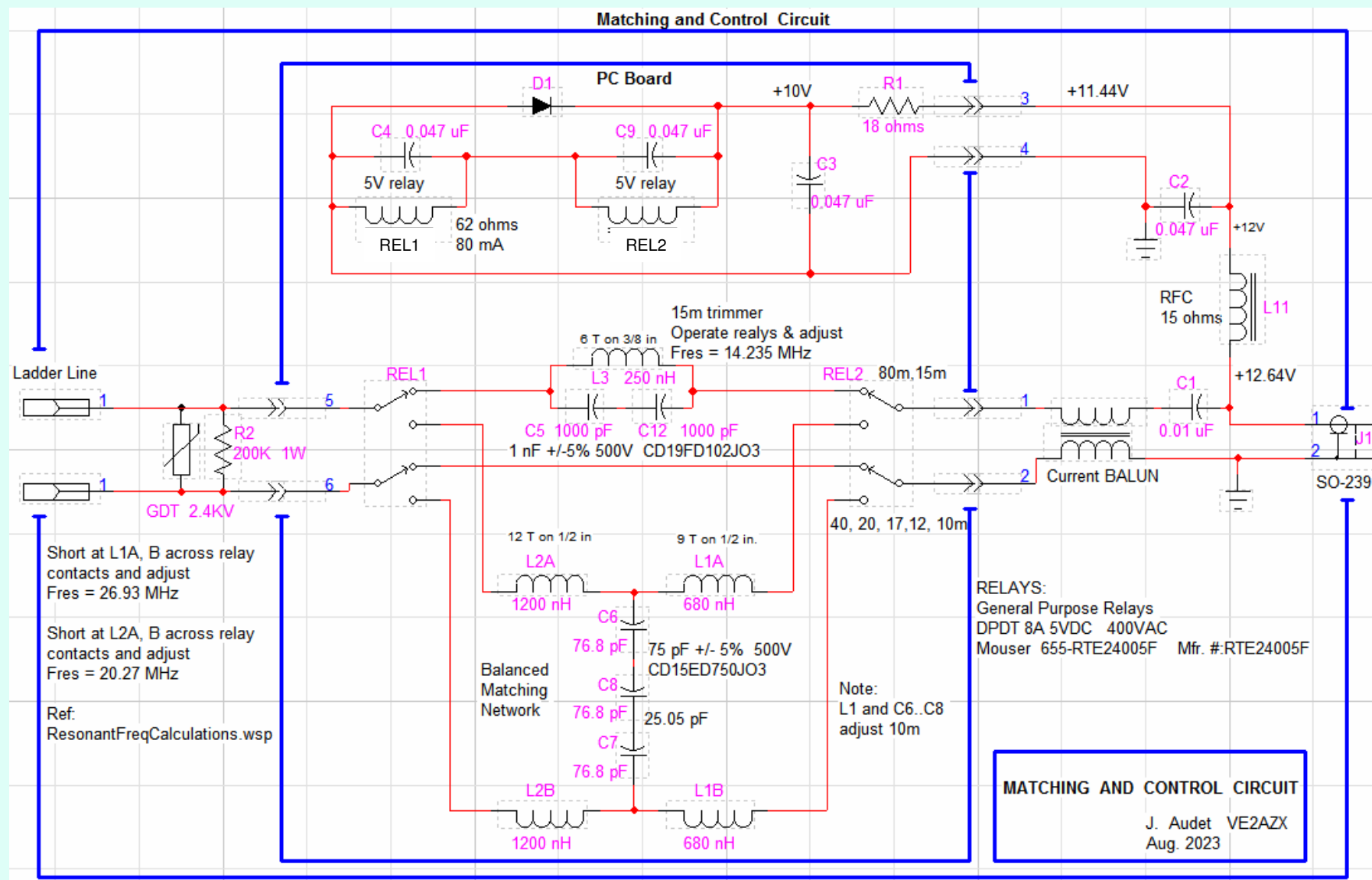




Ref.: Inverted Vee 80m to 10m-39.5_NO TRL.wsp

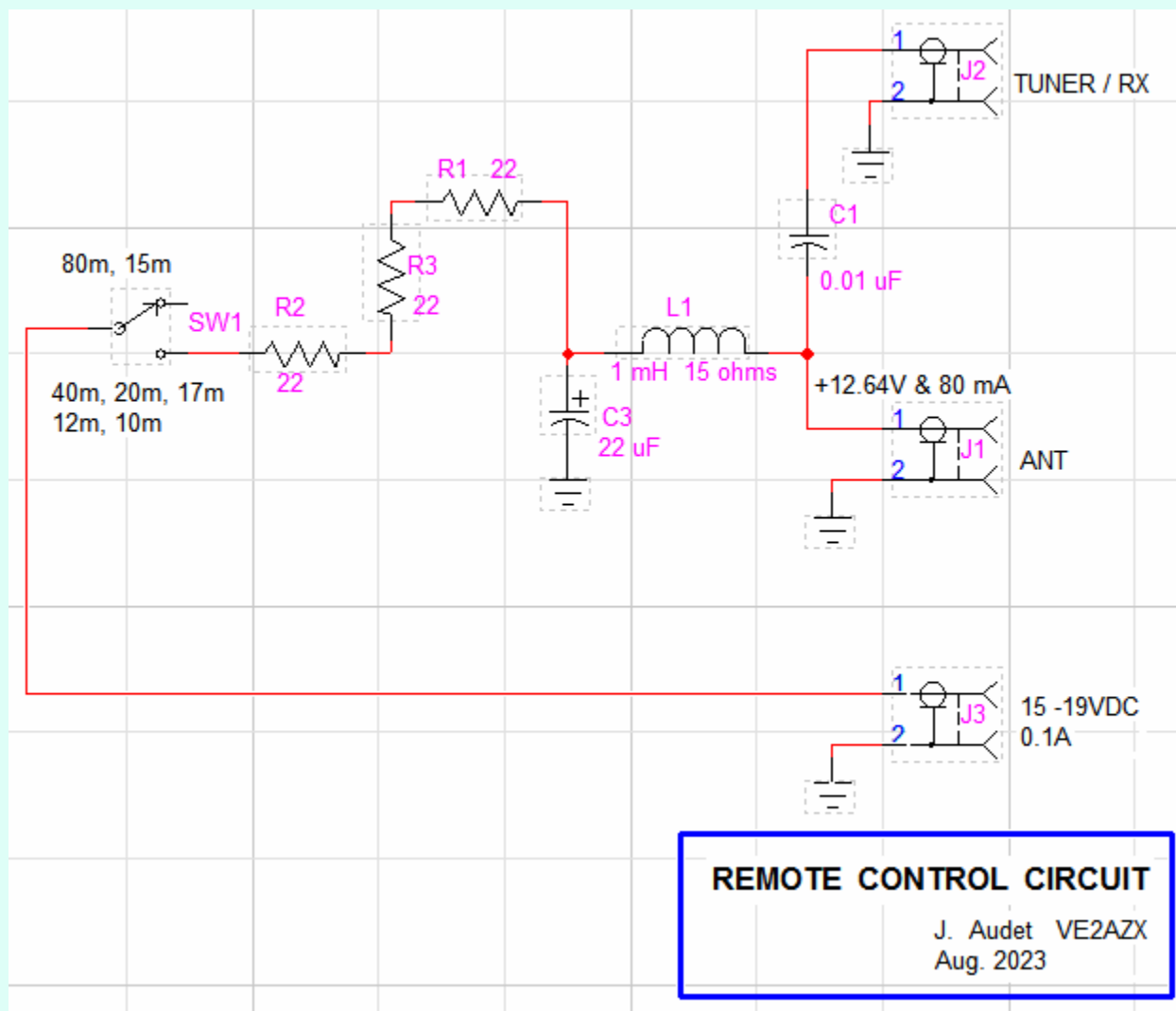Ref.: Inverted Vee 80m to 10m-39.5_NO TRL-Revised-TRL-Loss-50ohmFeederAdded-Compare w Mesures.wsp



COMPONENT LAYOUT

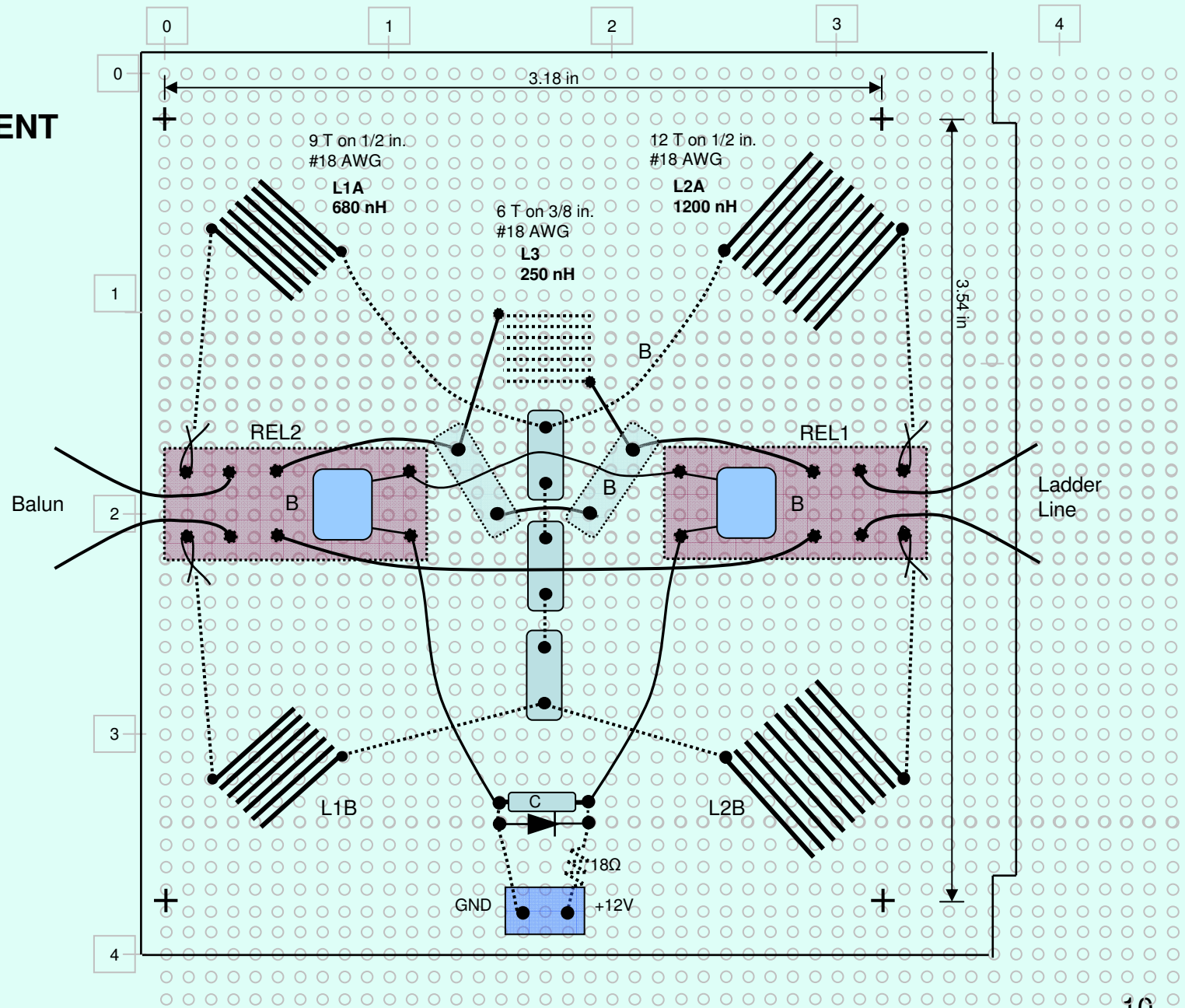


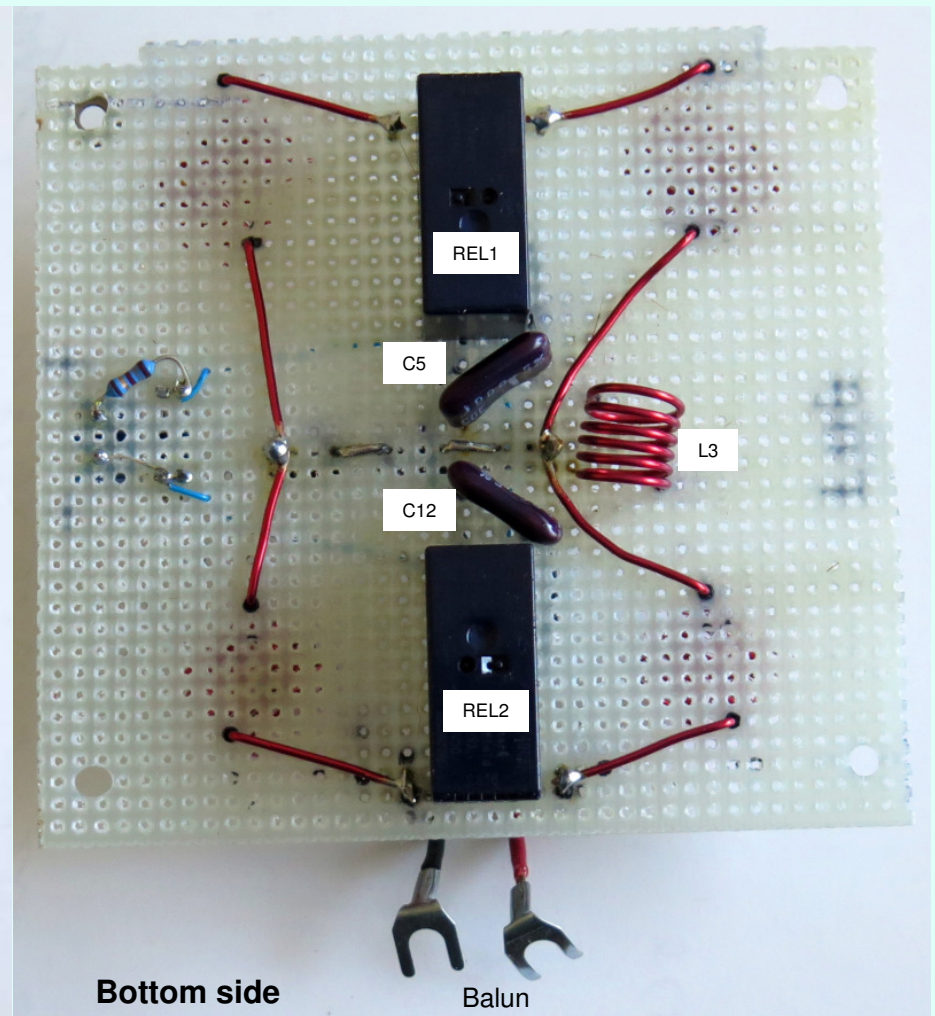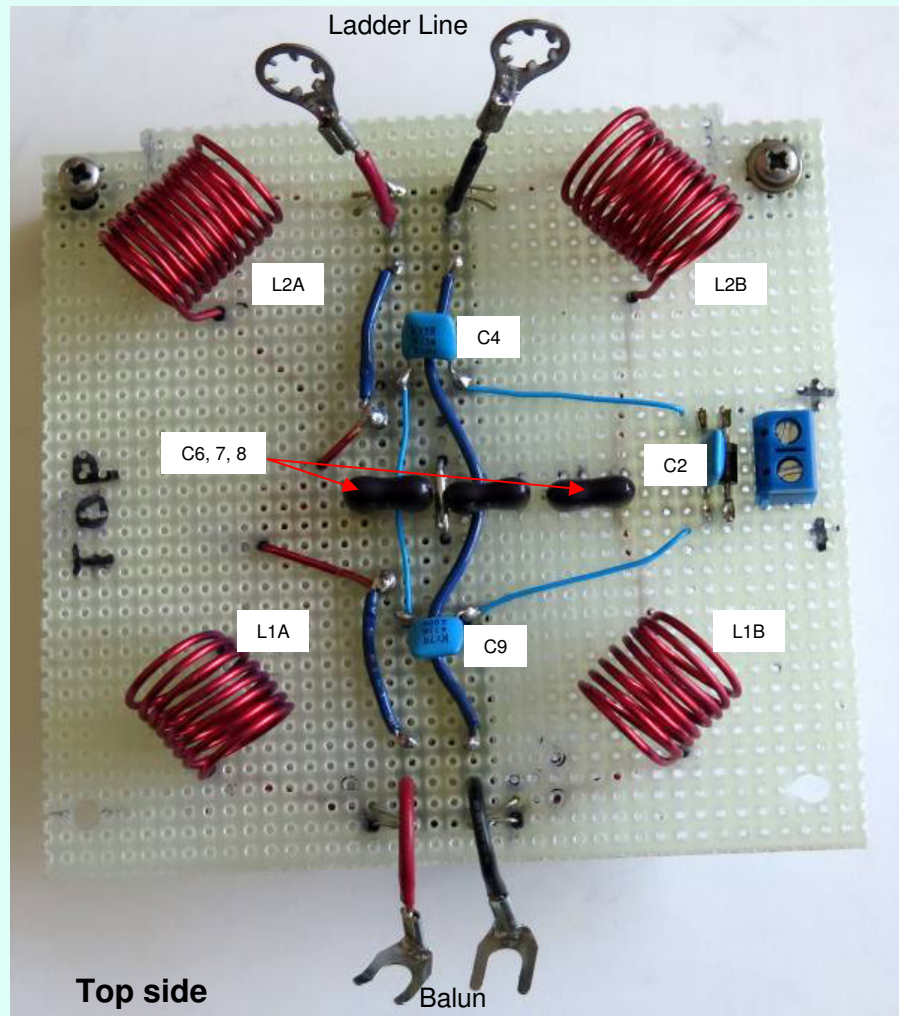

NOTE: The board was sprayed with silicone conformal coating to keep the moisture out.


BALUN, RELAYS and FILTER

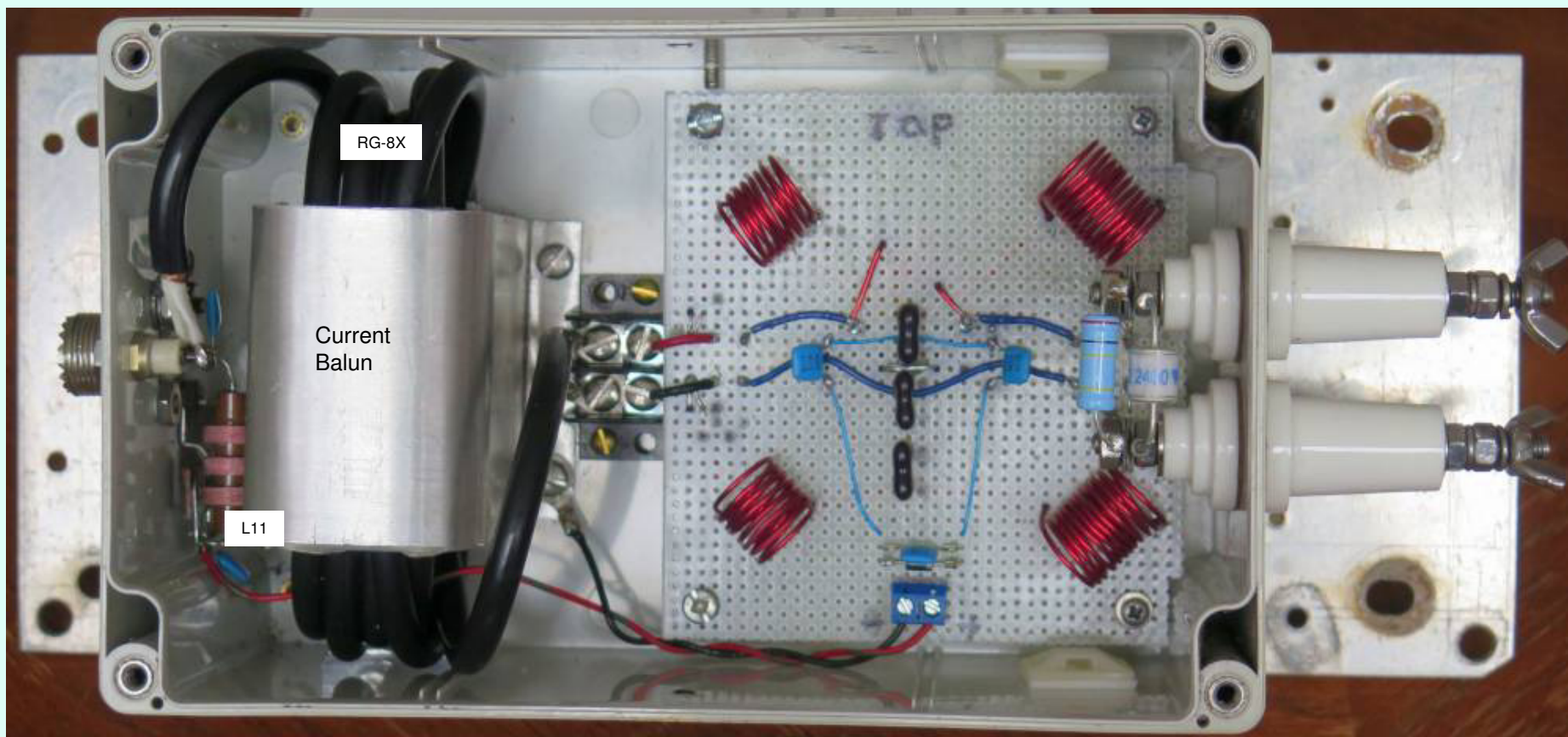Grey ABS plastic watertight enclosure Hammong Mfg. #1554UGY or 1554U2GY




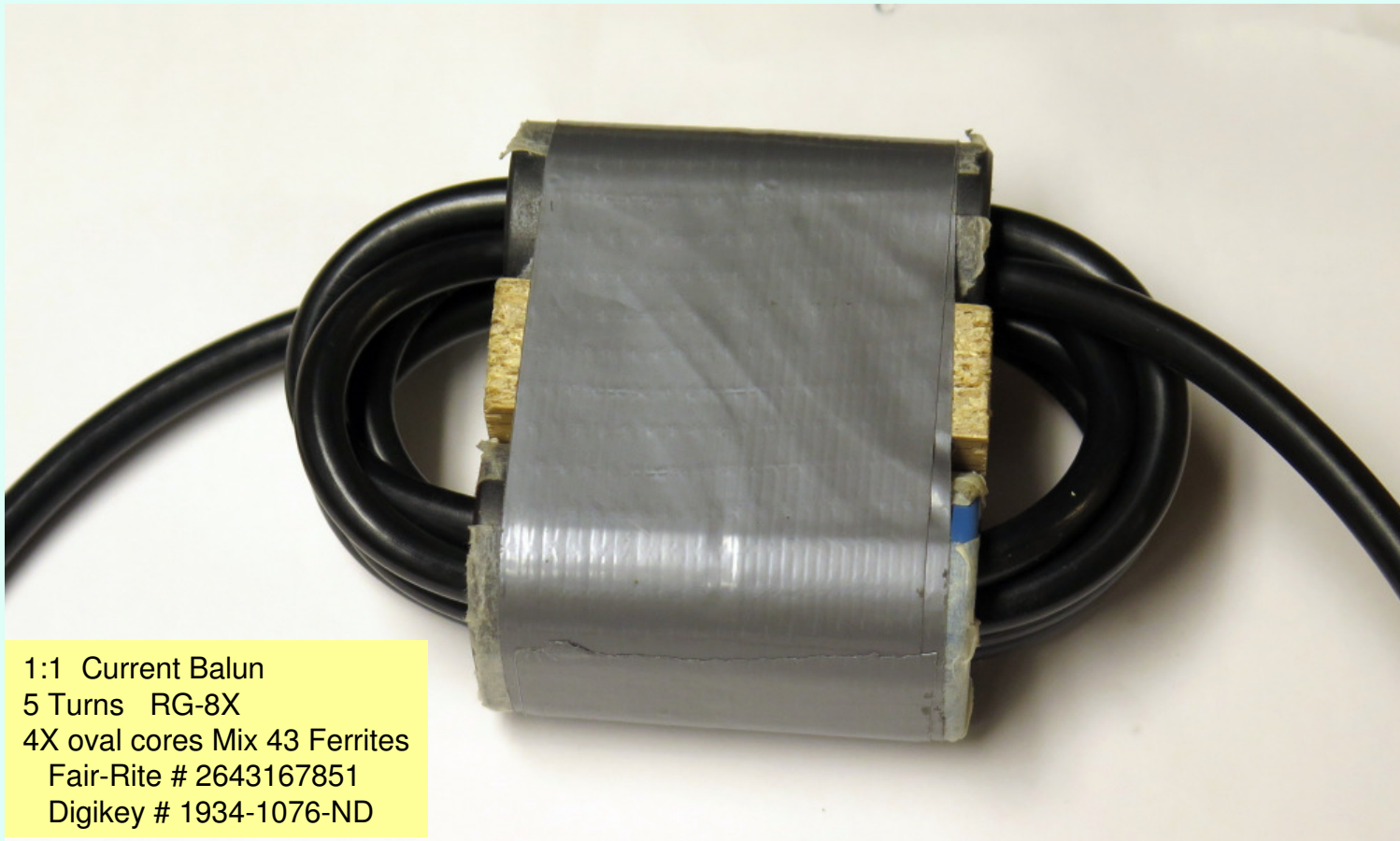1:1 Current Balun


Provides 2500 Ω to 8000 Ω over 3.5 to 30 MHz



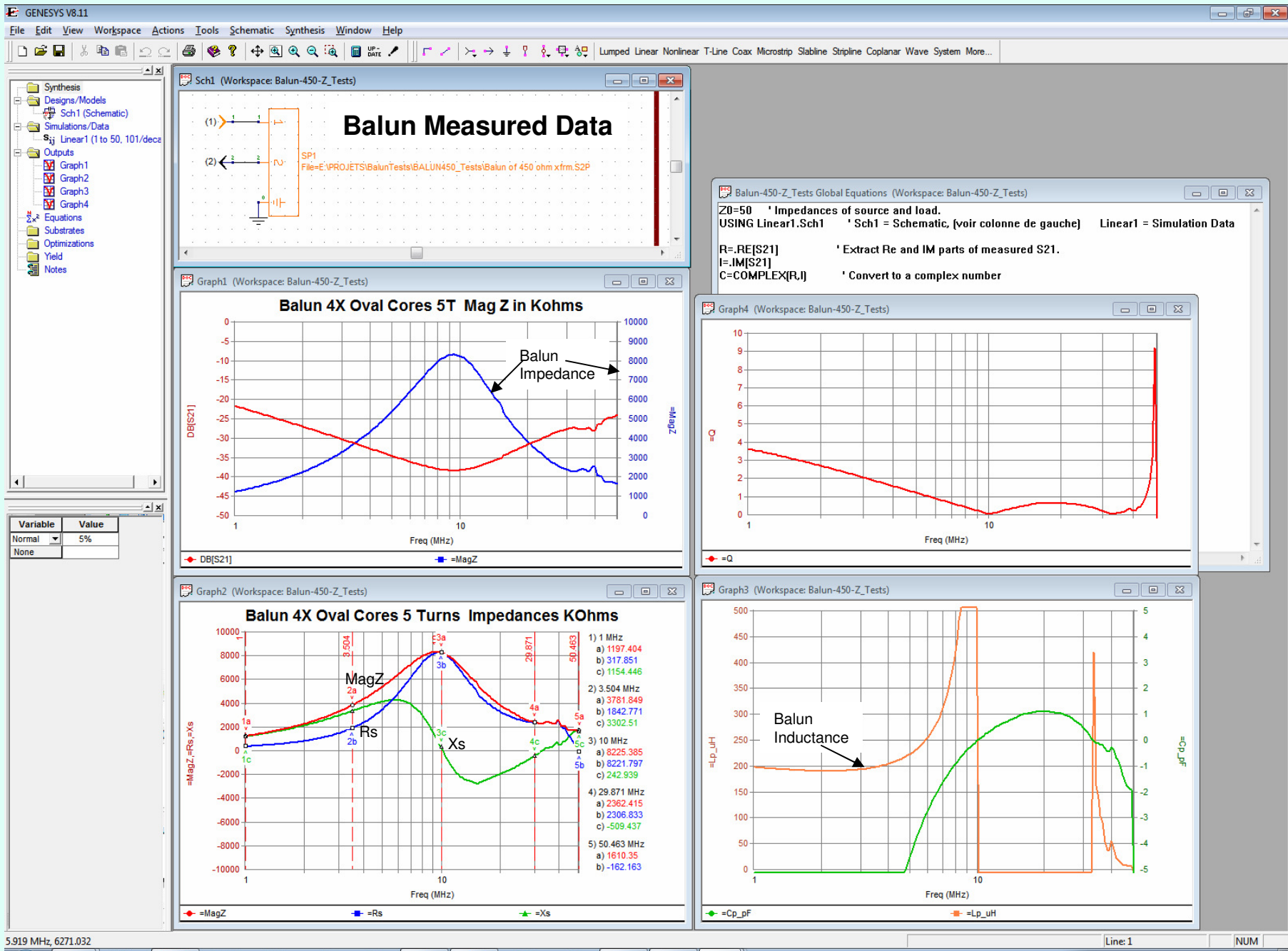1:1 Current Balun
5 Turns RG-8X
4X oval cores Mix 43 Ferrites
Fair-Rite # 2643167851
Digikey # 1934-1076-ND



Installed Matching and Control Circuit

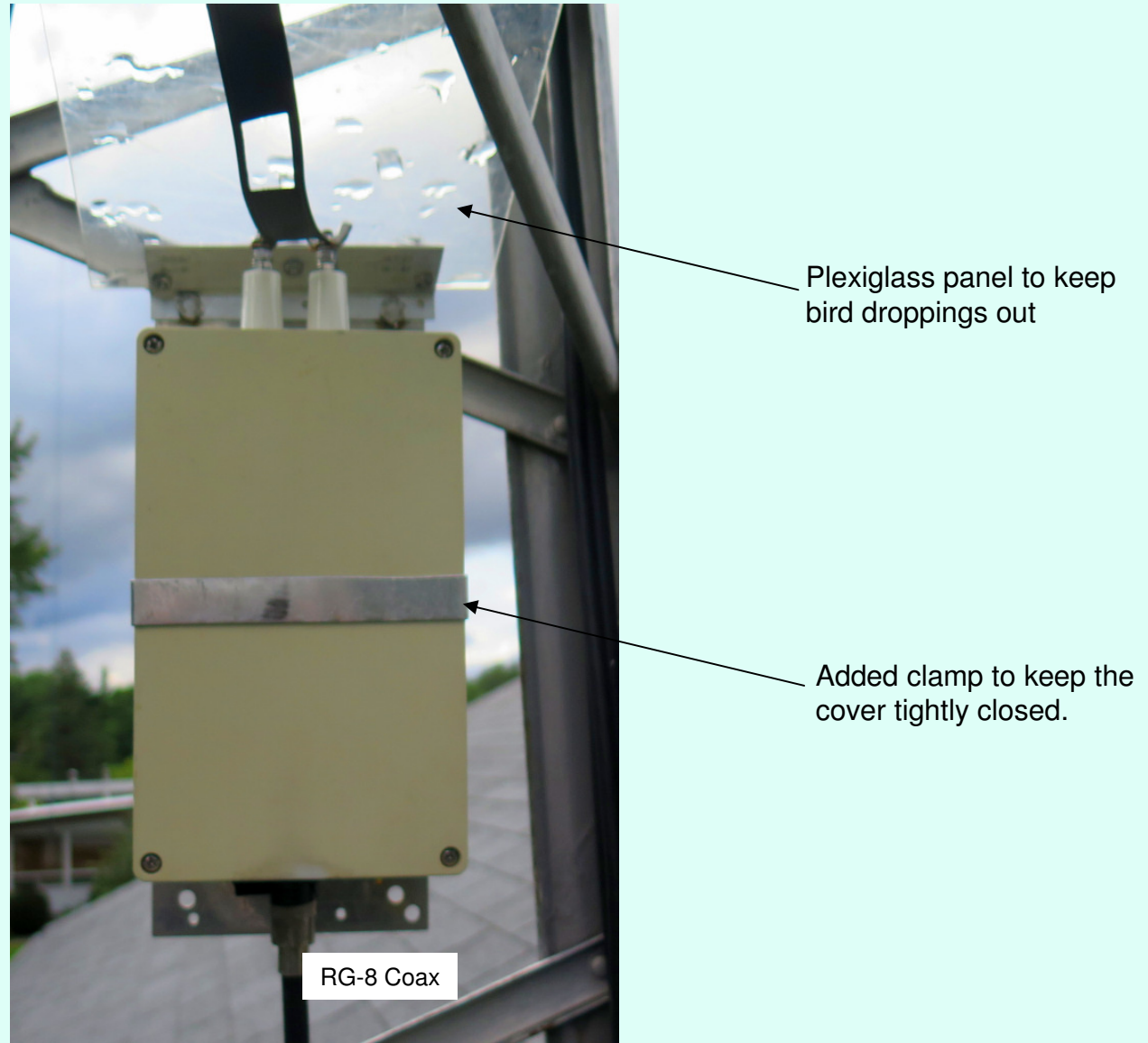



NOTE: INITIAL ANTENNA TESTS:

The Impedance at the end of the ladder line was measured: (33.7 ft @ $V_f = 1$)
The calibration was done using the balun connected to the high voltage insulators.
The calibration plane was at the high voltage insulators.
OSL type calibration was done (Open, Short, Load).

The antenna length was adjusted to “resonate” at 3750 KHz, that is at the point of minimum SWR.
The 15m resonance should produce acceptable SWR. (below 2:1)






NOTE: Reducing the antenna length wire will increase the resonant frequency.
The % frequency increase was less than the decrease in % length.
This is not a problem however.

VSWR MEASUREMENTS

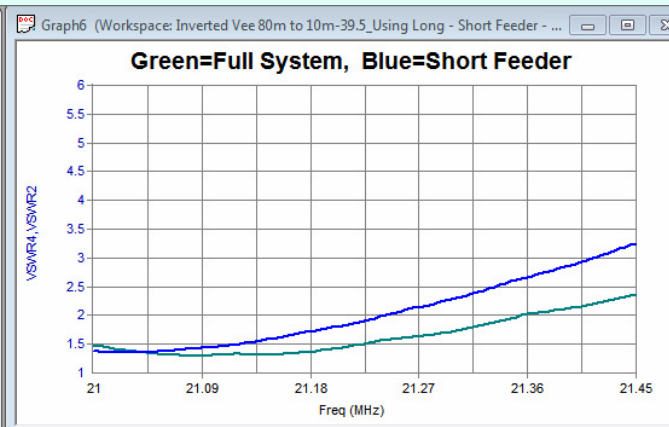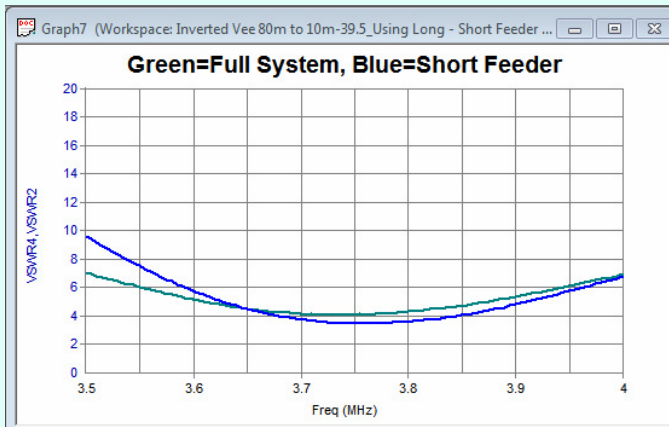

Full System uses the matching circuit and the short feeder

Short Feeder (410Ω)
= 29 pi 8.5 in.

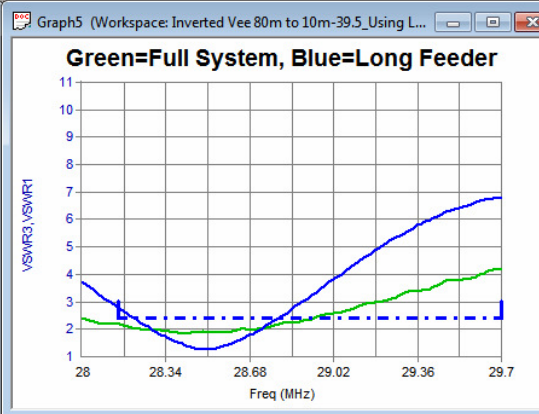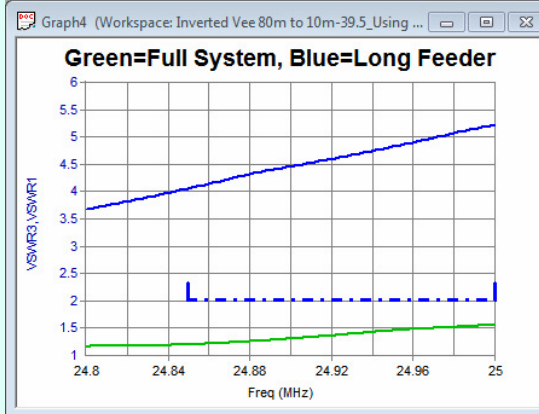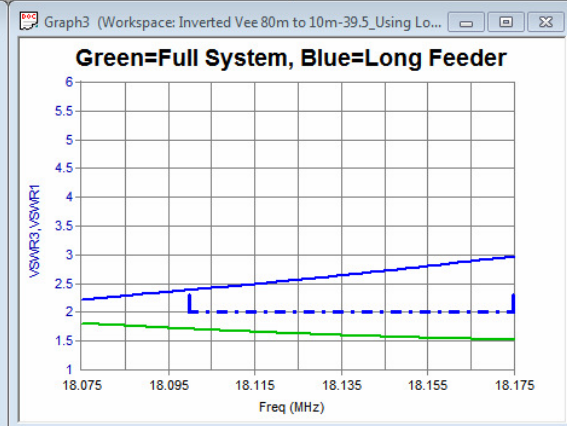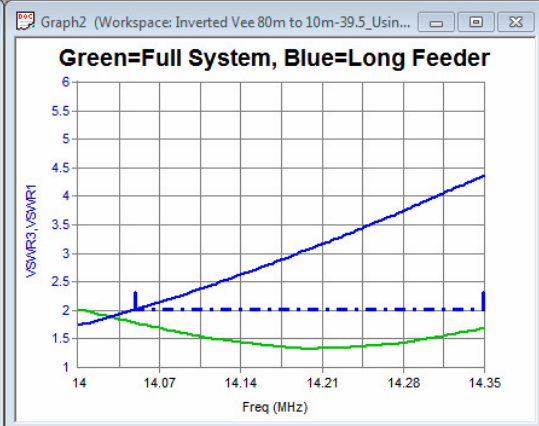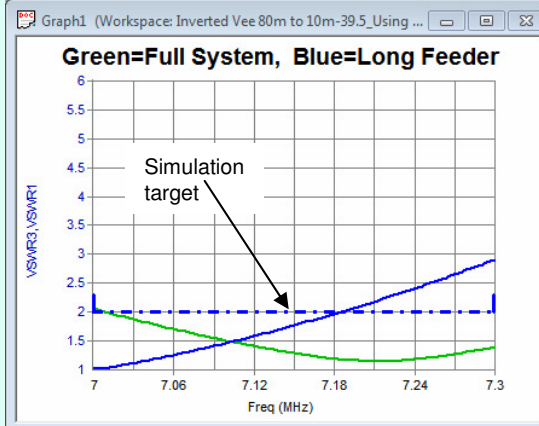

All blue curves use the short or long feeder

Full System uses the matching circuit and the short feeder

Long Feeder (410Ω) = 38.89 ft (38 ft 10.7 in.)
Used on: 10, 12, 17, 20, 40m

ANTENNA MEASUREMENTS & SIMULATIONS

Includes about 50 ft of RG-8 cable

For 40, 20, 17, 12, 10m bands:

Blue= Measured VSWR using additional 410Ω line.









Green= The additional line is replaced by a simulated and optimized L-C-L circuit.

For 80, 15m bands:

Correction done for the 15m band only.

Blue= Measured VSWR without correction.

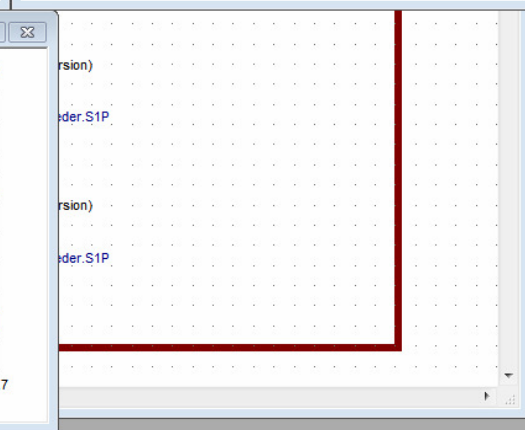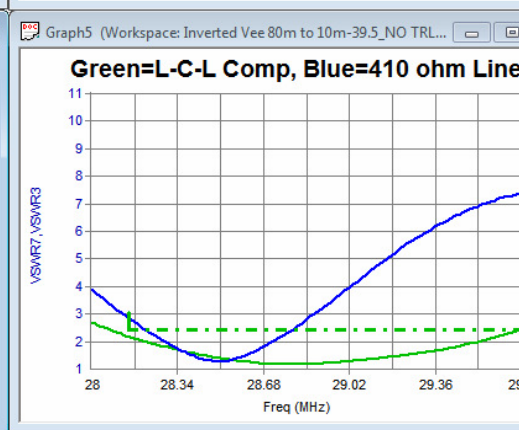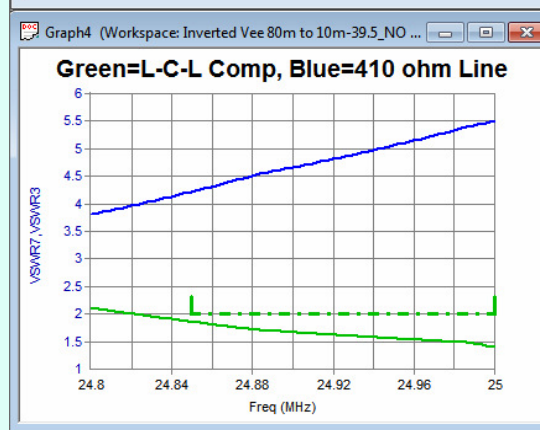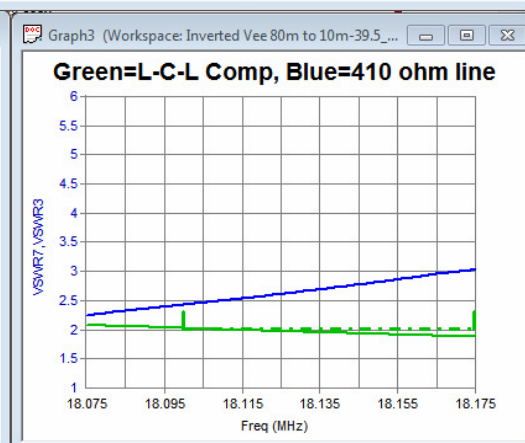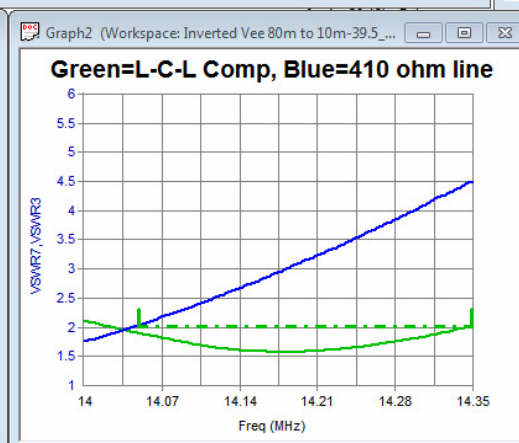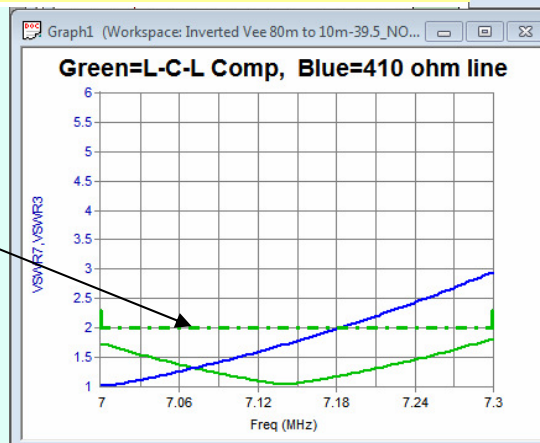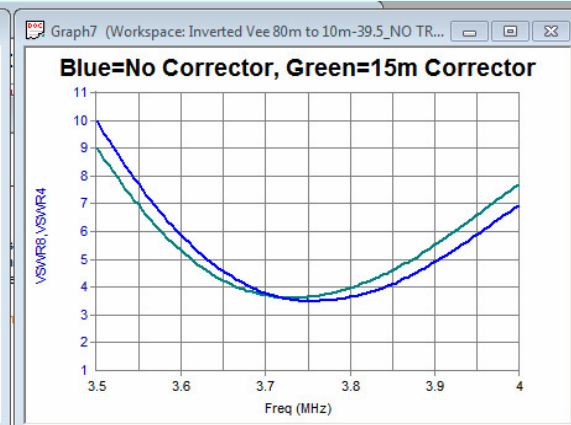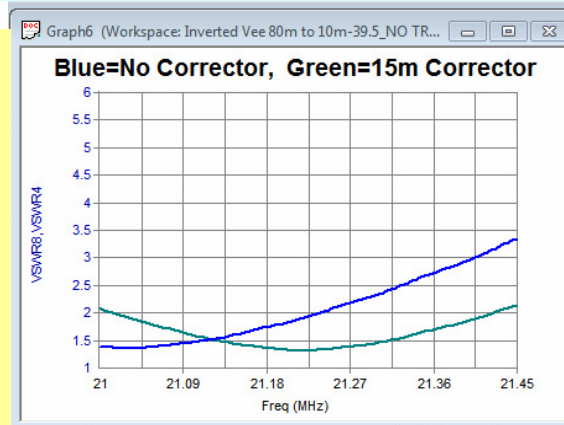Green= Simulated L-C parallel added in series.



Ref: Inverted Vee 80m to 10m-39.5_NO TRL-Revised-TRL-Loss-50ohmFeederAdded-Compare w Mesures.wsp

ANTENNA MEASUREMENTS & SIMULATIONS

The feeder length has been reduced by 4 in.
Includes about 50 ft of RG-8 cable.

For 40, 20, 17, 12, 10m bands:









Green= Measured VSWR using optimized matching circuit. Completed system.

Blue= The additional line is replaced by a simulated and optimized L-C-L circuit.

For 80, 15m bands:


Green= Measured VSWR with L-C parallel circuit for 15m band. Completed system.

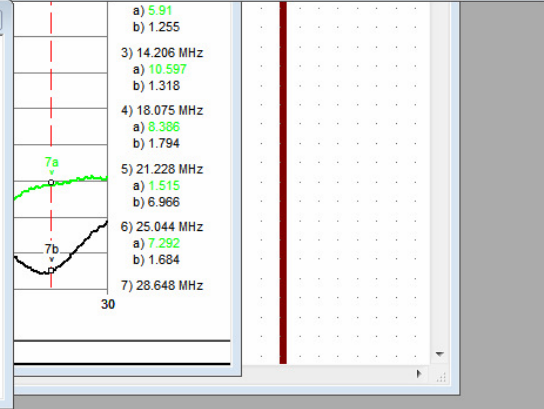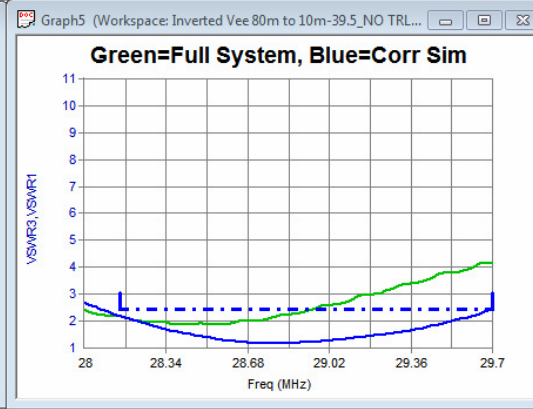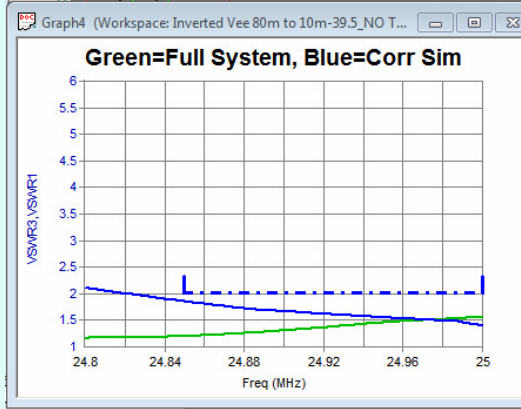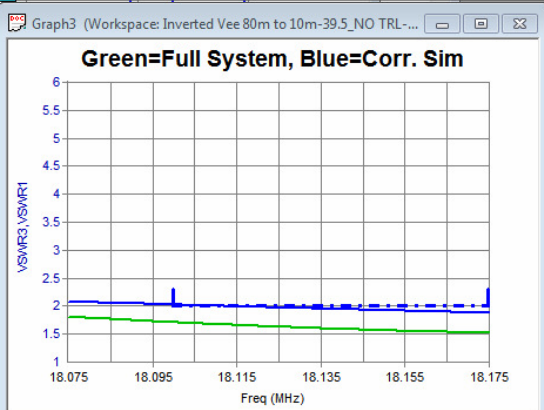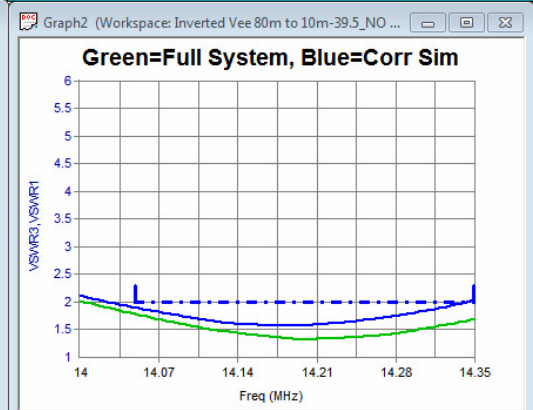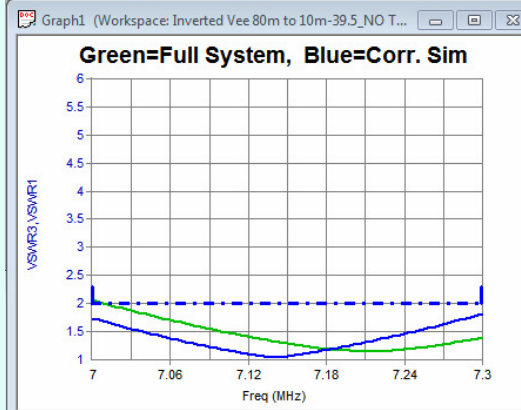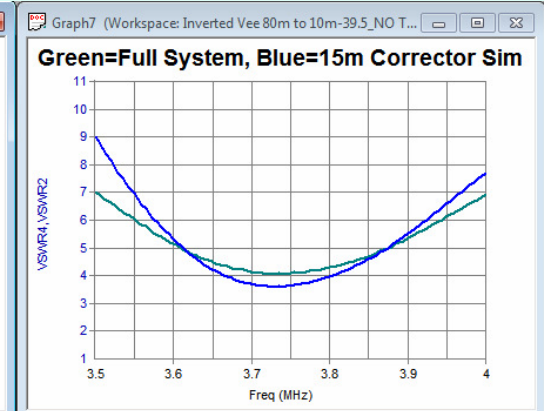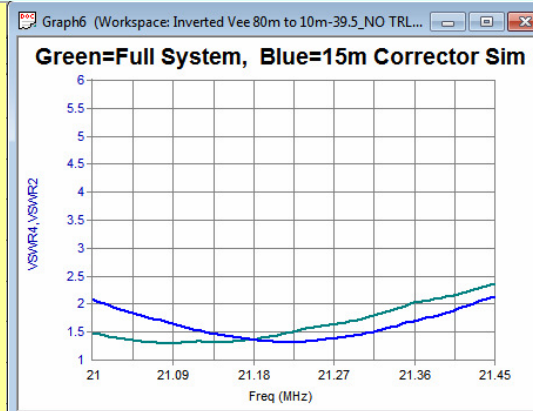Blue= Simulated L-C parallel added in series.



MEASURED VSWR FROM 3.5 TO 30 MHz

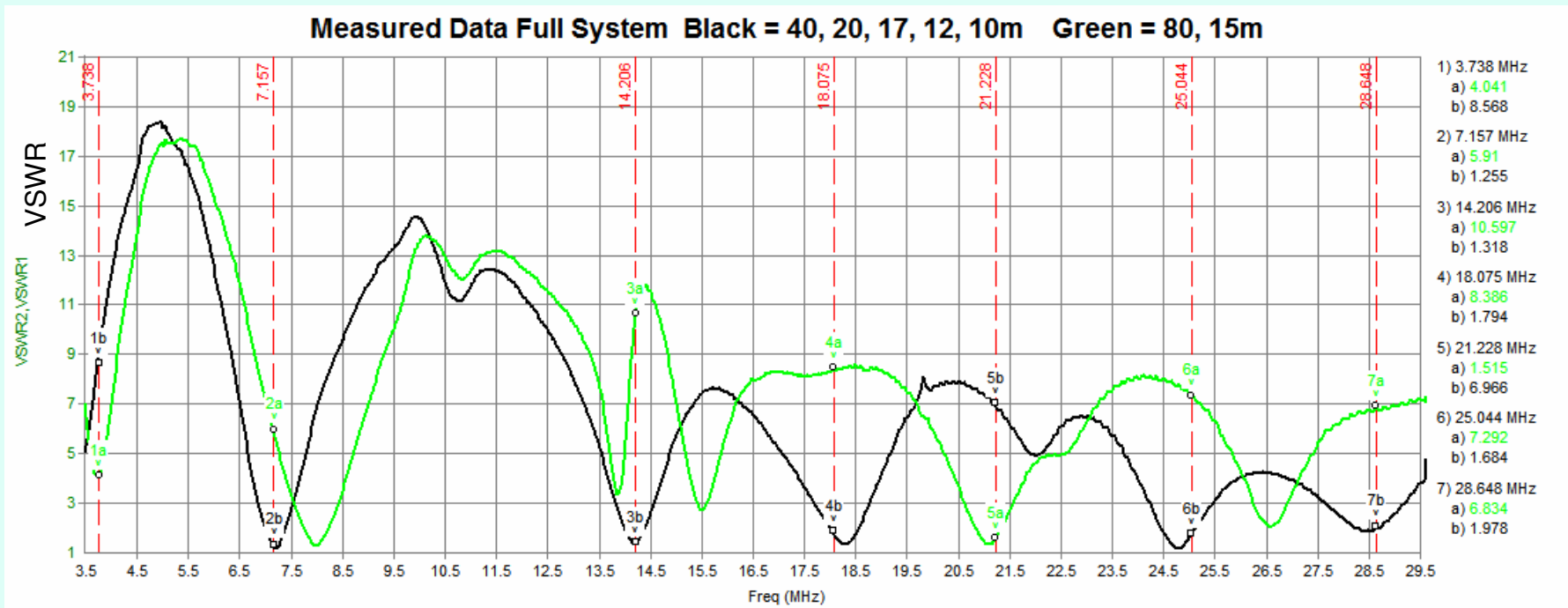Completed system, using the matching circuit as previously described for 40, 20, 17, 12, 10m.




NOTE: Measurements includes about 50 ft of RG-8 cable

The above curves corresponds to the green curves in previous pages.

Ref: Inverted Vee 80m to 10m-39.5_Using Long - Short Feeder - Compare w Mesures-FullSystem-Feeder-4po.wsp

Ladder Line dB Loss on 80m Band

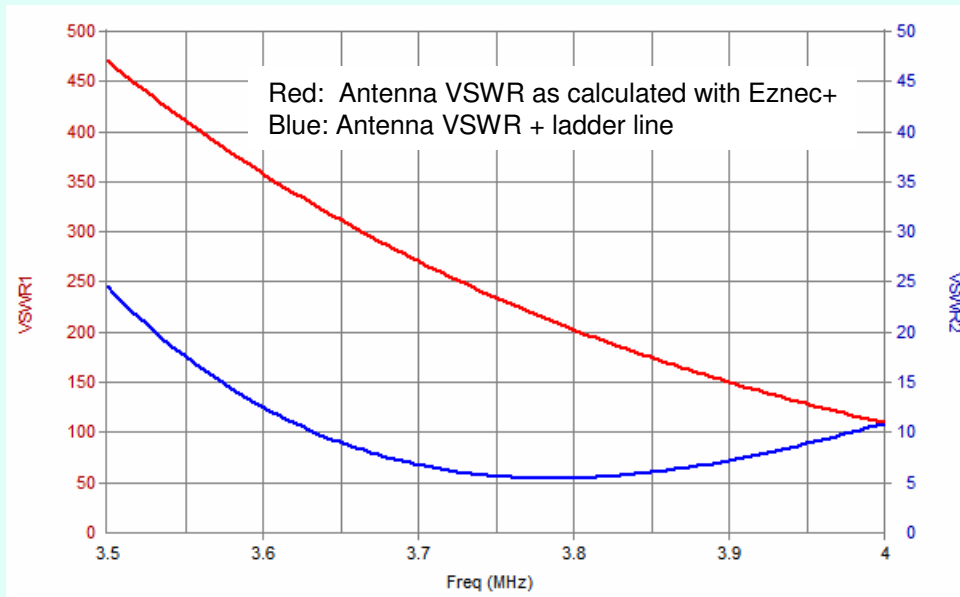Extremely high VSWR at the antenna gives reflection losses in the 410Ω ladder line. (VSWR = 234 @ 3.75 MHz)
The ladder line 'matches' these wild antenna impedances.
At the end of the 'short' ladder line the minimum VSWR is about 5.5.



BLUE:

Ladder line losses as calculated with TLDetails.


Losses include:

- Conductor + Dielectric Losses = 0.08 dB
- Reflection losses vary from 1.3 to 1.76 dB

PINK:

As calculated with EZnec+ V6.0

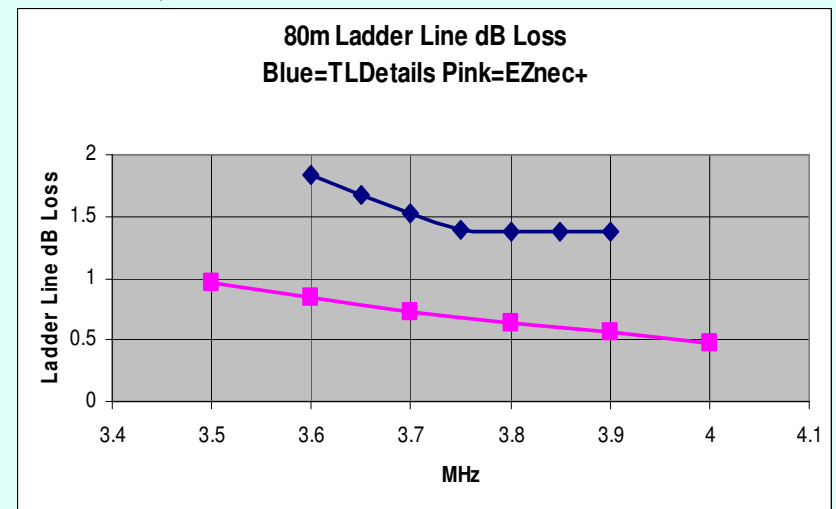
Decreased level in the radiation pattern caused by losses in the ladder line



Ref: TRL Losses -33 ft.xls
Antenna Impedance-NO TRL.wsp


Current on the coax shield vs differential current inside the 50 Ω coax

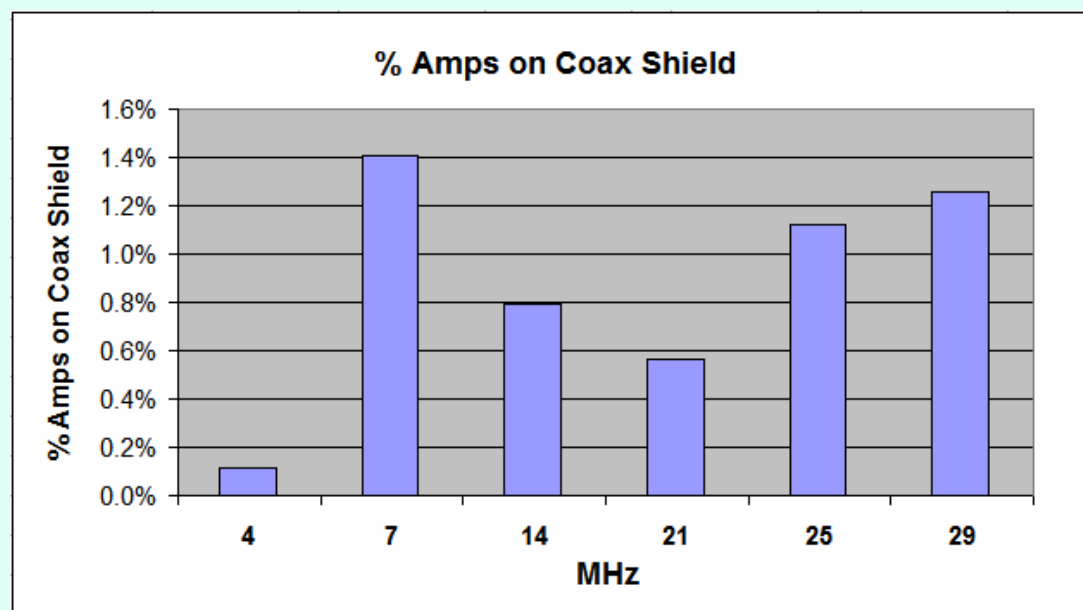This is a well balanced antenna that minimizes the unbalanced currents on the feeder.




Ref: Current probe tests.xls

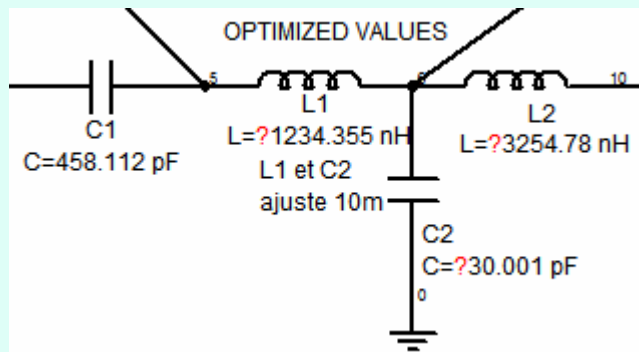USING A SERIES CAP TO BRING 80m IN WHEN THE L – C – L NETWORK IS USED



C1 at input

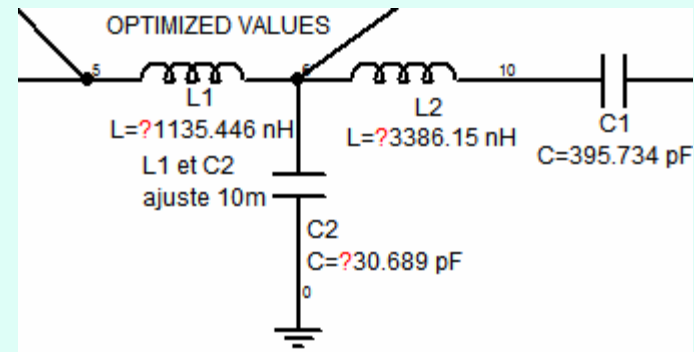

C1 at output

NOTE: In the balanced configuration L1 and L2 values are divided by 2 and the C1 values are multiplied by 2. The balanced configuration was used as shown on the schematic page 8.

SUMMARY of SWR READINGS

As Built No C1	C1 at Input	C1 at output
1) 3.738 MHz a) 3.583 b) 3.583	1) 3.738 MHz a) 3.477	1) 3.738 MHz a) 3.491
2) 7.104 MHz a) 1.155	2) 7.104 MHz a) 1.687	2) 7.104 MHz a) 1.683
3) 14.206 MHz a) 1.577	3) 14.206 MHz a) 1.89	3) 14.206 MHz a) 1.789
4) 18.075 MHz a) 2.065	4) 18.075 MHz a) 2.31	4) 18.075 MHz a) 2.102
5) 21.228 MHz b) 1.309	5) 21.228 MHz b) 1.309	5) 21.228 MHz b) 1.309
6) 25.044 MHz a) 1.15	6) 25.044 MHz a) 1.361	6) 25.044 MHz a) 1.352
7) 28.648 MHz a) 1.204	7) 28.648 MHz a) 1.969	7) 28.648 MHz a) 2.075

NOTE:

- The red SWR readings are done with the L-C-L network.
- The blue SWR readings are done without the L-C-L network.

80m OK now with C1

Slightly worse w/r No C1

Slightly worse w/r No C1

Slightly worse w/r No C1

The L - C - L network is bypassed

Slightly worse w/r No C1

Worse w/r No C1