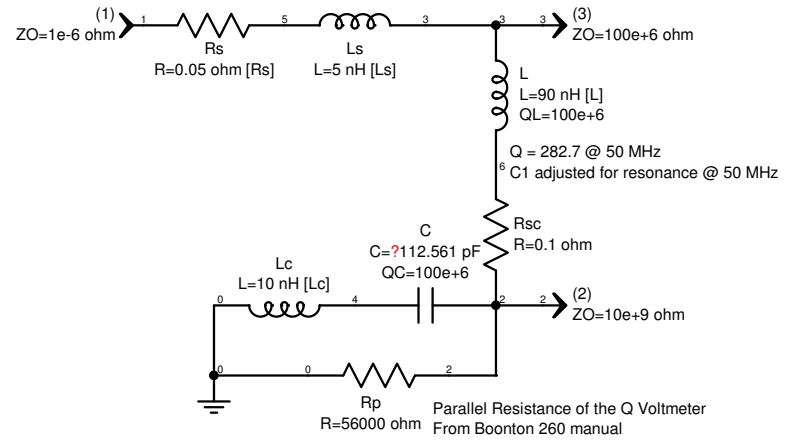


Q Factor Corrections for the source resistance and inductance plus corrections for Lc and Rp of resonating capacitor

Jacques Audet
V1.0 Feb. 2022



$Q_m = Q$ at measured resonant frequency: f (MHz)

$Q_1 = Q$ corrected for L only

$Q_c = Q$ of capacitor C coming from R_p

$R_p =$ Voltmeter resistance (across C)

$f_0 =$ computed resonant frequency of L and C only (MHz)

$L =$ Inductance of inductor under test L (μH)

$C =$ Resonant capacitor (pF)

$L_c =$ Residual inductance of Resonant Capacitor C (μH)

$L_s =$ Source inductance (μH)

$X_c =$ Effective Reactance of C at resonance at frequency: f

$X_L =$ Reactance of L at resonance at frequency: f

$R_s =$ Source resistance (Ω)

$R_{sc} =$ ESR of inductor under test (Ω)

$$X_c = \frac{10^6}{2 \cdot \pi \cdot f \cdot C} - 2 \cdot \pi \cdot f \cdot L_c \quad X_c \text{ is the effective reactance of } C \text{ is in pF at: } f$$

$$Q_c = \frac{R_p}{X_c} \quad Q_c = \text{factor of the capacitor, including } R_p \text{ the parallel resistance of the Q Voltmeter}$$

$$X_{L_s} = 2 \cdot \pi \cdot f \cdot L_s \quad \text{Reactance of source } L_s \text{ in } \mu H \text{ at: } f$$

$$X_c = X_L + X_{L_s} \quad \text{At resonance: } f$$

$$X_L = X_c - X_{L_s} \quad \text{At resonance: } f$$

$$X_L = \frac{10^6}{2 \cdot \pi \cdot f \cdot C} - 2 \cdot \pi \cdot f \cdot L_s \quad \text{At resonance: } f$$

$$L = \frac{X_L}{2 \cdot \pi \cdot f} \quad L \text{ of inductor only } \mu H$$

$$\frac{f}{f_0} = \sqrt{\frac{L}{L + L_s + L_c}} \quad \text{The resonant frequencies are inversely proportional to the square root of the inductances}$$

$$f_0 = \frac{f}{\sqrt{\frac{L}{L + L_s + L_c}}} \quad \text{This is the resonant freq of } L \text{ and } C \text{ only}$$

Calculate the Q of L at fo

$$Q_{m1} = \frac{2 \cdot \pi \cdot f \cdot (L + L_s)}{R_s + R_{sc}} \quad Q_{m1} = Q \text{ of the Inductances without the Capacitor}$$

$$\frac{1}{Q_m} = \frac{1}{Q_{m1}} + \frac{1}{Q_c} \quad \text{Combining the inductor and capacitor Q's}$$

$$Q_{m1} = \frac{1}{\frac{1}{Q_m} - \frac{1}{Q_c}} \quad \text{Solving for } Q_{m1}$$

$$Q_{m1} = \frac{Q_c \cdot Q_m}{Q_c - Q_m} \quad \text{Rearranging}$$

$$R_{sc} = \frac{2 \cdot \pi \cdot f \cdot (L + L_s)}{Q_{m1}} - R_s \quad \text{Solve for } R_{sc}, \text{ the ESR of the inductor, assumed to be constant at } f \text{ and } f_0$$

Substitute the expression for Qm1 above into Rsc

$$R_{sc} = \frac{Q_c \cdot Q_m \cdot R_s - 2 \cdot \pi \cdot L \cdot Q_c \cdot f + 2 \cdot \pi \cdot L \cdot Q_m \cdot f - 2 \cdot \pi \cdot L_s \cdot Q_c \cdot f + 2 \cdot \pi \cdot L_s \cdot Q_m \cdot f}{Q_c \cdot Q_m}$$

$$R_{sc} = \frac{2 \cdot \pi \cdot L \cdot f}{Q_m} - \frac{2 \cdot \pi \cdot L \cdot f}{Q_c} - R_s - \frac{2 \cdot \pi \cdot L_s \cdot f}{Q_c} + \frac{2 \cdot \pi \cdot L_s \cdot f}{Q_m} \quad \text{Rearranging}$$

$$R_{sc} = \frac{2 \cdot \pi \cdot f \cdot (L + L_s)}{Q_m} - \frac{2 \cdot \pi \cdot f \cdot (L + L_s)}{Q_c} - R_s \quad \text{Rearranging}$$

$$R_{sc} = 2 \cdot \pi \cdot f \cdot (L + L_s) \cdot \left(\frac{1}{Q_m} - \frac{1}{Q_c} \right) - R_s \quad \text{Rearranging}$$

$$Q_1 = \frac{2 \cdot \pi \cdot f_0 \cdot L}{R_{sc}} \quad \text{The corrected Q of inductor} = Q_1 \text{ at } f_0$$

Example 1 Lc set to 10 nH The corrected Q = Q1 is Correct

$$Q_m := 168.87 \quad R_s := 0.05 \quad L_s := 0.005 \quad \mu\text{H} \quad f := 46.294 \quad \text{MHz} \quad C := 112.561 \quad \text{pF}$$

$$R_p := 56000 \quad L_c := 0.010 \quad \text{nH}$$

$$X_c := \frac{10^6}{2 \cdot \pi \cdot f \cdot C} - 2 \cdot \pi \cdot f \cdot L_c = 27.634 \quad \text{Effective } X_c$$

$$Q_c := \frac{R_p}{X_c} = 2.026 \times 10^3 \quad \text{Q of resonant capacitor C coming from } R_p$$

$$X_L := X_c - 2 \cdot \pi \cdot f \cdot L_s = 26.18 \quad \text{Reactance of coil under test}$$

$$L := \frac{X_L}{2 \cdot \pi \cdot f} = 0.09 \quad \text{Inductance of coil under test}$$

$$f_0 := \frac{f}{\sqrt{\frac{L}{L + L_s + L_c}}} = 50.003 \quad \text{This is the resonant freq } f_0 \text{ of L and C only}$$

ESR of inductor under test (Ω)


$$R_{sc} := 2 \cdot \pi \cdot f \cdot (L + L_s) \cdot \left(\frac{1}{Q_m} - \frac{1}{Q_c} \right) - R_s = 0.100004$$

Q @ fo of inductor only, after corrections

$$Q_1 := \frac{2 \cdot \pi \cdot f_0 \cdot L}{R_{sc}} = 282.76$$

Simulations (see top of first page)

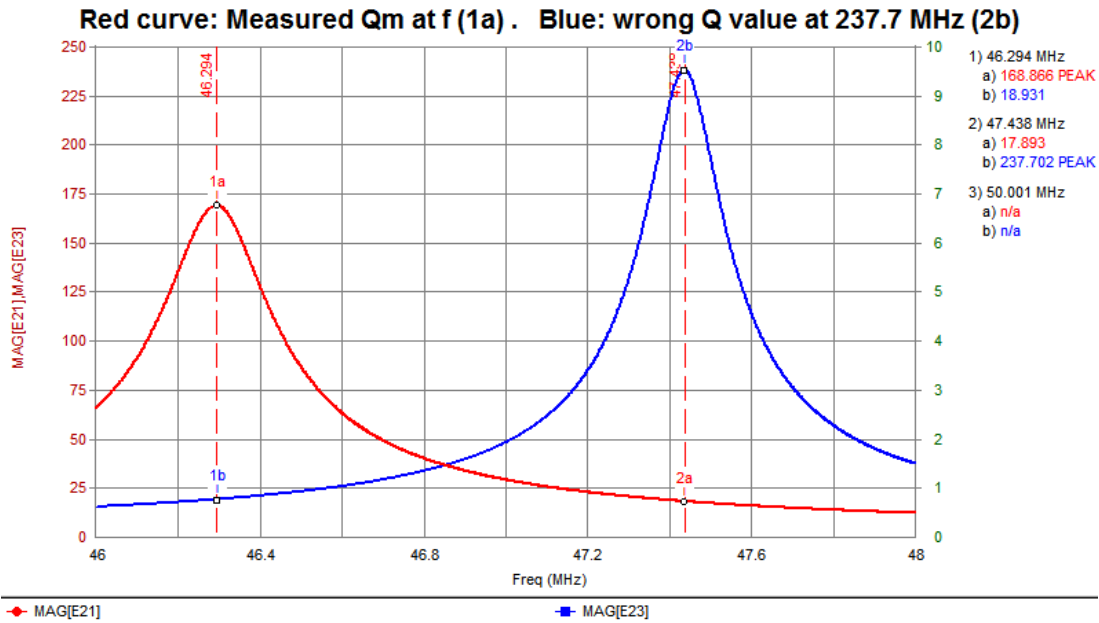MAG[E21] is the voltage (ratio) obtained on a standard Q measurement
 MAG[E23] is the voltage ratio: V across Cap / V at source output.



Example 2 Lc set to 0 The corrected Q = Q1 is Correct

$\underline{Qm} := 176$ $\underline{Rs} := 0.05$ $\underline{Ls} := 0.005 \text{ } \mu\text{H}$ $\underline{f} := 48.669 \text{ MHz}$ $\underline{C} := 112.561$
 $\underline{Rp} := 56000$ $\underline{Lc} := 0.000$

$$\underline{Xc} := \frac{10^6}{2 \cdot \pi \cdot f \cdot C} - 2 \cdot \pi \cdot f \cdot Lc = 29.052 \quad \text{Effective } Xc$$

$$\underline{Qc} := \frac{Rp}{Xc} = 1.928 \times 10^3 \quad \text{Q of resonant capacitor C coming from Rp}$$

$$\underline{XL} := Xc - 2 \cdot \pi \cdot f \cdot Ls = 27.523 \quad \text{Reactance of coil under test}$$

$$\underline{L} := \frac{XL}{2 \cdot \pi \cdot f} = 0.09001 \quad \text{Inductance of coil under test}$$

$$\underline{fo} := \frac{f}{\sqrt{\frac{L}{L + Ls + Lc}}} = 50.003 \quad \text{This is the resonant freq fo of L and C only}$$


ESR of inductor under test (Ω)

$$\underline{Rsc} := 2 \cdot \pi \cdot f \cdot (L + Ls) \cdot \left(\frac{1}{Qm} - \frac{1}{Qc} \right) - Rs = 0.099998$$

Q @ fo of inductor only, after corrections

$$\underline{Q1} := \frac{2 \cdot \pi \cdot fo \cdot L}{Rsc} = 282.781$$

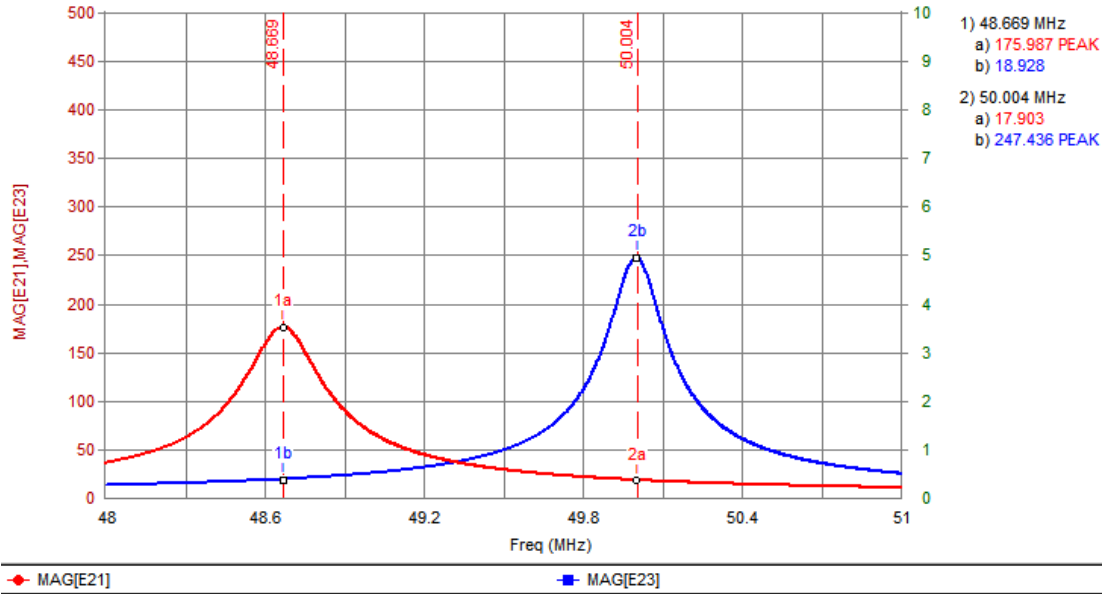Red curve: Measured Qm at f (1a) . Blue: wrong Q=247.4 @ 50 MHz (2b)



Example 3 Lc and Ls set to 0 The corrected Q = Q1 is correct

$\underline{Q_m} := 172.126$ $\underline{R_s} := 0.05$ $\underline{L_s} := 0.000$ μH $\underline{f} := 50$ MHz $\underline{C} := 112.561$
 $\underline{R_p} := 56000$ $\underline{L_c} := 0.000$

$\underline{X_c} := \frac{10^6}{2 \cdot \pi \cdot f \cdot C} - 2 \cdot \pi \cdot f \cdot L_c = 28.279$ Effective Xc

$\underline{Q_c} := \frac{R_p}{X_c} = 1.98 \times 10^3$ Q of resonant capacitor C coming from Rp

$\underline{X_L} := X_c - 2 \cdot \pi \cdot f \cdot L_s = 28.279$ Reactance of coil under test

$\underline{L} := \frac{X_L}{2 \cdot \pi \cdot f} = 0.09001$ Inductance of coil under test


$\underline{f_o} := \frac{f}{\sqrt{\frac{L}{L + L_s + L_c}}} = 50$ This is the resonant freq fo of L and C only

ESR of inductor under test (Ω)

$\underline{R_{sc}} := 2 \cdot \pi \cdot f \cdot (L + L_s) \cdot \left(\frac{1}{Q_m} - \frac{1}{Q_c} \right) - R_s = 0.100011$

Q @ fo of inductor only, after corrections

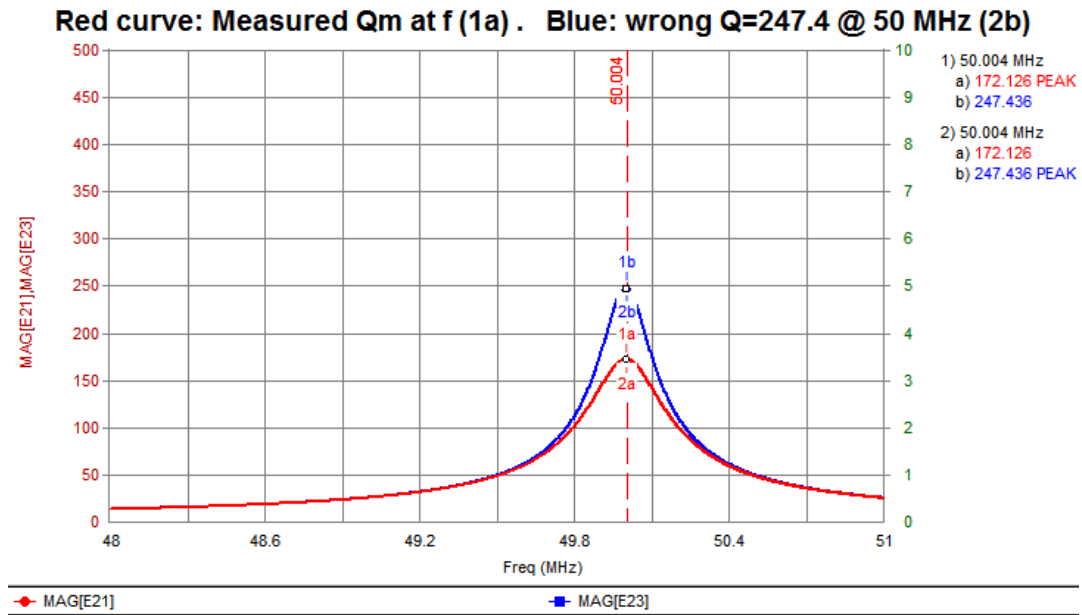$\underline{Q_1} := \frac{2 \cdot \pi \cdot f_o \cdot L}{R_{sc}} = 282.756$



Example 4 Lc and Ls set to 0 The corrected Q = Q1 is correct

$\underline{\underline{O_m}} := 188.51$ $\underline{\underline{R_s}} := 0.05$ $\underline{\underline{L_s}} := 0.000 \text{ } \mu\text{H}$ $\underline{\underline{f}} := 50 \text{ MHz}$ $\underline{\underline{C}} := 112.561$
 $\underline{\underline{R_p}} := 10^{10}$ $\underline{\underline{L_c}} := 0.000$

$\underline{\underline{X_c}} := \frac{10^6}{2 \cdot \pi \cdot f \cdot C} - 2 \cdot \pi \cdot f \cdot L_c = 28.279$ Effective Xc

$\underline{\underline{Q_c}} := \frac{R_p}{X_c} = 3.536 \times 10^8$ Q of resonant capacitor C coming from Rp

$\underline{\underline{X_L}} := X_c - 2 \cdot \pi \cdot f \cdot L_s = 28.279$ Reactance of coil under test

$\underline{\underline{L}} := \frac{X_L}{2 \cdot \pi \cdot f} = 0.09001$ Inductance of coil under test

$\underline{\underline{f_0}} := \frac{f}{\sqrt{\frac{L}{L + L_s + L_c}}} = 50$ This is the resonant freq fo of L and C only

ESR of inductor under test (Ω)

$\underline{\underline{R_{sc}}} := 2 \cdot \pi \cdot f \cdot (L + L_s) \cdot \left(\frac{1}{Q_m} - \frac{1}{Q_c} \right) - R_s = 0.100013$

Q @ fo of inductor only, after corrections


$\underline{\underline{Q_1}} := \frac{2 \cdot \pi \cdot f_0 \cdot L}{R_{sc}} = 282.753$

Conclusion

Computing $\text{Mag}[E23]$ the voltage ratio: V across Cap / V at source output ONLY gives the right results when R_p is very high (negligible).

The Mathcad corrections provide the right Q factor of the coil under test under ALL conditions.

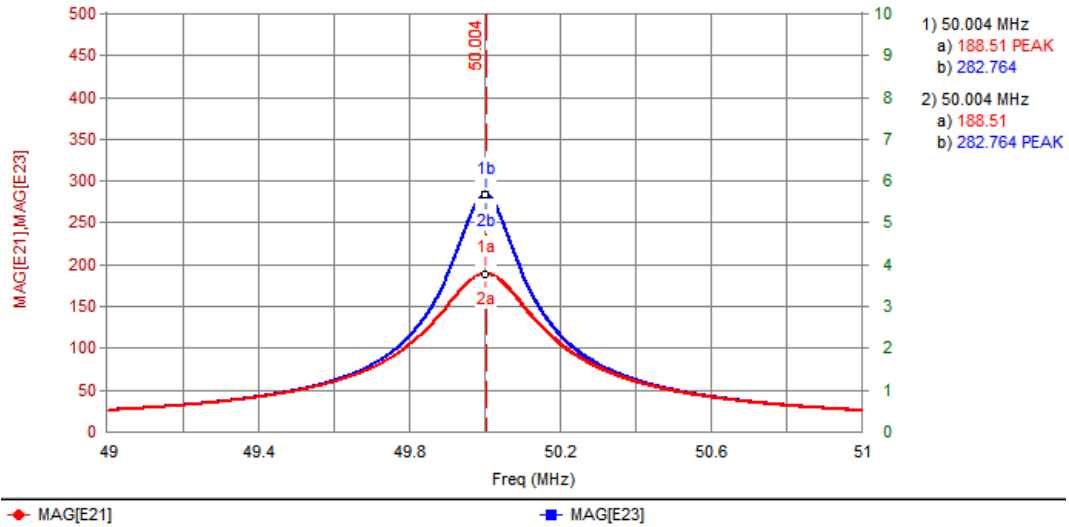Red curve: Measured Qm at f (1a) . Blue: correct Q=282.7 @ 50 MHz (2b)



Calculation of R_p (Mohms) vs frequency f (MHz)

$$R_p(f) := 10^{(2574.584367 + 6.708083 \cdot f^{-0.15} + 26.44179 \cdot \ln(f) - 2580.071643 \cdot f^{0.01})}$$

Ref : Boonton260_Rp Curve.xls.xmcd

Ref. Q Meter Source Sim.wsp