

J. Audet VE2AZX Web: ve2azx.net

**RETURN LOSS BRIDGE SCHEMATIC** 

INPUT PORT

Models 1, 2, 3

This bridge design does not use a transformer with magnetic coupling. Instead it uses a current balun to pickup the bridge voltage. That makes it inherently very wideband. The balun impedance must be kept high over the frequency range of the bridge, since this impedance effectively appears in parallel with the unknown. A compensating impedance is used across the internal bridge reference termination to maintain balance at the frequency extremes of the bridge. This design is used in many commercial bridges.


With the beads placed close to the PCB, you need to measure the bridge directivity while you move the beads away from the PCB.


First on one side, then you try the other side.

One bead at a time, then two or three, until you find a spot that gives the highest directivity between 300 and 2000 MHz.


It's best to use a network analyzer setup so that you can observe the frequency response in real time.

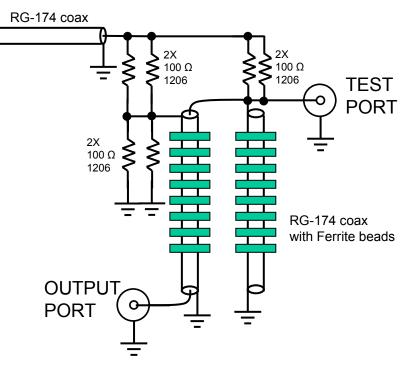To attach the bead, use anything that is non metallic, such as tie wraps, cords, glue. The RG174 cable lengths should be about the same, the exact length is not critical. Just use the length that is required as I did.



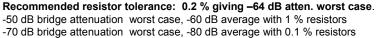




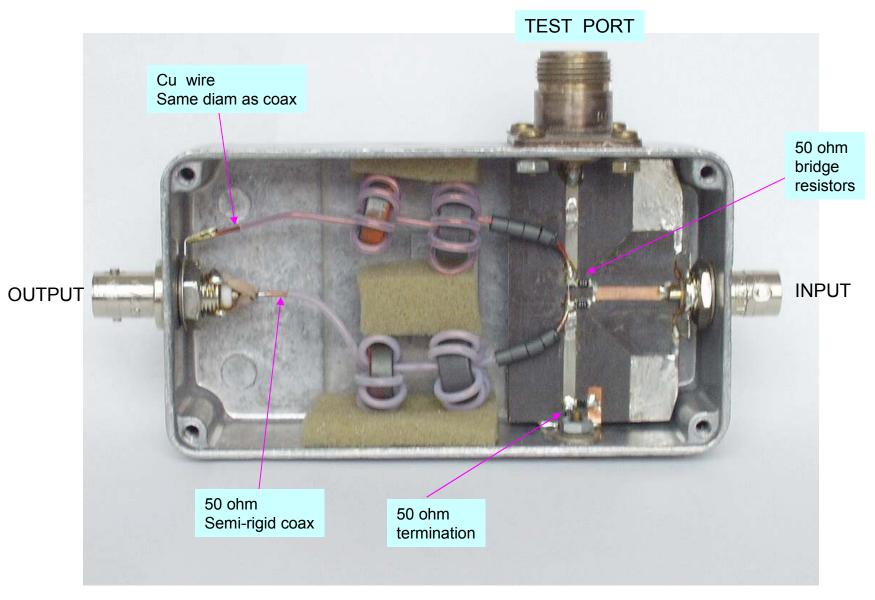


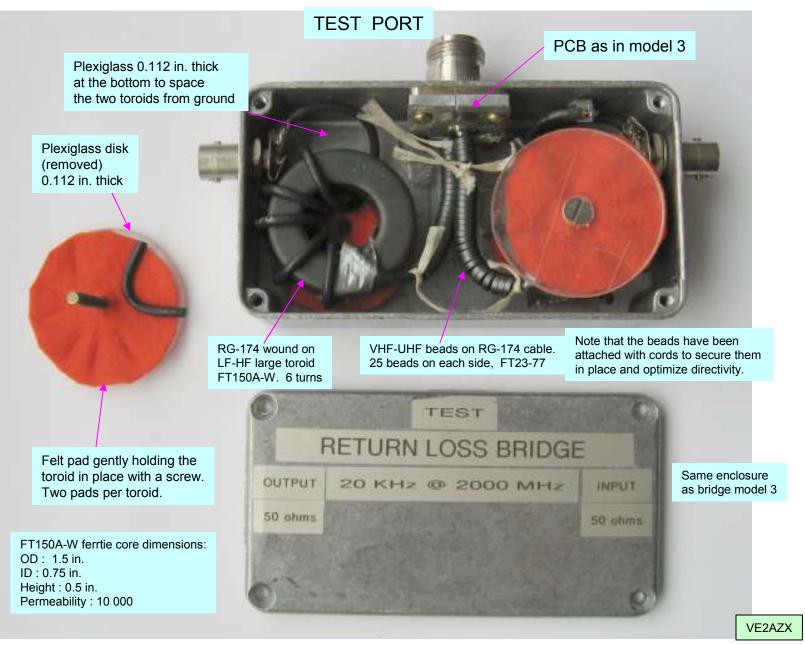RETURN LOSS BRIDGE MODEL 1 100KHz – 1000 MHz






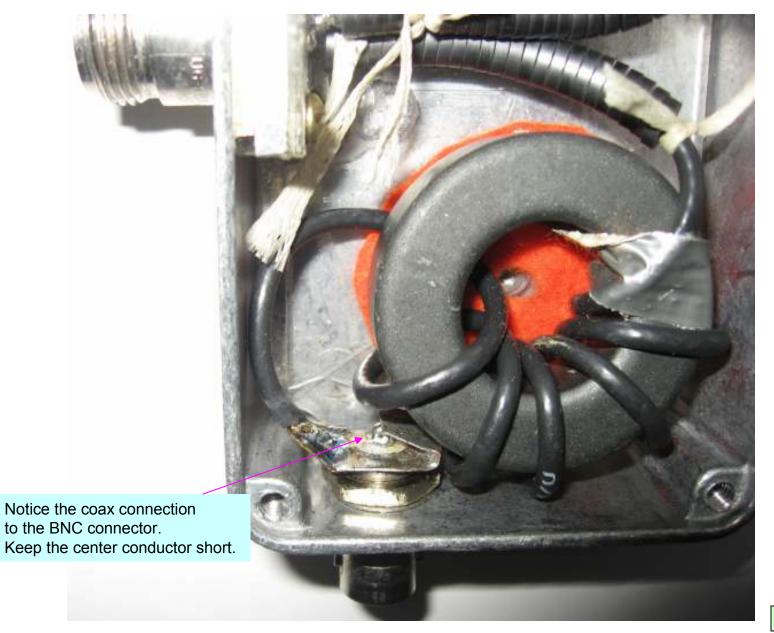RETURN LOSS BRIDGE MODEL 2 20KHz – 2000 MHz




VE2AZX

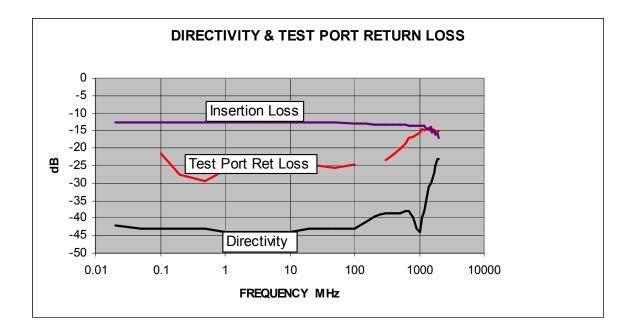RETURN LOSS BRIDGE MODEL 2 20KHz – 2000 MHz



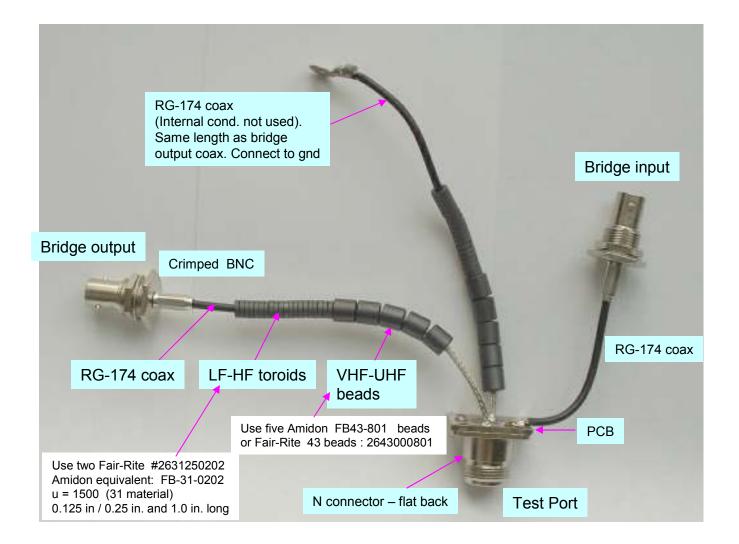
# **RETURN LOSS BRIDGE MODEL 2** performance tests




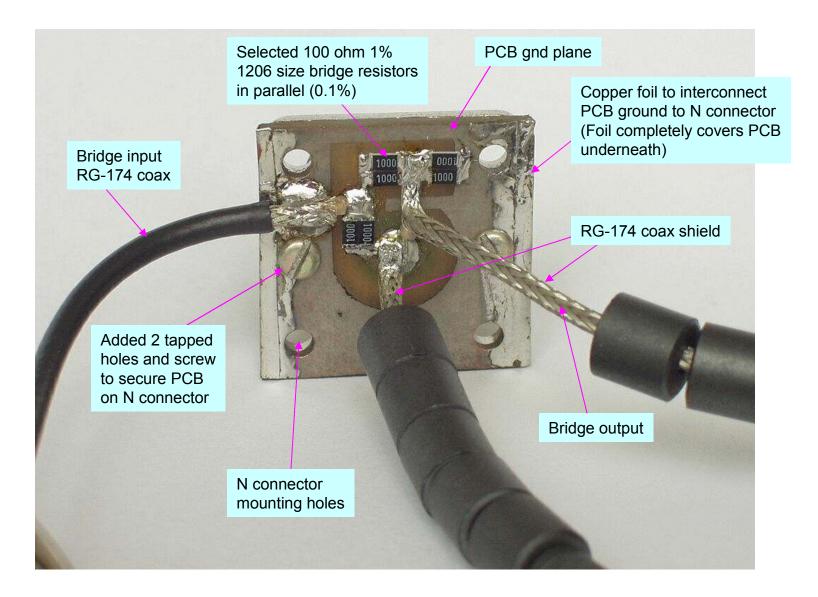RETURN LOSS BRIDGE MODEL 3 1 MHz to 2500 MHz






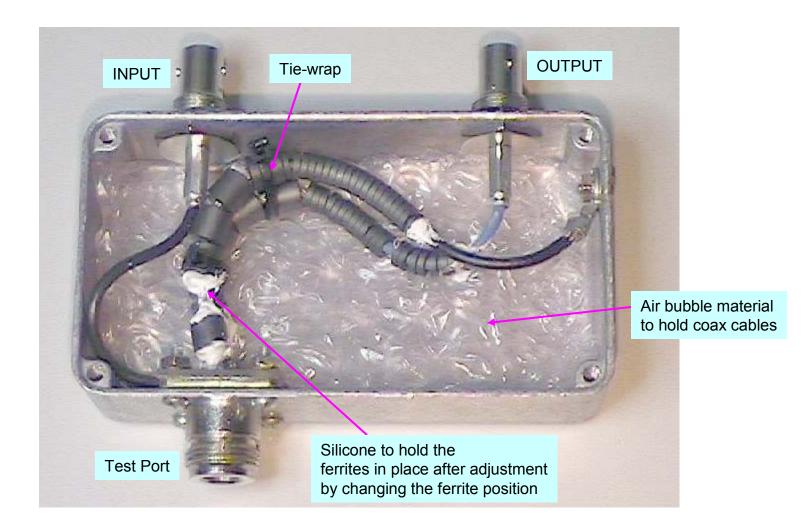**RETURN LOSS BRIDGE MODEL 3** N Connector with PCB




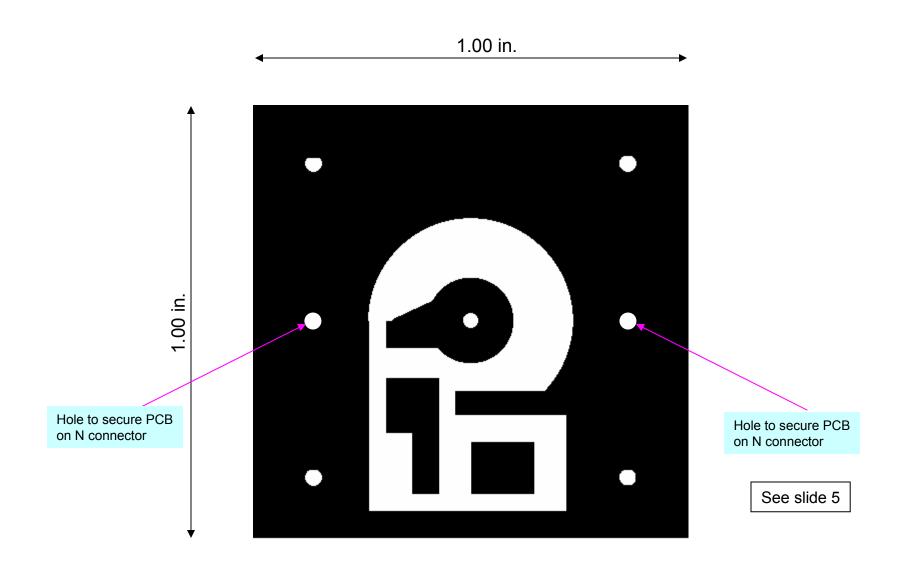
RETURN LOSS BRIDGE MODEL 3 bridge mounted in its enclosure







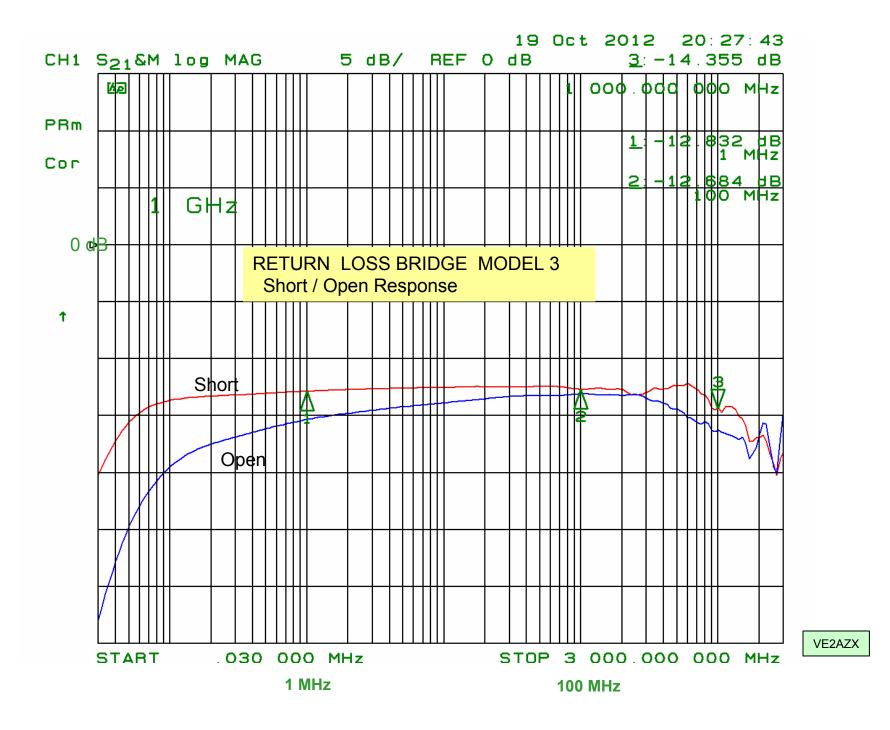
PCB for return loss bridge models 2 and 3



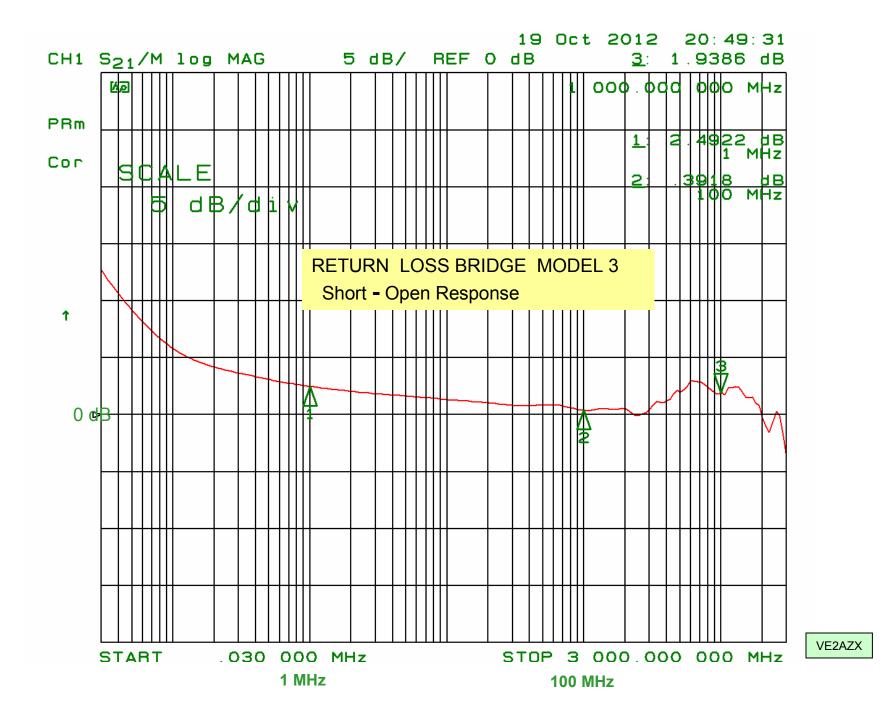

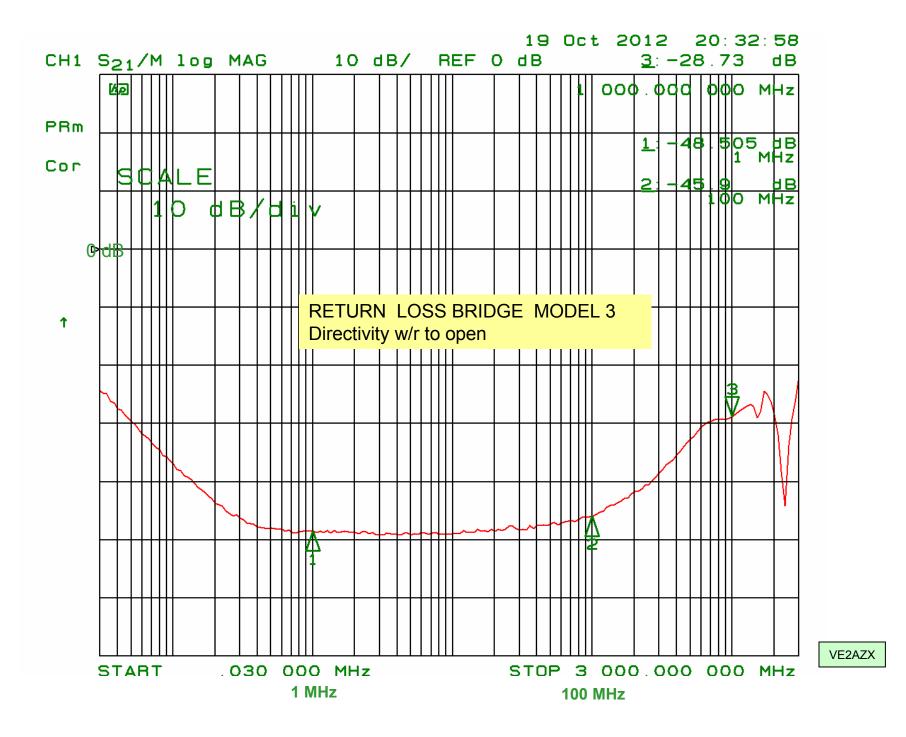

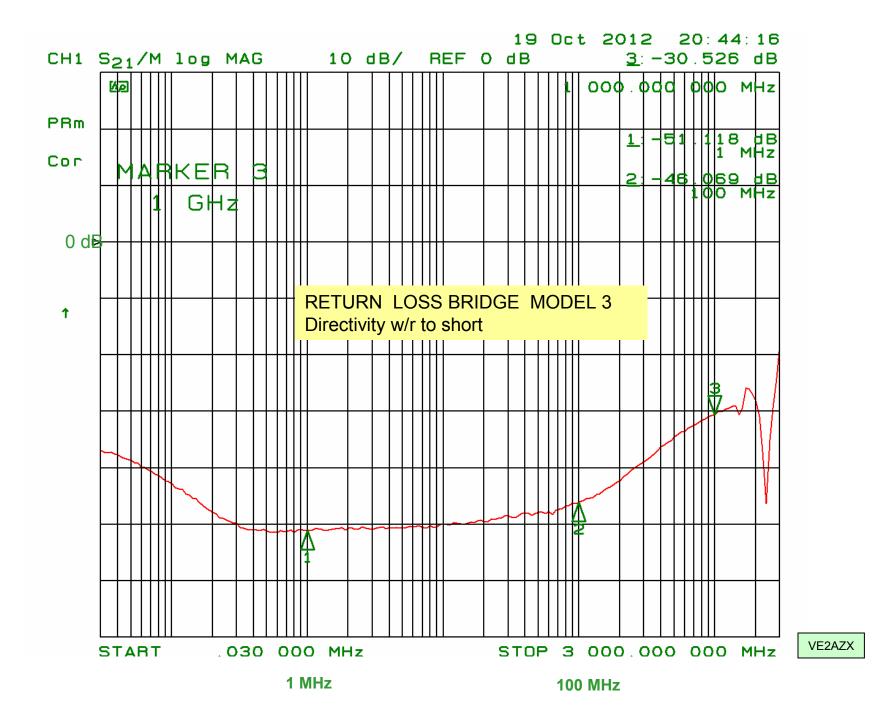

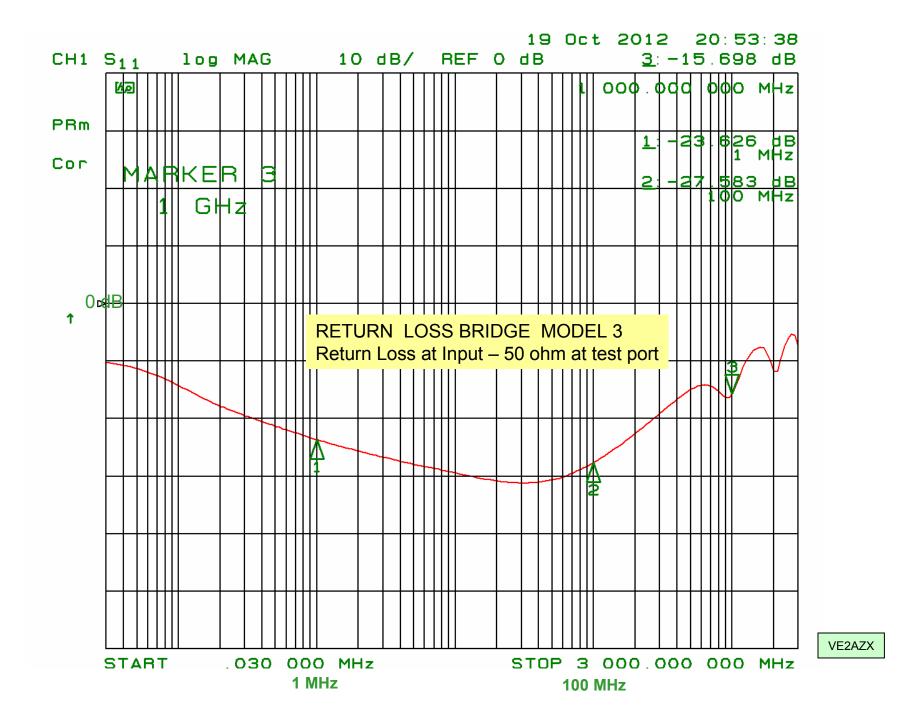

## **RETURN LOSS BRIDGE MODEL 3**

## Stocklist

## QTY

- Amidon FB43-801 Ferrite beads (u=850) or Fair-Rite 43 SHIELD BEAD: 2643000801 u = 800 (43 material)
   0.094 in / 0.296 in. and 0.297 in. Long Use 5 per side.
- Use Fair-Rite 31 SHIELD BEAD: 2631250202
  Amidon equivalent: FB-31-0202
  u = 1500 (31 material)
  0.125 in / 0.25 in. and 1.0 in. long
  Use two per side.
- 2 BNC Bulkhead Jacks, RG174 Digikey # A1813-ND
- 1 N type connector with flat back
- 1 Al Case Hammond Manufacturing # 1590B
- 6 Selected 100 ohm +/- 0.1 ohm 1206 SMT resistors
- 1 PCB
- 18 in. RG174 miniature coax.


Note that high freq performance critically depends on:

- 1- Using a small PCB, located behind the N test connector.
- 2- Using RG174 bulkhead BNC connectors.
- 3- Adjusting the location of the ferrite beads for best balance, preferably by looking at the S21 curve from 500 to 3000 MHz.
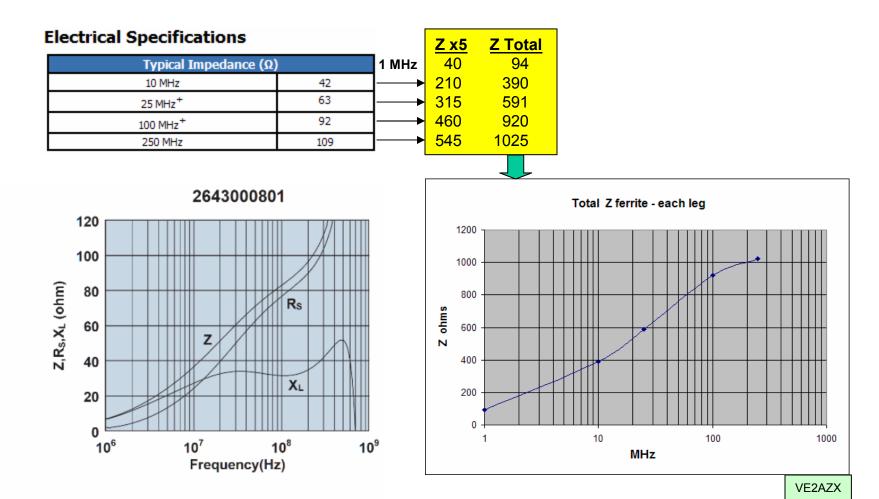
### Fair-Rite 43 SHIELD BEAD: 2643000801

u = 800 (43 material) 0.094 in / 0.296 in. and 0.297 in. long Very close to Amidon FB43-801 Use five per side http://www.fair-rite.com/cgibin/catalog.pgm

Fair-Rite authorized distributors: http://www.fair-rite.com/newfair/support.htm



Impedance, reactance, and resistance vs. frequency.

### Fair-Rite 31 SHIELD BEAD: 2631250202


http://www.fair-rite.com/cgibin/catalog.pgm

u = 1500 (31 material) 0.125 in / 0.25 in. and 1.0 in. long Use two per side

### **Electrical Specifications**

Typical Impedance (Ω)		<mark>Z x2</mark>
1 MHz	27	54
5 MHz	70	140
10 MHz <sup>+</sup>	90	180
25 MHz <sup>+</sup>	138	276
100 MHz <sup>+</sup>	230	460
250 MHz	240	480

2631250202

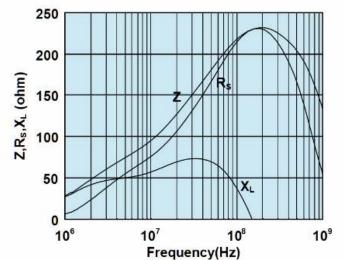

Impedance, reactance, and resistance vs. frequency.



