

Get the Most from your Antenna Analyzer

**Jacques Audet VE2AZX
September 2019 Rev. April 2023
Web: ve2azx.net**

Agenda

Review of Impedance concepts

Scalar and Vector Analyzer – Descriptions


What you can do with a scalar analyzer

What you can do with a vector analyzer

Some applications

Verify your analyzer

Impedance = Resistance and Reactance

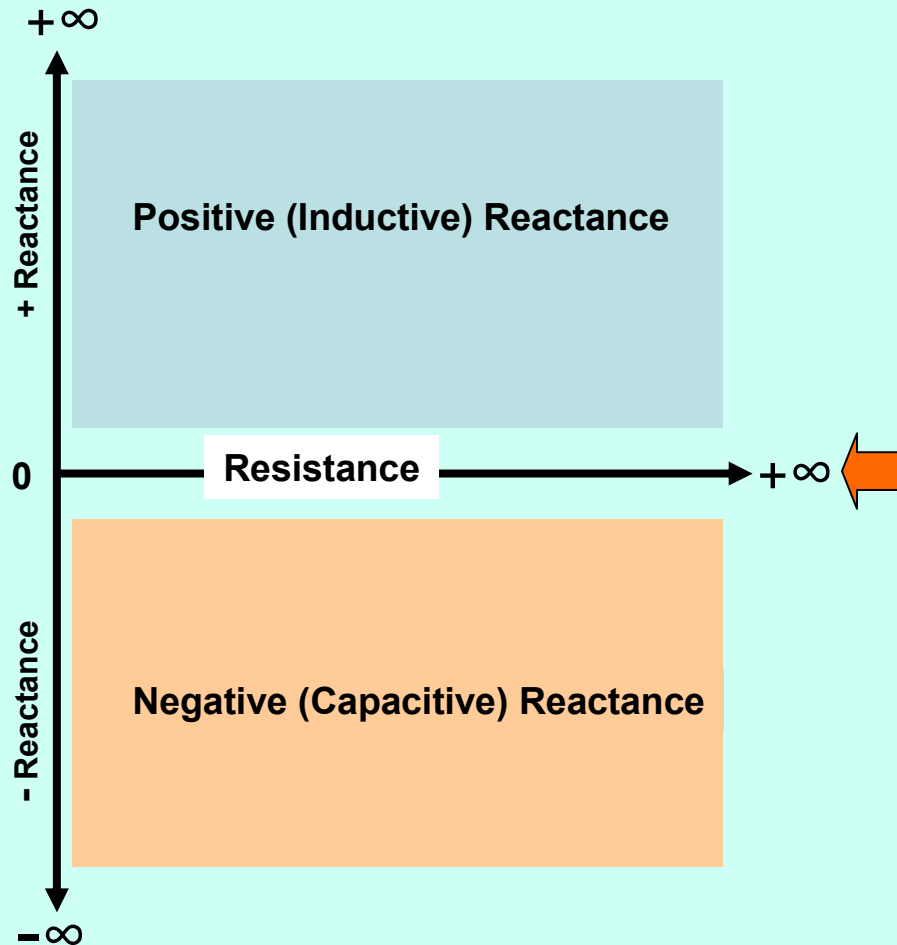


Resistance and reactance are independent
They combine at right angle like triangles

You can only dissipate power
in the resistance part

Reactances of opposite sign will subtract
This property is used in tuners, filters,
resonators...

Resistance R, Reactance X and Impedance Magnitude |Z|

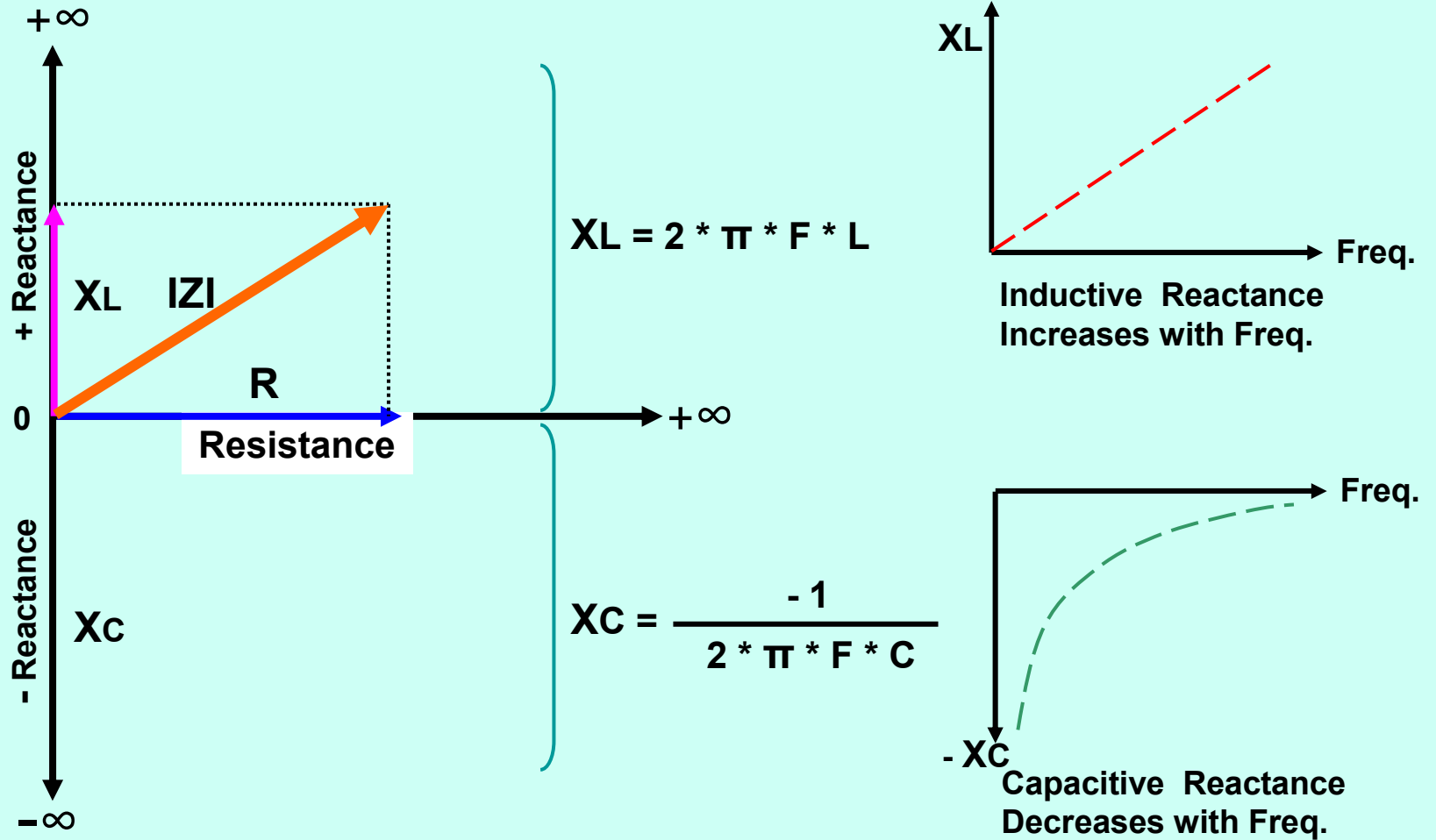

Impedance Z, Reflection Coefficient and SWR

Impedance = resistive (R)
and reactive part (X)

$$Z = R + j \cdot X$$

$$|Z| = \sqrt{R^2 + X^2}$$

Impedance magnitude

$$\Gamma = \frac{Z - Z_0}{Z + Z_0}$$

Reflection coefficient Γ (magnitude + angle). Z_0 is the reference Z
 Γ goes from $-1.0 > 0 > +1.0$

$$RL = -20 \cdot \log(|\Gamma|)$$


RL = Return Loss in dB $|\Gamma|$ = magnitude of the reflection coefficient

$$SWR = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

SWR (also called voltage standing wave ratio)
Goes from 1 to ∞


	SWR	Reflection Coeff.	Return Loss (dB)
$Z = Z_0$	1:1	0	∞
$Z = 0$	∞	-1	0
$Z = \infty$	∞	+1	0

The Smith Chart

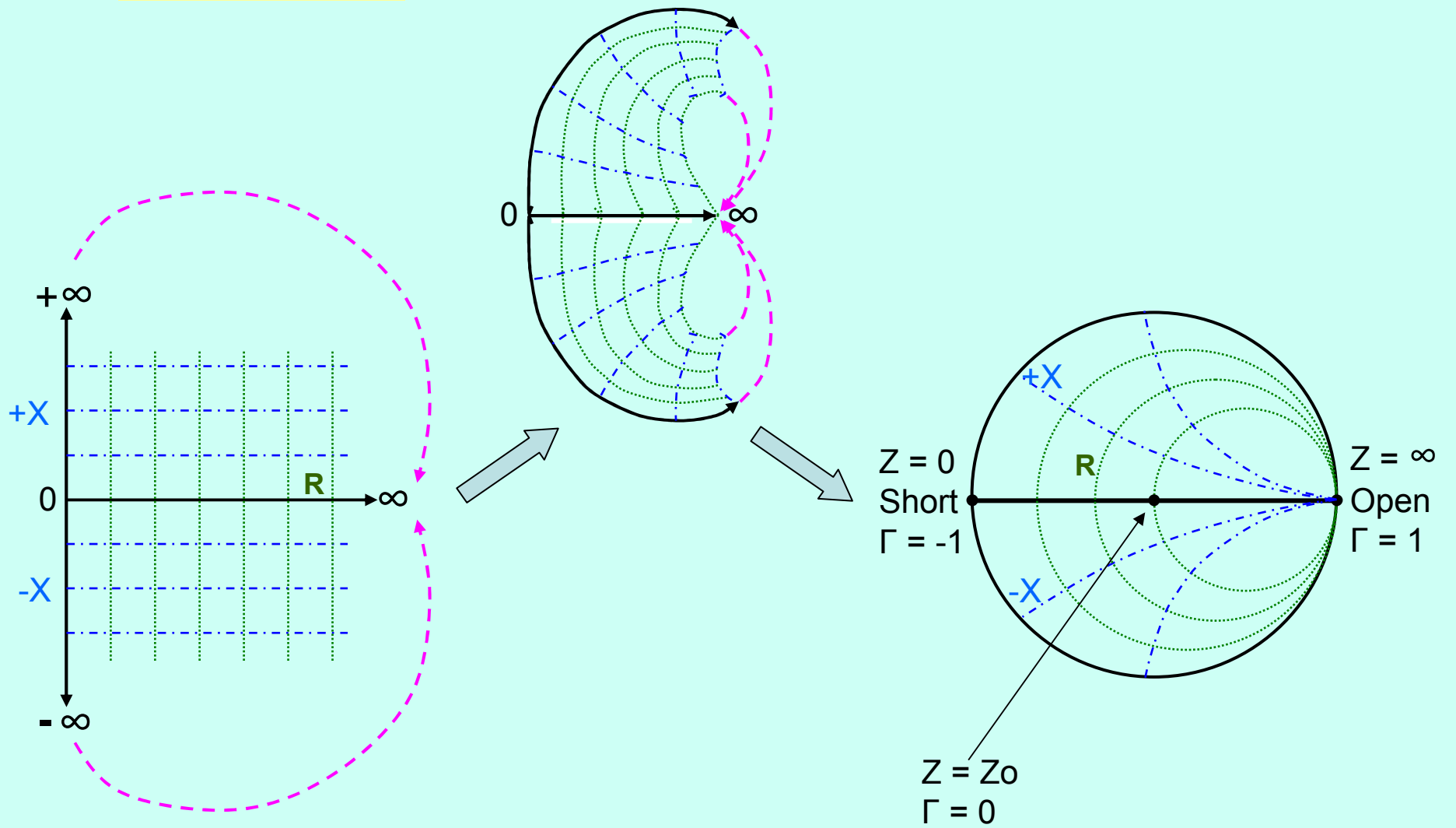

A Basic Scalar Analyzer

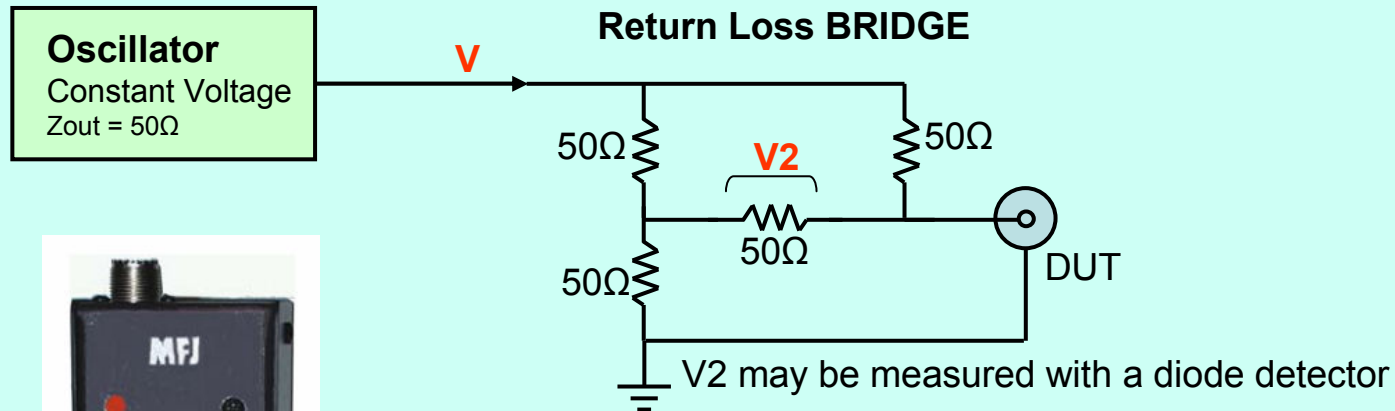One VOLTAGE MEASUREMENT allows measuring the SWR



Example of a basic SWR Analyzer: MFJ 207

V_2 voltage magnitude is measured with V constant.

V_2 corresponds to the magnitude of $\Gamma \rightarrow$ SWR

Measures SWR directly – but not so accurate



Cannot measure high SWR

Measures Trap Resonant Frequency and Q factor



Coax Impedance up to 100Ω

Ferrite Impedance magnitude. And more...

Trap Resonant Frequency

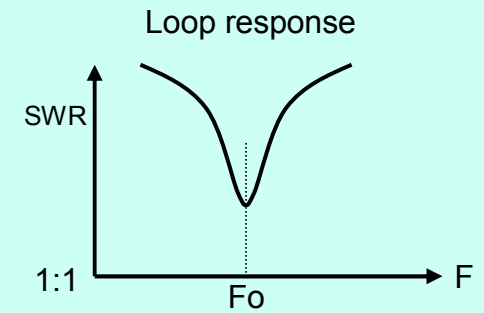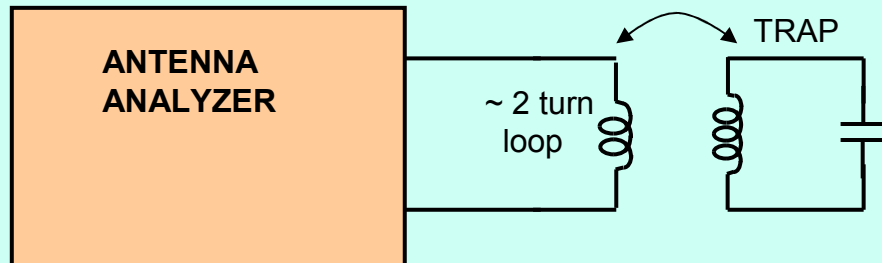

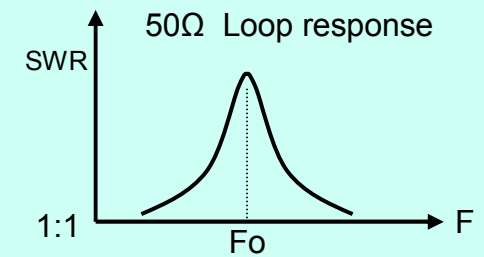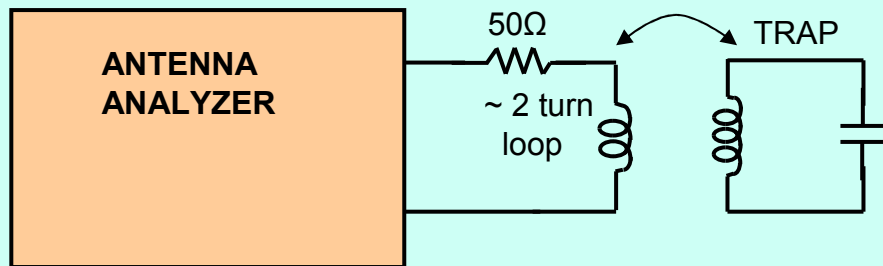In both cases:
the coupling loop is lightly
coupled to the trap to measure
the resonant frequency F_0 .



Q factor Measurement

Ref: http://ve2azx.net/technical/Q-FactorMeas_on_LC_Circuits.pdf

As before use a coupling loop (without the 50 Ω resistor)

Adjust the coupling to get 1:1 SWR at the resonant frequency F_o


Change the frequency to get an SWR of 2.6:1.

Record the TWO frequencies F_1 and F_2 that give an SWR of 2.6:1

Compute $Q = \frac{F_o}{F_2 - F_1}$

Example: $F_o = 7.100$ MHz, $F_2 = 7.135$ MHz, $F_1 = 7.064$ MHz

$$Q = \frac{7.1}{7.135 - 7.064} = 100$$

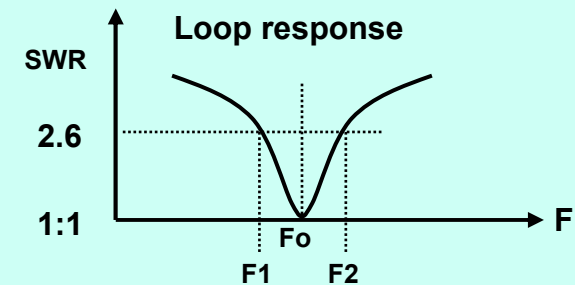

Mesuring the Impedance of a Coax Using an SWR Analyser (up to 100Ω)

Connect the cable to the SWR analyzer and **terminate the other end with a 50 ohms load**.

Measure the SWR. If you get 1:1, then the cable impedance is 50 ohms.

If the SWR is above 1:1, change the frequency to **maximize** the SWR reading.

Calculate the required frequency (F in MHz), which is related to the cable length L in feet :


$$F = 185 / L \quad (\text{This is approximately the quarter wavelength frequency})$$

Calculate Z_{cable} at the **frequency where the SWR is maximum**, or use the graph below:

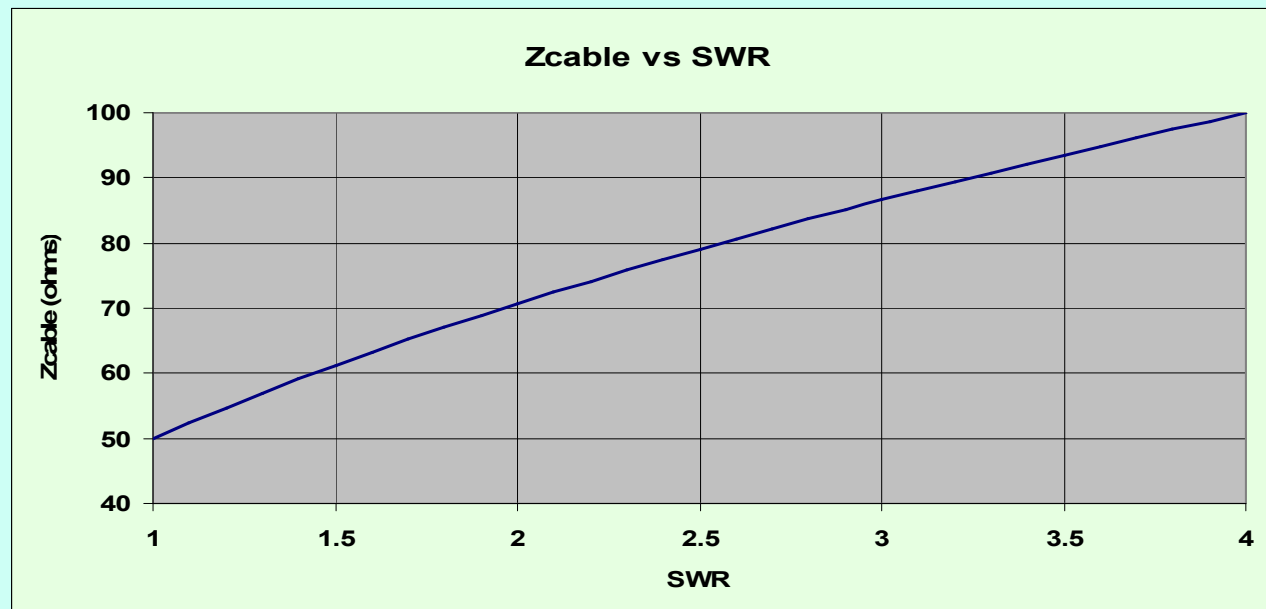
Exemple: SWR = 2.25 gives $Z_{\text{cable}} = 75$ ohms

$$Z_{\text{cable}} = 50 * \sqrt{\text{SWR}}$$

NOTE: This technique is valid for Z_{cable} from 50 ohms to 100 ohms.



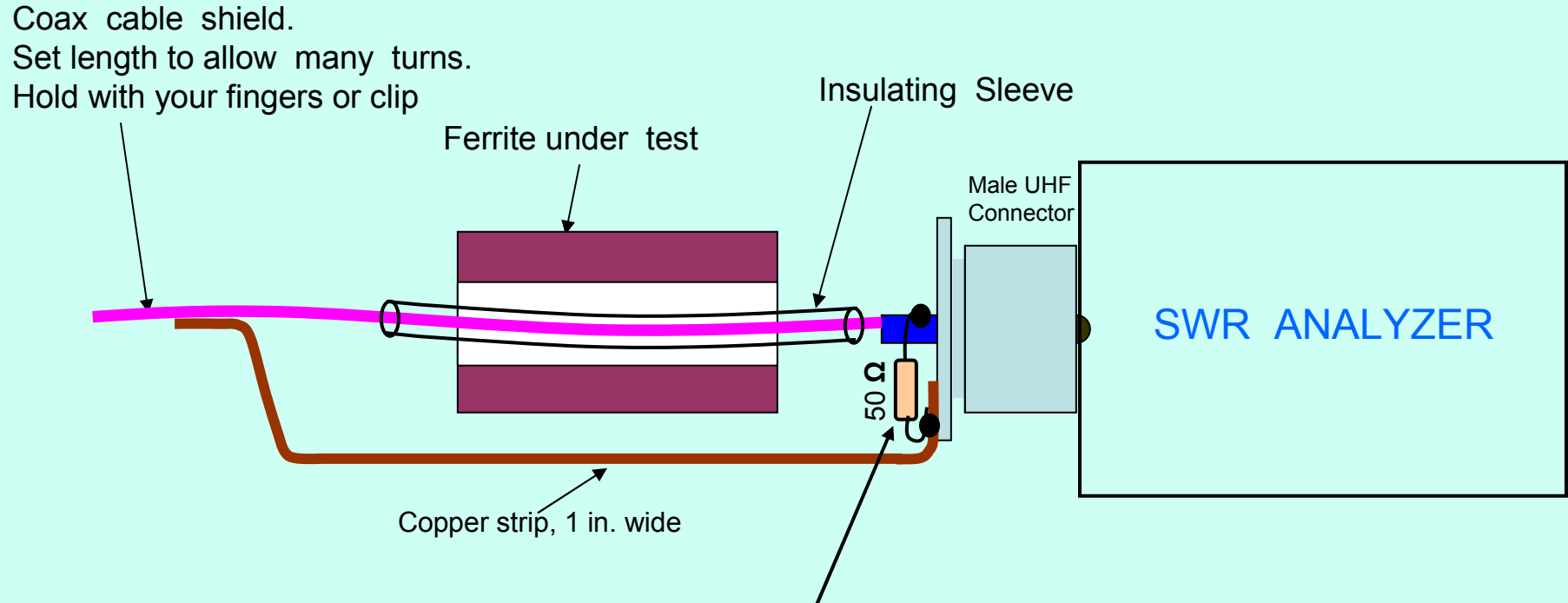
CHECK YOUR FERRITES WITH YOUR SWR ANALYZER




The ferrite is in parallel with the 50 ohms (1%) termination

NOTE: This technique may be used to check the impedance of an antenna, or any other device, by using a coaxial Tee and a 50 Ω termination.

FERRITE IMPEDANCE VS MEASURED SWR

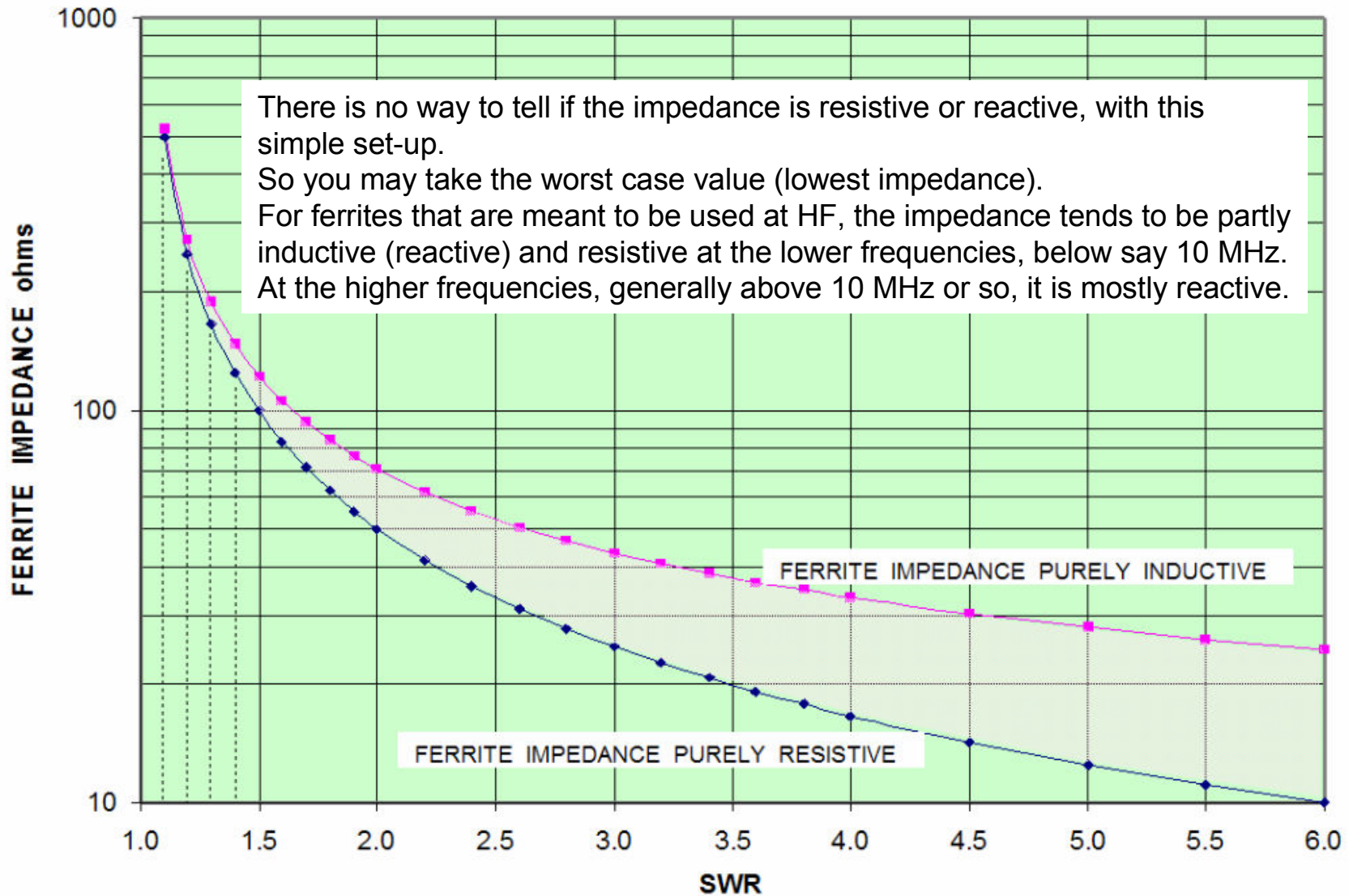

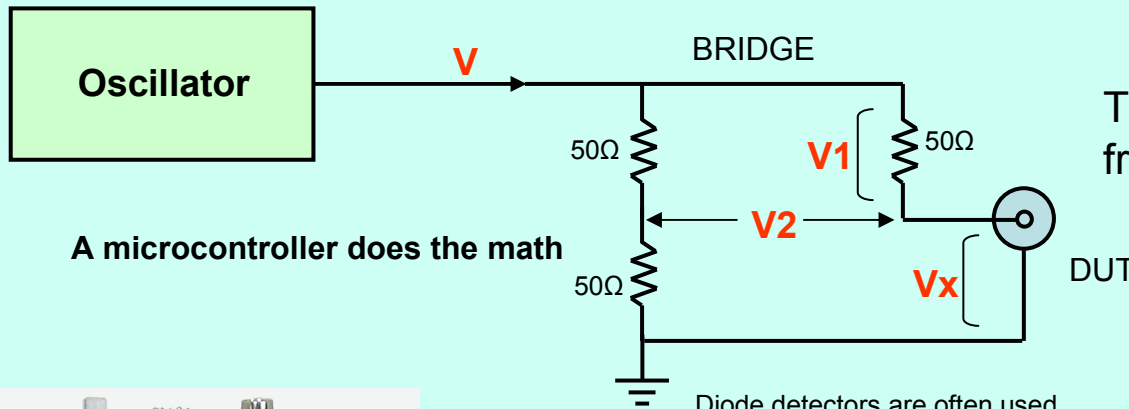
Three VOLTAGE MEASUREMENTS allow Measuring Resistance and Reactance, but NOT the sign



The impedance is computed from V_x , V_1 and V_2

A microcontroller does the math

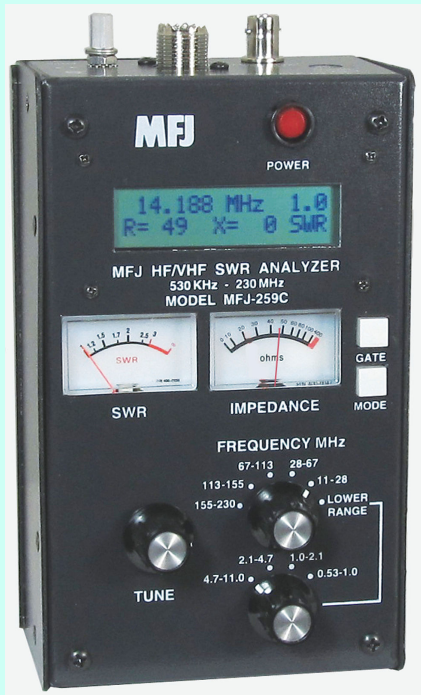Diode detectors are often used. Non linearities limit dynamic range and must be calibrated out.




The classical MFJ259

- More accurate than the MFJ 207**
- Measures Impedance Magnitude, R_L , RefCo (Γ)**
- Measures capacitance and inductance**
- Measures Coax losses**
- Broadband detectors make it susceptible to interferences.**

The Vector Analyzer

Measure Resistance and Reactance, including the sign

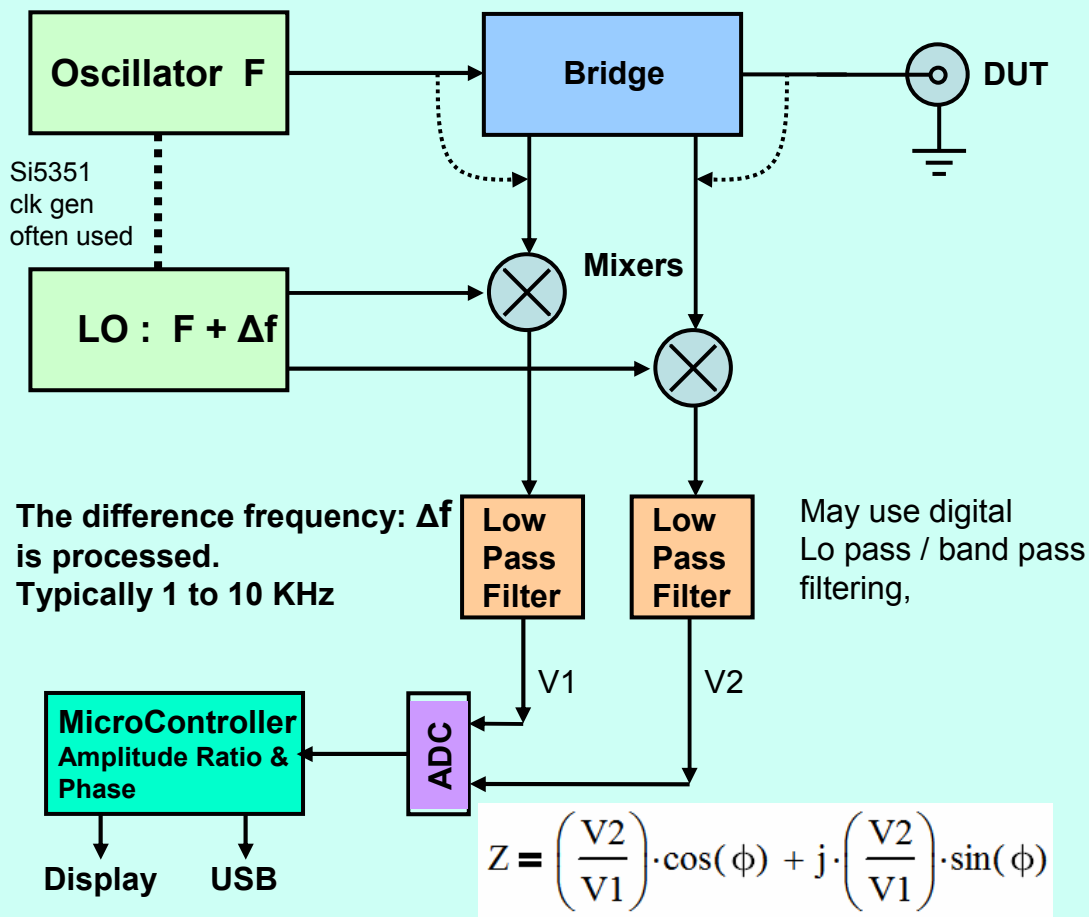Typical system based on super-heterodyne receiver



Potentially larger dynamic range
Since it has selective receivers

More accurate: OSL calibration
(Open, Short, Load) (No adj'nt inside)

Smith Chart Display

Q Factor of Components


USB link to power and control unit
from the computer. Easier !

Allows more complex
measurements. Ex: TDR, crystals.



Vector Analyzer Calibration

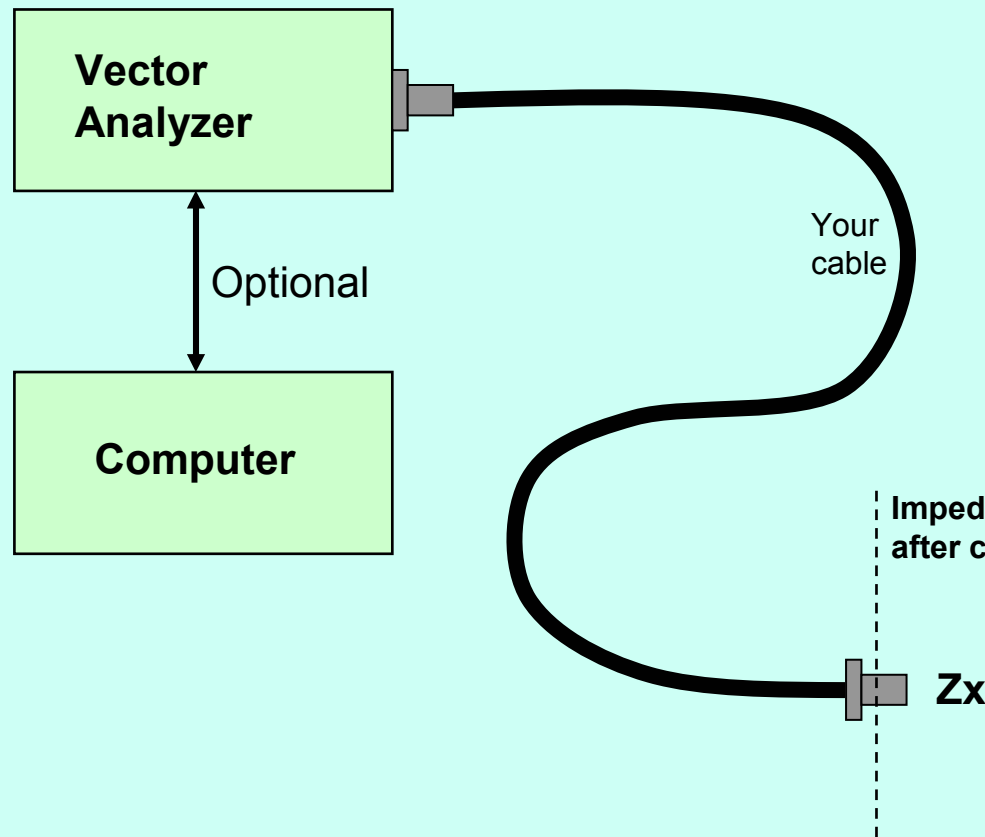The analyzer accuracy critically depends on three standards




The imperfections of the standards are described in a CAL KIT definition file.

They are taken into account when calculating the value of Z_x


Impedance Z_x is measured at the cable end after calibration with short, open and load.



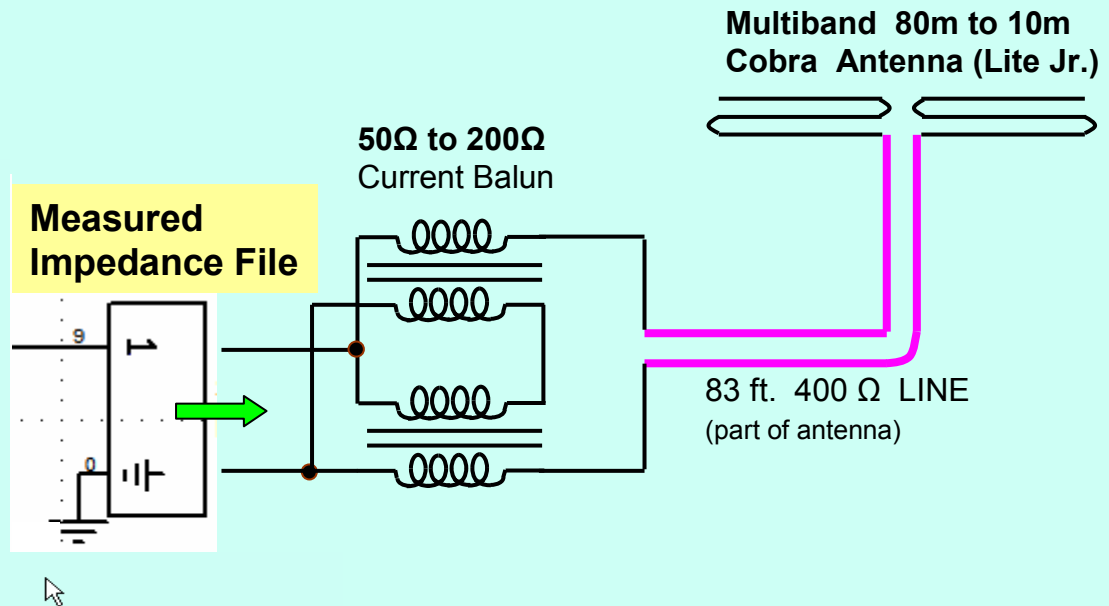Using a Vector Analyzer to design a Matching Network to correct Bad SWR across the 80m Band




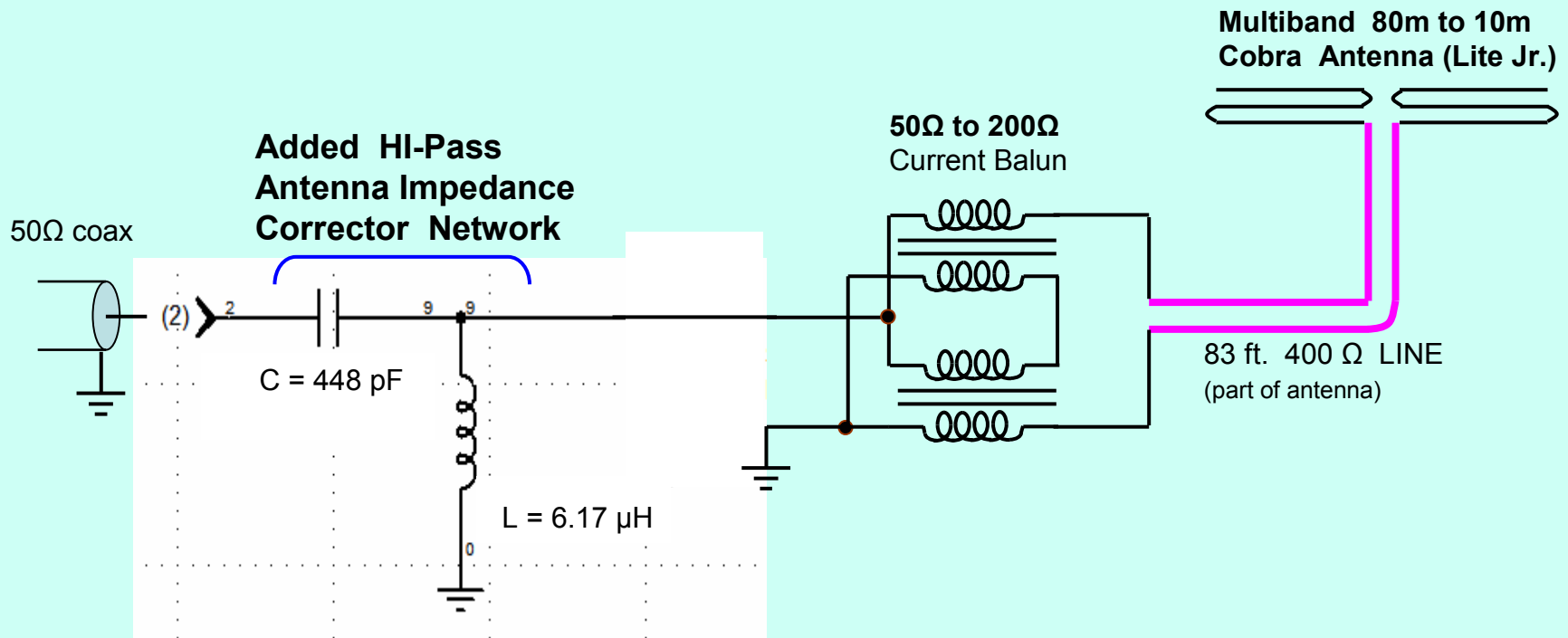Using a Vector Analyzer to design a Matching Network to correct Bad SWR across the 80m Band





C and L components were manually optimized in my RF simulator.

Antenna Impedance Corrector for 80m band

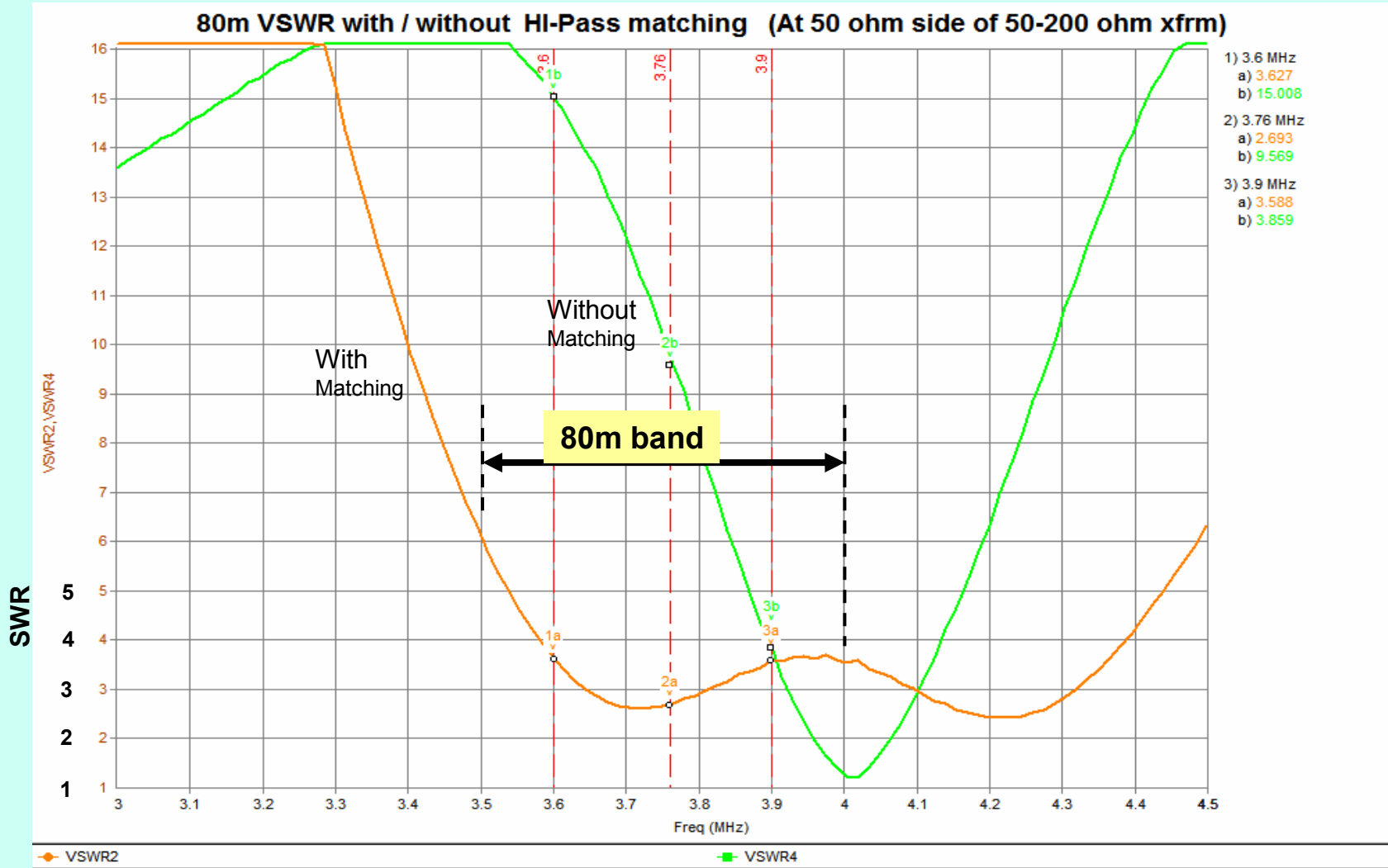


Antenna Impedance Corrector

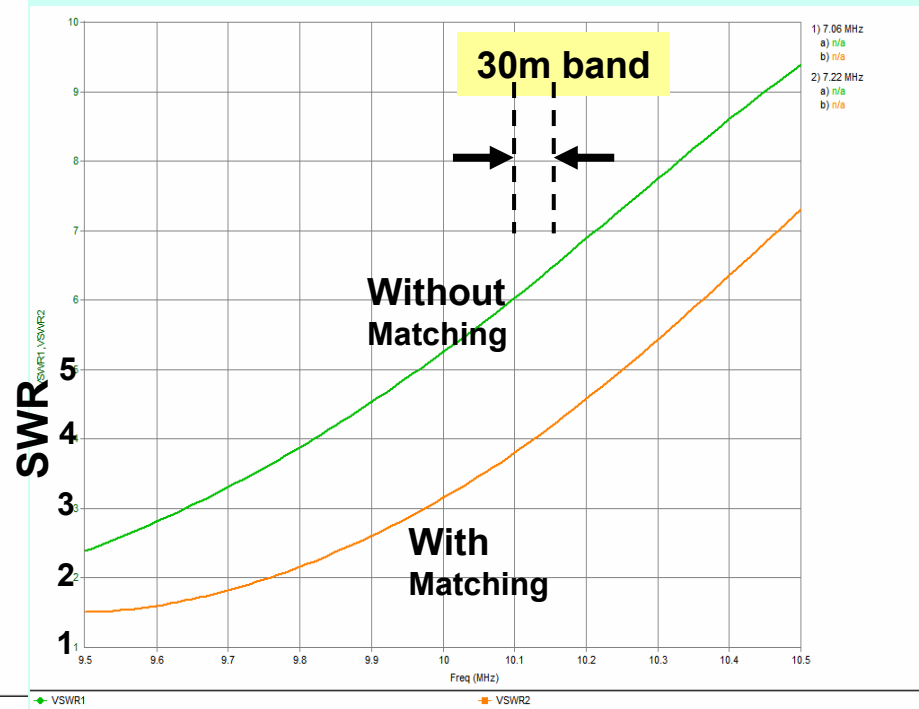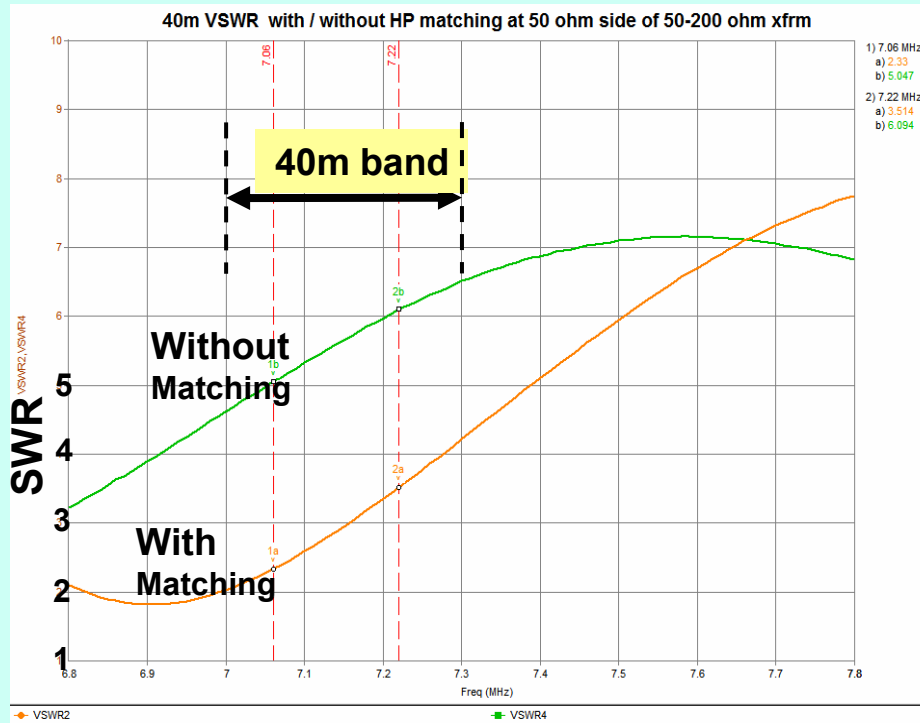SWR with / without Matching 40m and 30m Bands



Antenna Impedance Corrector

SWR with / without Matching 20m band

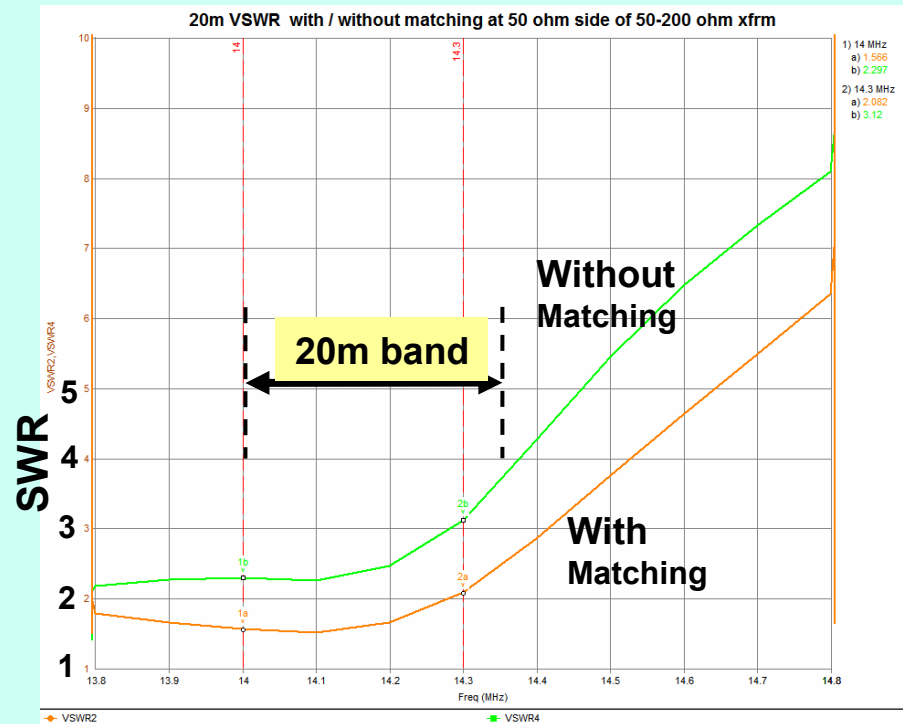

The effect of the impedance corrector decreases as frequency increases.

Using a Vector Analyzer to check if your tuner is operating within its matching range

MFJ 929 Tuner Spec's

- Impedance matching range : 6 to 1600 ohms
- SWR matching range : Up to 8:1 for < 50 ohms and up to 32:1 for > 50 ohms

MFJ 929 Tuner




Tuner losses increase as you get closer to its impedance/SWR limits.

The Vector Analyzer will allow you to check where you are on this chart

The Tuner will work properly when antenna impedances lie inside the green area

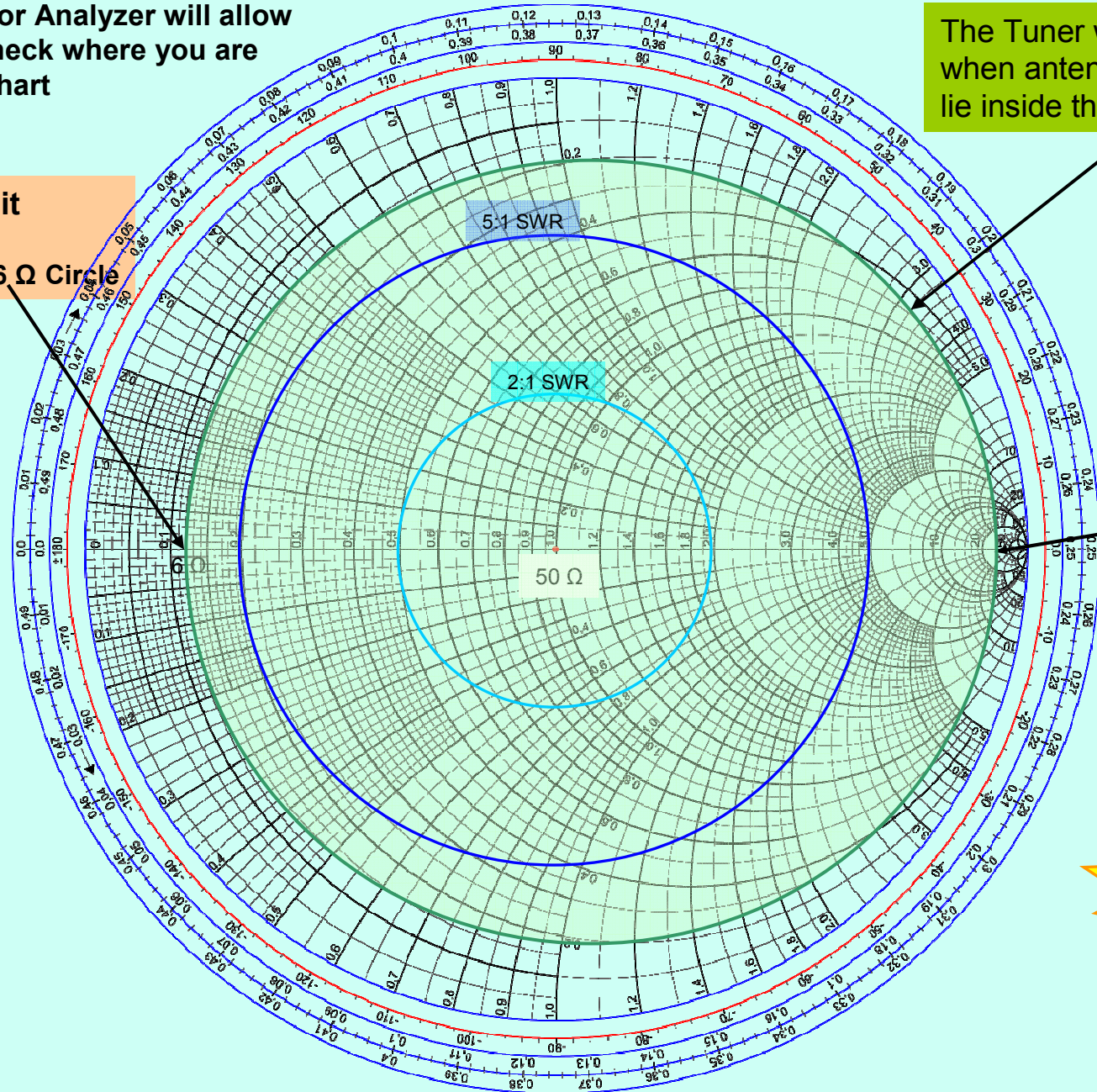
Tuner Limit
8:1 SWR
= $50\Omega / 8 = 6.25\Omega$ Circle



Tuner Limit
32:1 SWR
= $50\Omega * 32 = 1600\Omega$

Plot the Chart for every band.

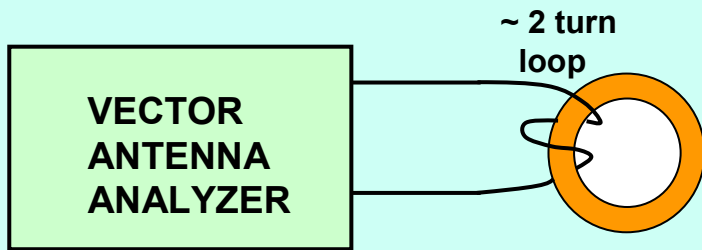Using a Vector Analyzer to Identify Ferrite type (Not for powdered Iron)




Adjust the frequency until **Resistance = Reactance**

The obtained frequency tells us:

Ferrite useable frequency range


The LOW frequency permeability → The material type

Material	Init Perm. μ_i	$F_{(X=R)}$ MHz	$F_{(X=R) MAX}$ MHz
61	125	45	
52	250	30	
51	350	20	
44	500	18	
46	500	8	
43	800	15	30
31	1500	3.5	10
77 (72)	2000	1.6	
78	2300	2	
73	2500	2	
75 (J)	5000	0.7	
76 (W)	10000	0.2	

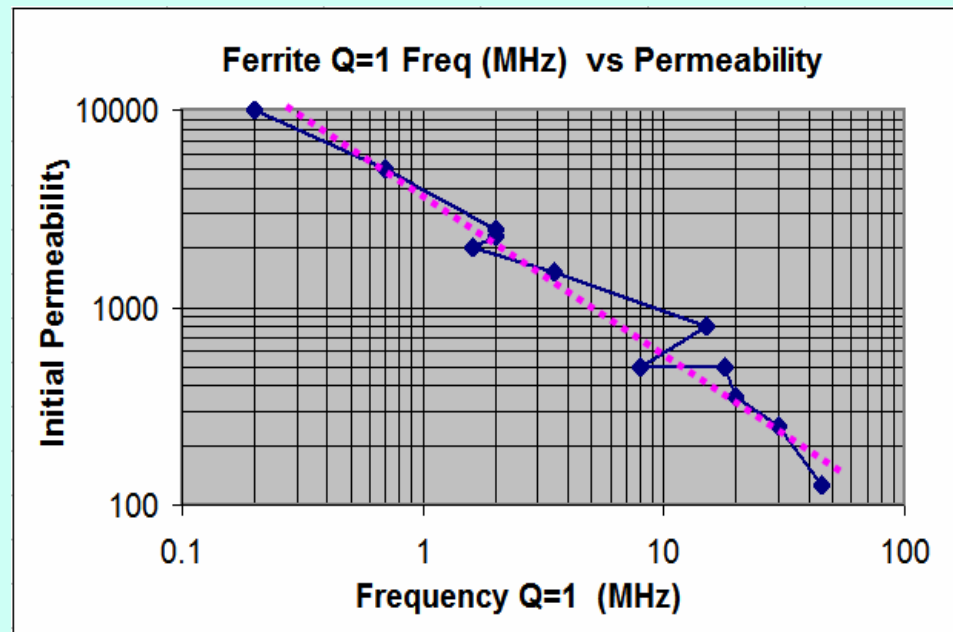


Measurement Examples Clamp-on Ferrite $\mu \sim 800$

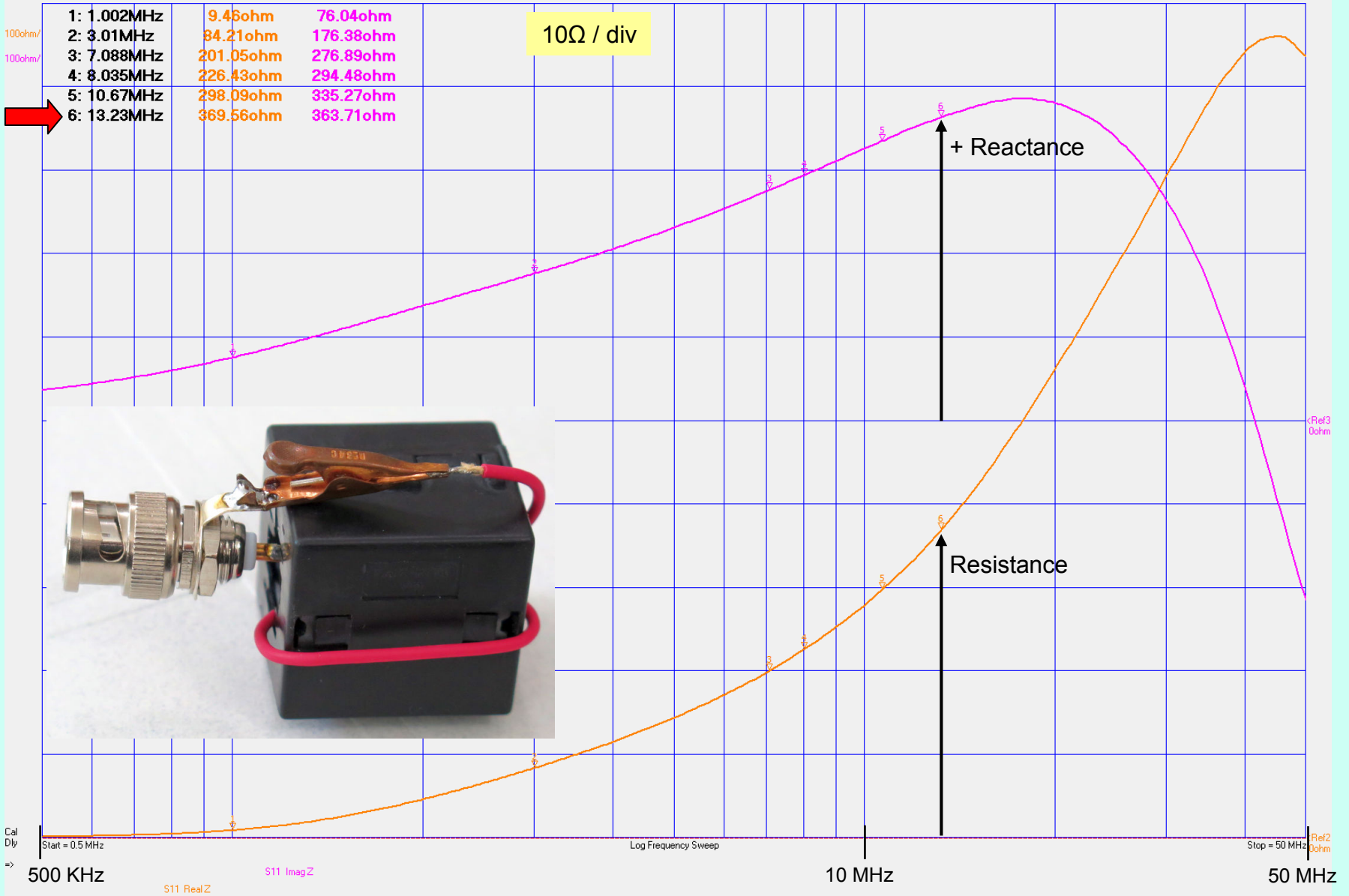DG85AQ Vector Network Analyzer Software
23/06/2019 11:02:56 AM BLACK SQUARE FERRITE




Measurement Examples Clamp-on Ferrite $\mu \sim 500$ Inductance and Z magnitude added

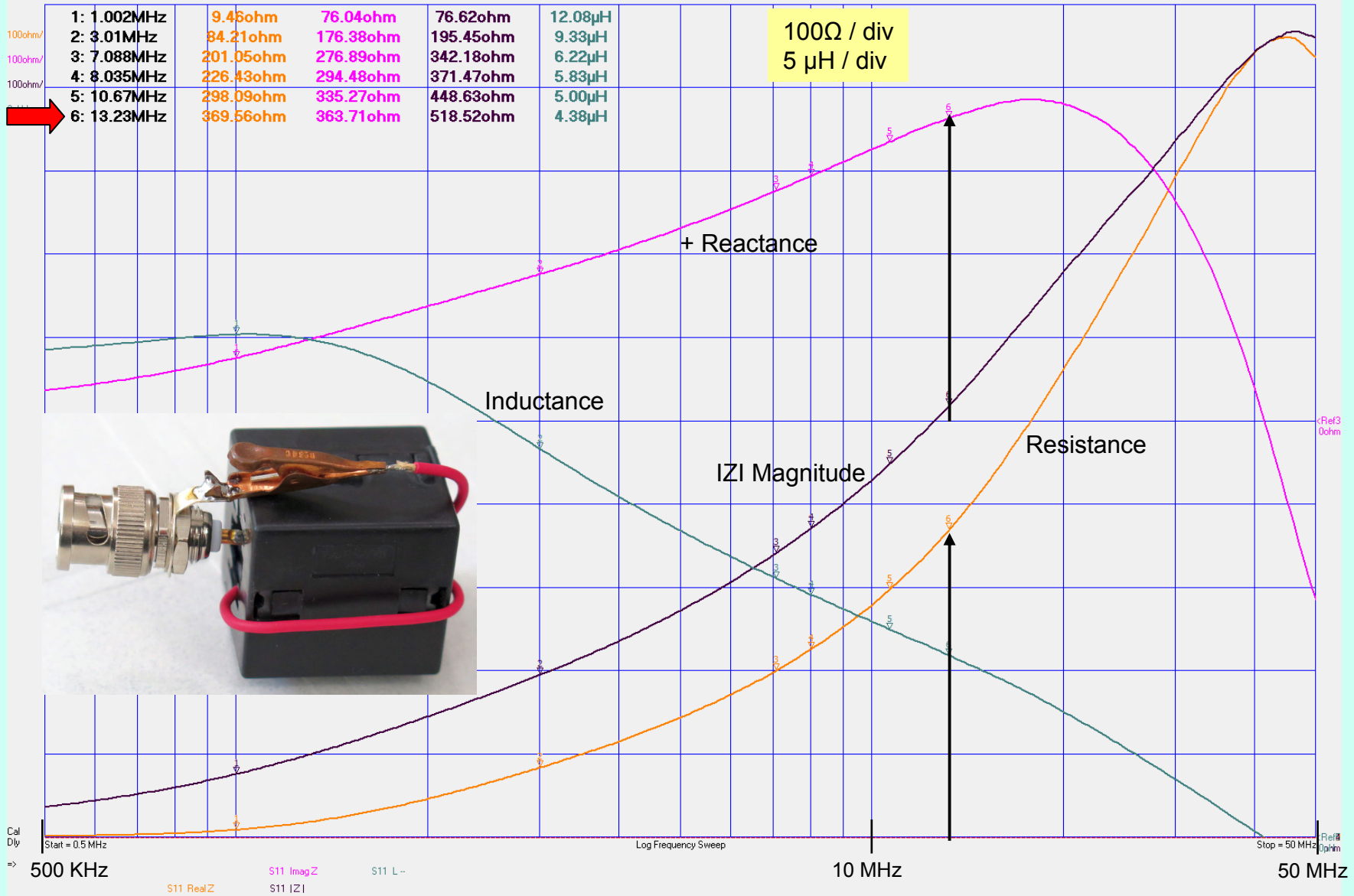DG8SAQ Vector Network Analyzer Software
23/06/2019 11:03:20 AM BLACK SQUARE FERRITE-1




Measurement Examples 0.5 in Ferrite $\mu = 5000$ from specs

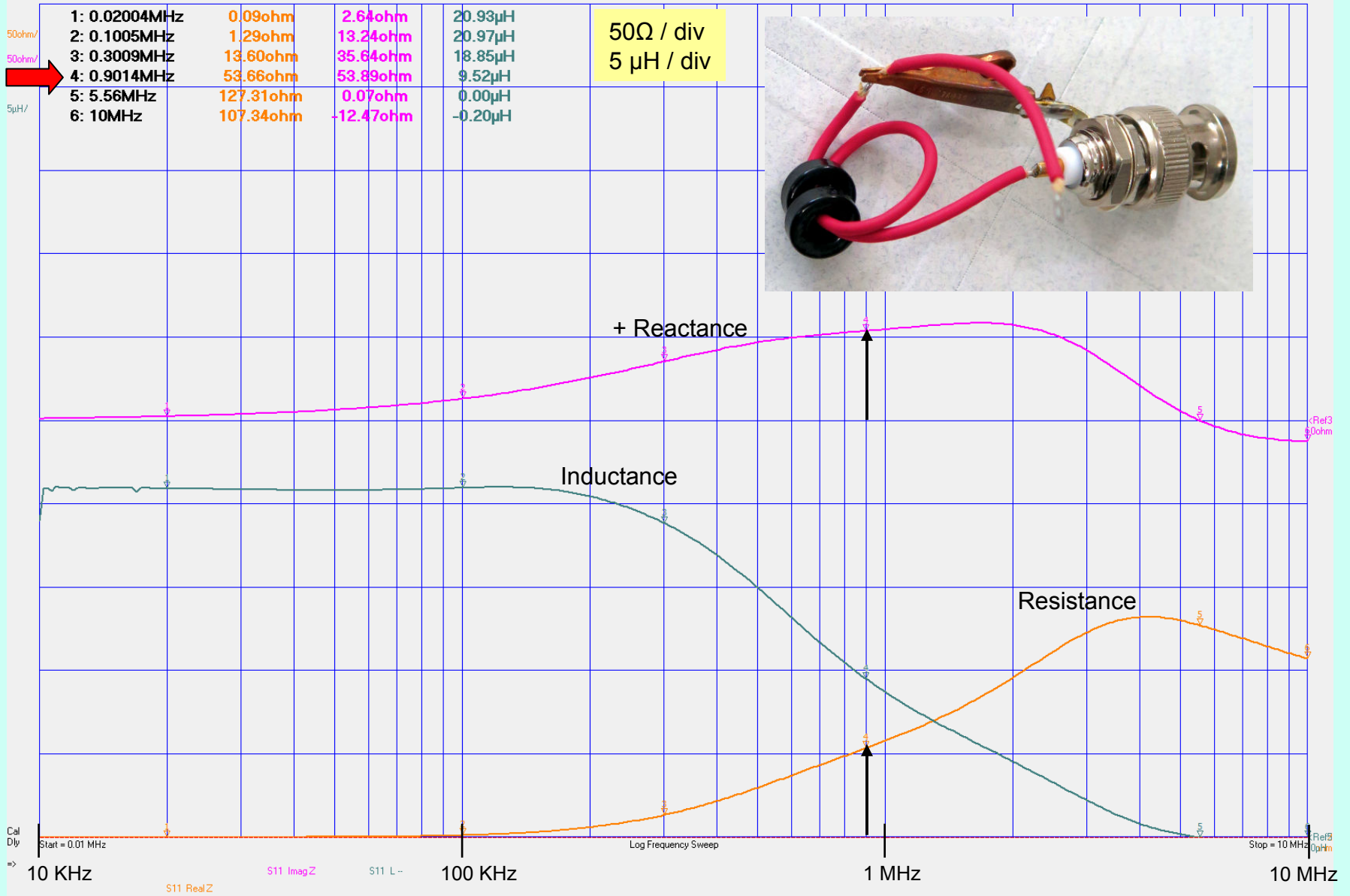DG85AQ Vector Network Analyzer Software
23/06/2019 11:44:42 AM 240-2522-ND Core 0.5 in u=5000




Measurement Examples 2.4 in Ferrite $\mu = 800$ from specs, #43 material

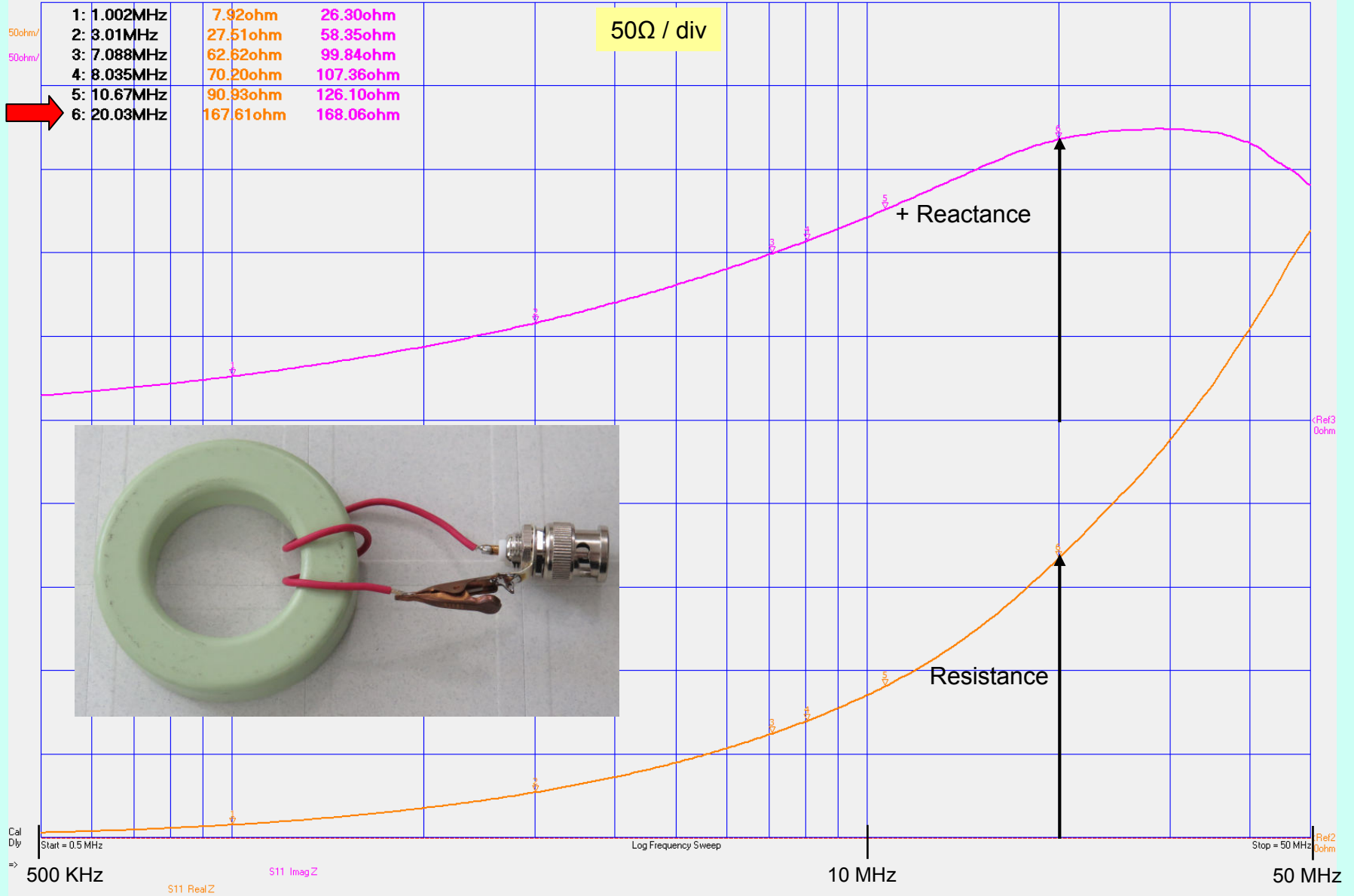DG85AQ Vector Network Analyzer Software
23/06/2019 11:13:58 AM FT-240-43 Core



Time Domain Reflectometry (TDR)

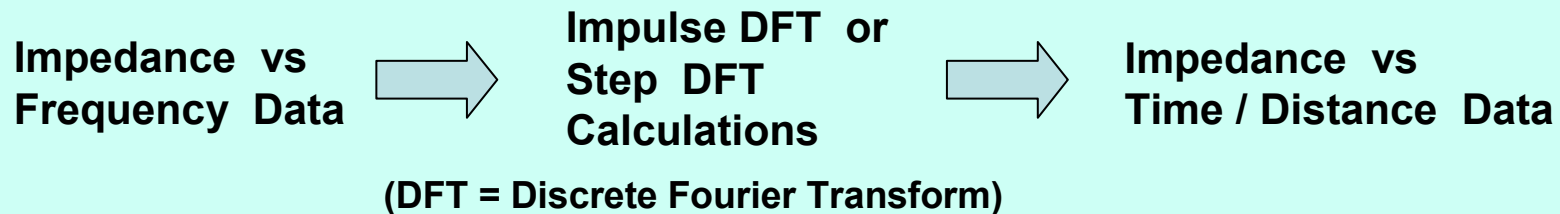

- Measure impedance values vs frequency and
- Transform them towards equivalent values along time.
- Distance is related to time via the Velocity Factor (varies from 0.66 to 0.95)

Need to use the whole frequency span to resolve small discontinuities.
Frequency sweep 10 KHz to 600 MHz, 2000 points

Allows testing coax cable discontinuities: shorts, opens, impedance (bumps), kinks...

$$\text{Time Resolution (sec)} \sim = \frac{1}{10 * \text{Freq span (Hz)}}$$


$$\text{Max Time Span (sec)} \sim = \frac{\text{\# of freq points}}{2 * \text{Freq span (Hz)}}$$

340 m

$$\text{Distance Resolution (cm)} \sim = \frac{3 * V_f}{\text{Freq span (GHz)}} \rightarrow 1.7 \text{ cm at 600 MHz span}$$


Using a Vector Analyzer to Measure the IMPEDANCE PROFILE of 50Ω feed line of my sloper antenna

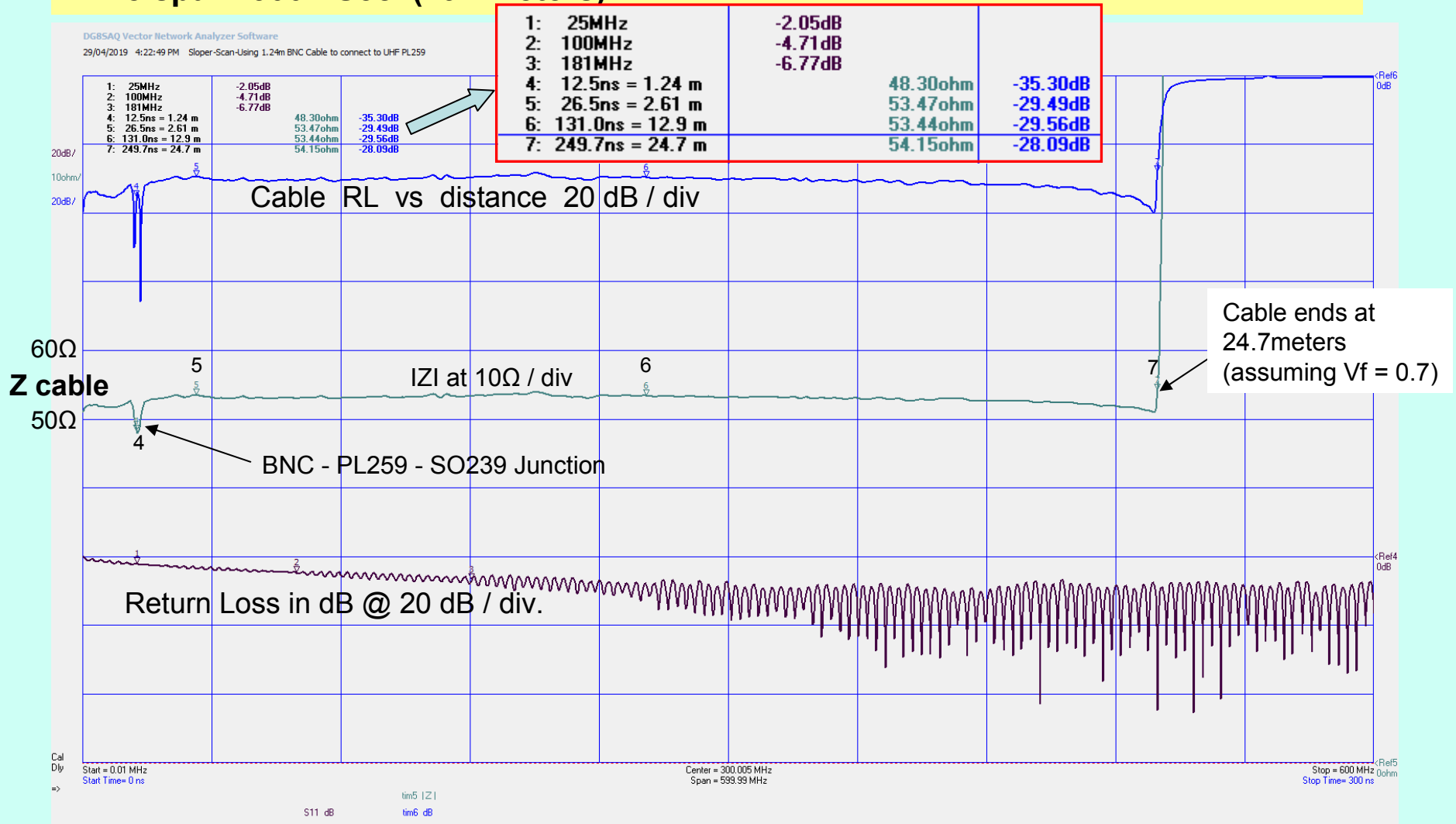Frequency sweep 10 KHz to 600 MHz, 2000 points
Time span: 300 nSec (29.7meters)




Verify IZI vs cable length to identify line shorts/opens.

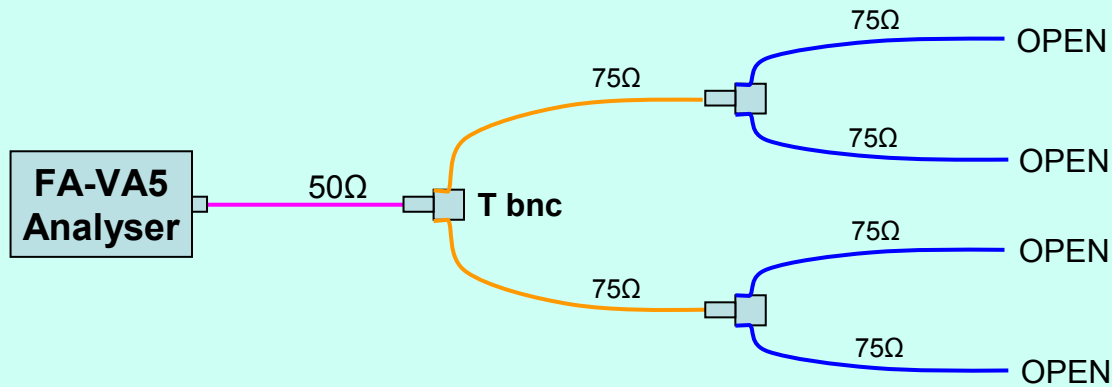IMPEDANCE PROFILE Measurement on a Phasing Harness of a Four Loop VHF Antenna.
No loop present Frequency sweep 10 KHz to 600 MHz, 2000 points



Verify IZI vs cable length to identify line shorts/opens.

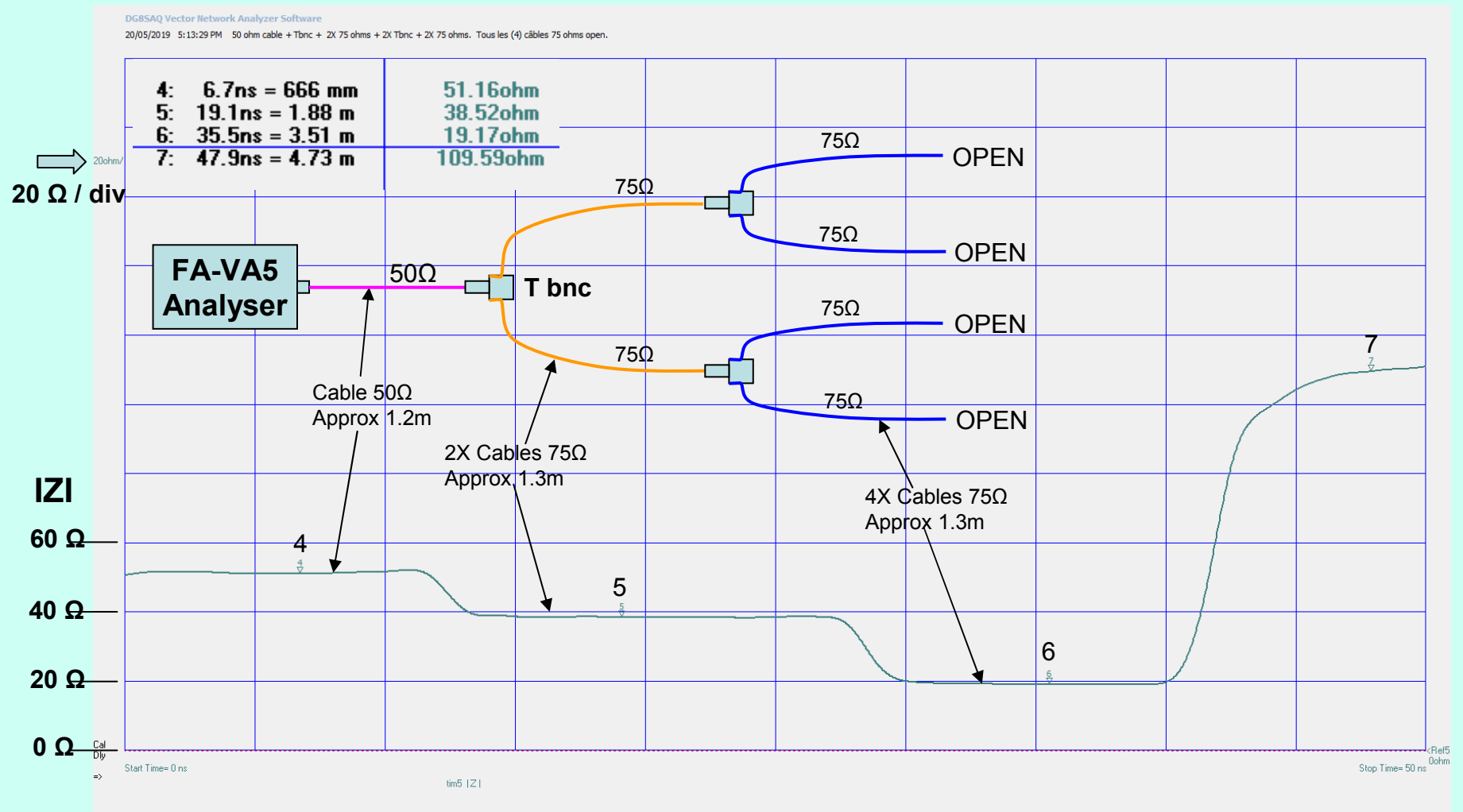IMPEDANCE PROFILE Measurement on a Phasing Harness of a Four Loop VHF Antenna.
 No loop present Frequency sweep 10 KHz to 600 MHz, 2000 points




Quartz Crystal Testing


Access the TOOLS Menu of VNWA Software. Sweep was 101 points +/- 1% of frequency, Precise Mode. Measures the crystal impedance over a narrow range of frequencies. Need to have 1 Hz resolution here.

From this data, the VNWA software derives the crystal equivalent circuit

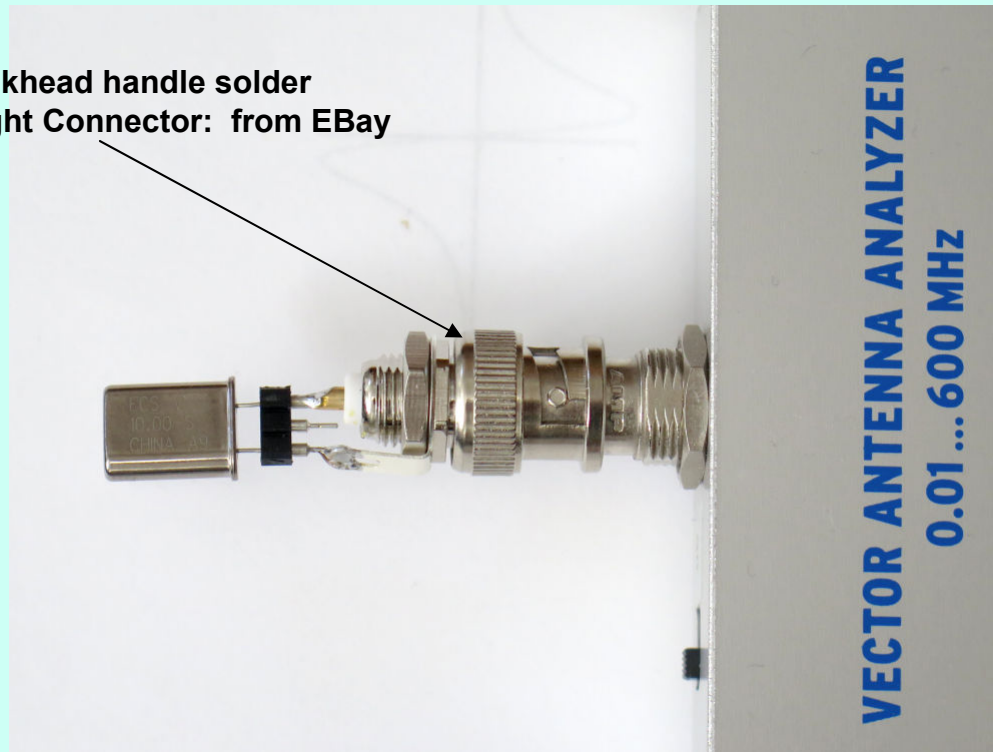BNC male plug bulkhead handle solder panel mount straight Connector: from EBay



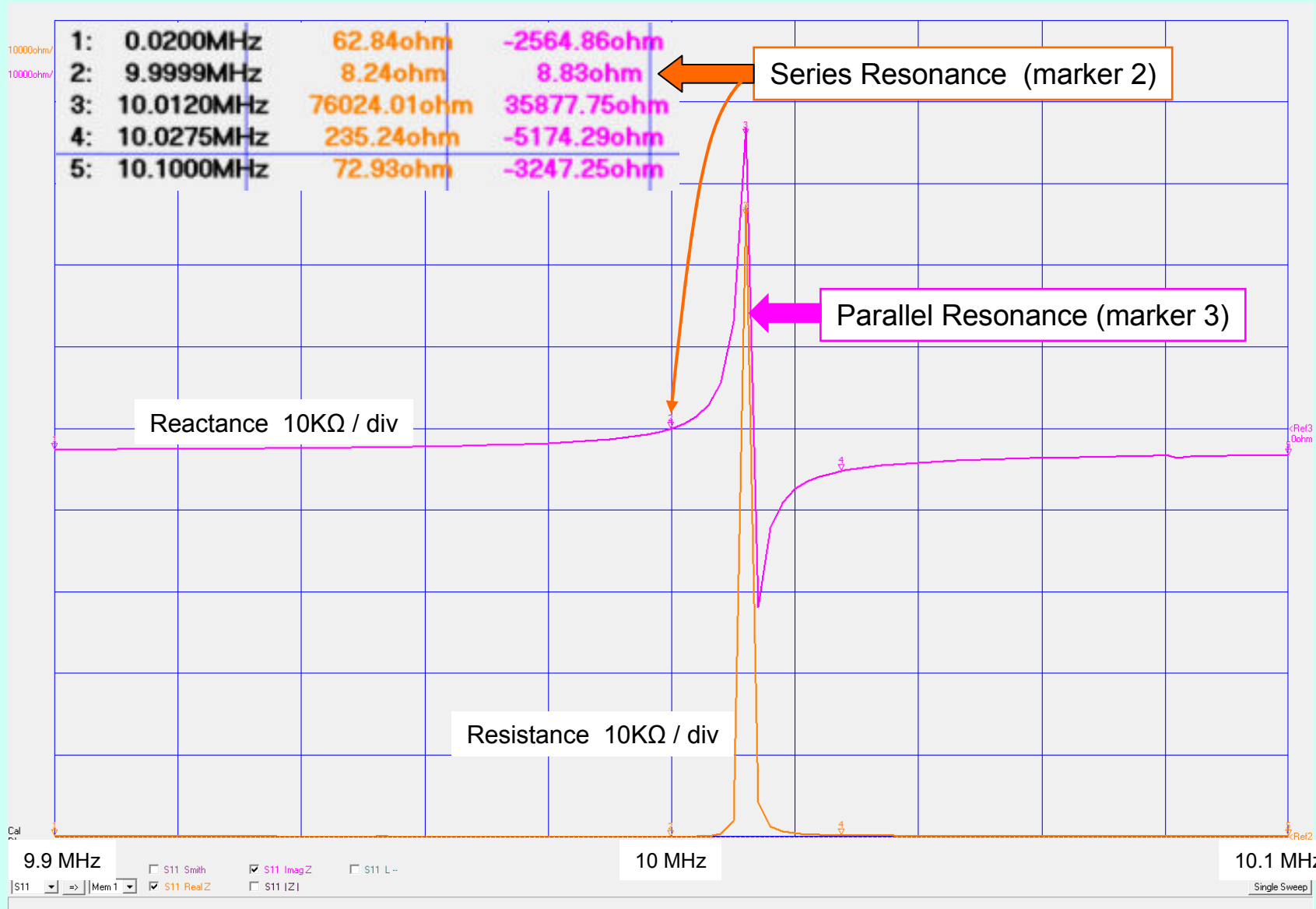Measured Resistance and Reactance of 10 MHz Crystal




Measurement Results on a 10 MHz crystal Repeated 5 times.

The VNWA software fits the element values to the measured data

Crystal Analyzer - Analysis will be performed into 3-port data spaces s_11 and s_21 !!!

Equivalent Circuit

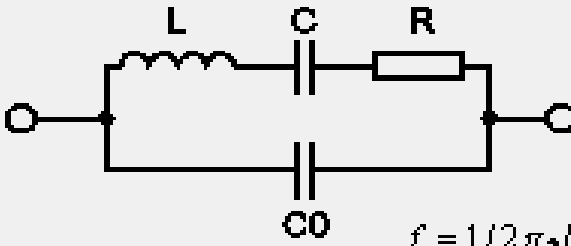

$L = 13.23296 \text{ mH}$
 $C = 19.14262 \text{ fF}$
 $R = 8.2970438870511 \text{ Ohm}$
 $C0 = 4.8270520441794 \text{ pF}$
 $f = 1/2\pi\sqrt{L \cdot C} = 9.9997888072102 \text{ MHz}$
 $R \cdot Q = \sqrt{L/C} = 831.43420892701 \text{ x1000}$

Q = 100208

source = S11 Transmission Test Jig Impedances = 50 Ohms

Batch Crystal Analyzer

#	f / Hz	Q	L / H	C / F	R / Ohm
1	9999786.039	106713	0.01381190026	1.834025688E-14	8.13
2	9999789.986	100701	0.01337477724	1.893964992E-14	8.34
3	9999796.192	103122	0.01367100922	1.852923074E-14	8.33
4	9999796.295	102048	0.01364758271	1.856103637E-14	8.4
5	9999788.807	100208	0.01323296589	1.914262159E-14	8.3

10 Hz max Freq. delta

Verify the Accuracy of your Analyzer


These tests apply to the full frequency range of the analyzer.

Connect a 50Ω termination at the analyzer input. Check SWR. Should be $< 1.1:1$

Connect two 50Ω terminations at the analyzer input, using a Tee.
Check SWR. Should be $2:1$


Connect a 100Ω termination at the analyzer input. Check SWR. Should be $2:1$

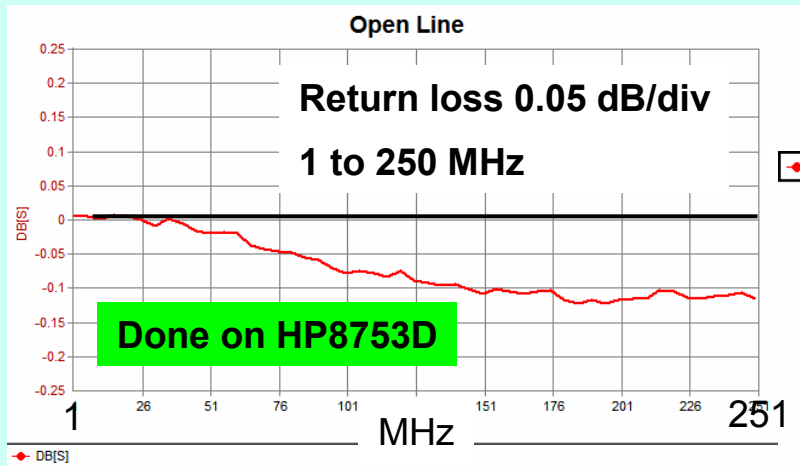VNA acid test : Measurements at / close to infinite SWR using an Open Line




Return loss sweep on an OPEN low loss line @ 0.05 dB / div.
Must always stay at / below 0 dB

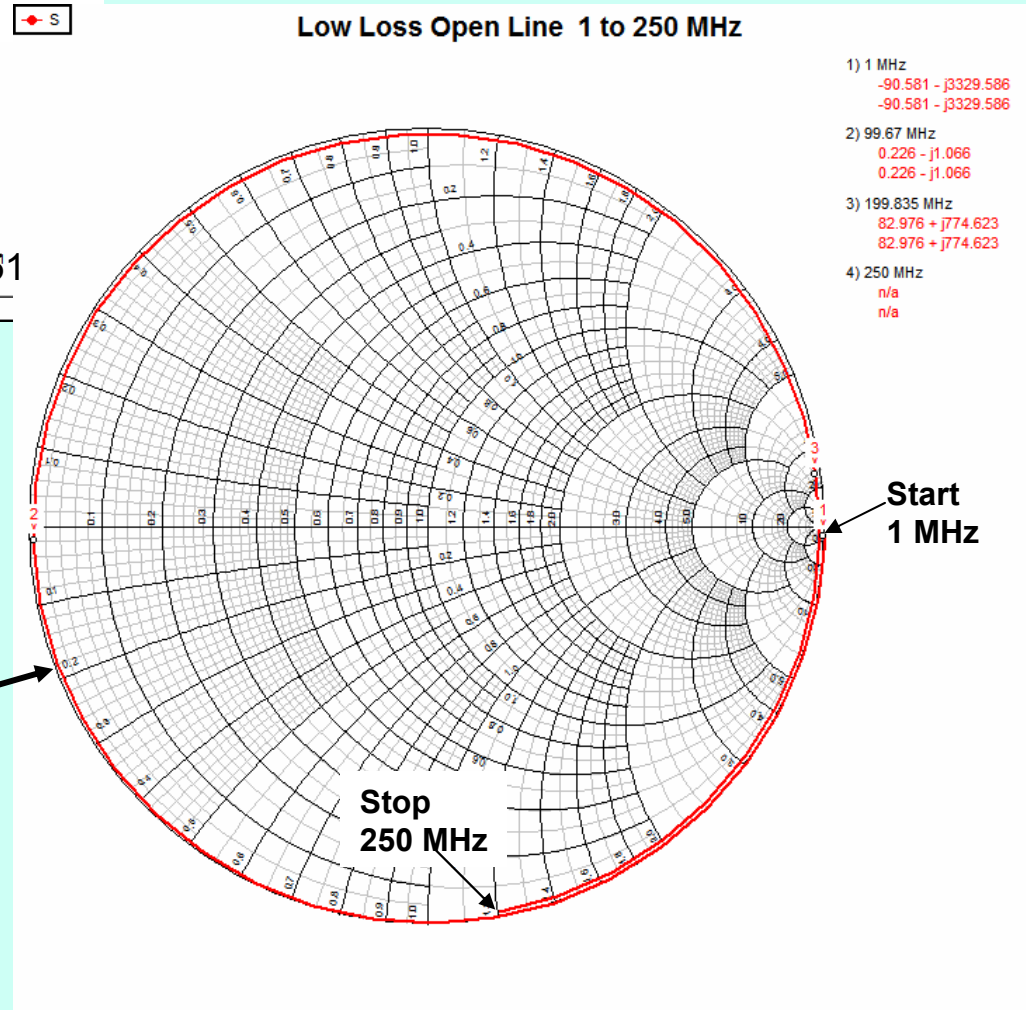Smith chart shows a well behaved S11 curve
 circling progressively inside:
 -> **Cal Kit Data OK**
 -> **Analyzer is accurate**



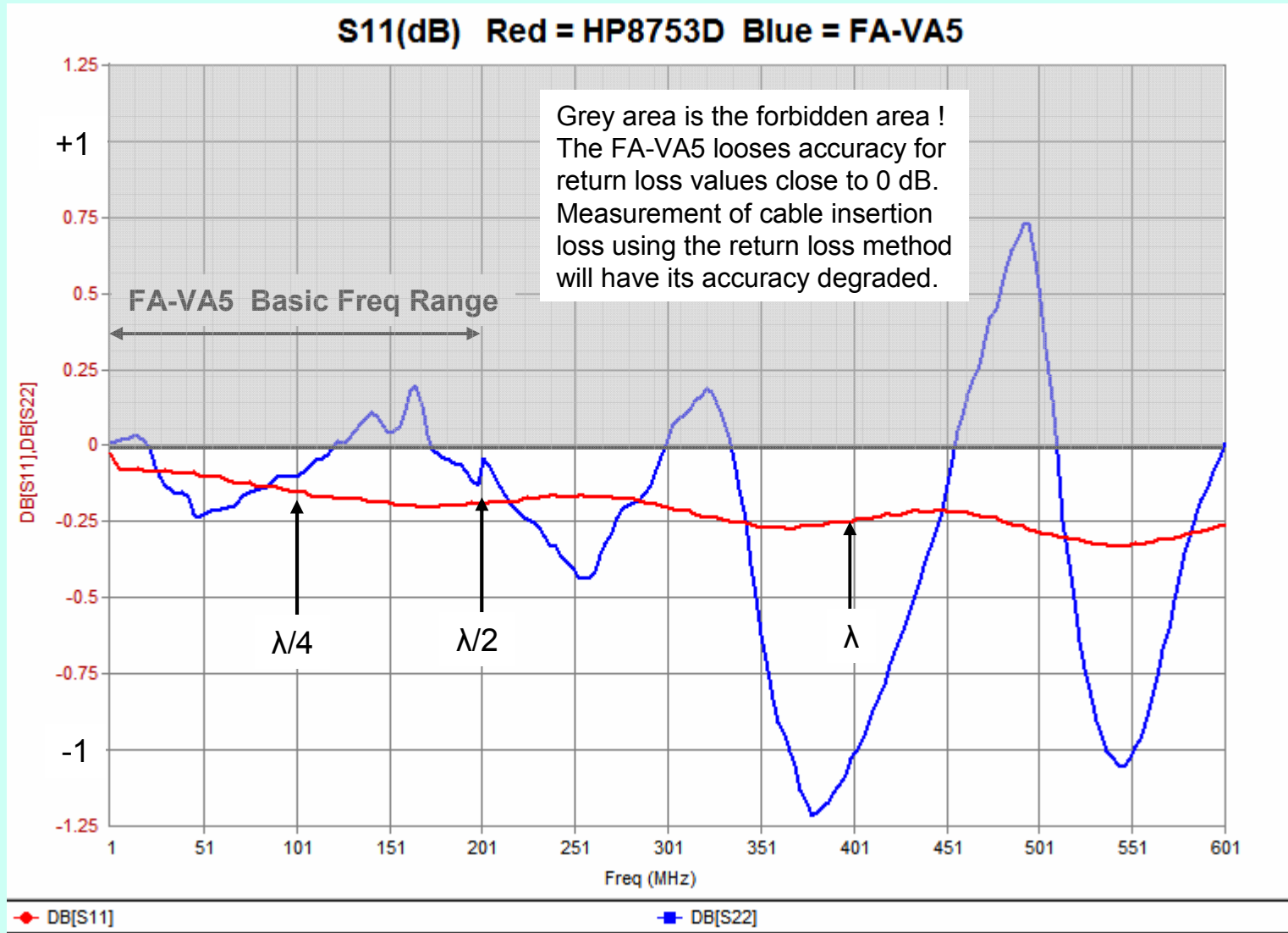VNA acid test : Measurements at / close to infinite SWR on an Open Line



About your Calibration Standards

Measurement accuracy never better than the standards used

CAL KIT definitions:

SHORT: *delay* in pS and frequency dependant *inductance and resistance*

OPEN: *delay* in pS and frequency dependant *capacitance*

LOAD: *delay* in pS and actual *resistance* plus *series inductance* and *shunt cap.*

The VNA software must “know” these CAL KIT parameters via a CAL KIT file !

Most important above 30 MHz

References

FA-VA5 Presentation: <https://www.youtube.com/watch?v=X8Z7veGV57o>

Understanding the Fundamental Principles of Vector Network Analysis
<https://literature.cdn.keysight.com/litweb/pdf/5965-7707E.pdf>

A short review of antenna and network analyzers:
<https://rigexpert.com/a-short-review-of-antenna-and-network-analyzers/>

Q Factor Measurement on L – C Circuits:
http://ve2azx.net/technical/Q-FactorMeas_on_LC_Circuits.pdf

Check your ferrites with your SWR Analyzer:
http://ve2azx.net/technical/Check_your_Ferrites.pdf

Questions ?

Jacques Audet VE2AZX
September 2019 Rev. April 2023
Web: ve2azx.net